

## Quiescent Operating Point, DC Load Line, AC without Load, and AC with Load Analysis

Source: Electronic Devices: A Design Approach Ali Aminian and Marian Kazimierczuk, 2004

Reference Figure 6-1

### Determine Quiescent Point $I_{CQ}$ and $V_{CEQ}$

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2} = 12 \frac{5100}{17600 + 5100} = 2.7 \text{ Volts}$$

$$V_E = V_B - V_{BE} = 2.7 - 0.7 = 2 \text{ Volts}$$

$$I_E = \frac{V_E}{R_E} = \frac{2}{1000} = 2 \text{ mA}$$

$$V_{CE} = V_{CC} - I_E(R_C + R_E) = 12 - 2 \times 10^{-3} (2000 + 1000) = 6 \text{ Volts}$$

$$I_{CEQ} = I_C = I_E = 2 \text{ mA}$$

$$V_{CEQ} = V_{CE} = 6 \text{ Volts}$$

### DC Load Line

$$V_{CE \text{ Cut-off}} = V_{CC} = 12 \text{ Volts} \quad I_{C \text{ Sat}} = \frac{V_{CC}}{R_C + R_E} = \frac{12}{2000 + 1000} = 4 \text{ mA}$$

### AC Load Line (without Load)

$$I_{o(NL)} = I_{CQ} + \frac{V_{CEQ}}{R'} \quad \text{where } R' = R_C \quad I_{o(NL)} = 2 \times 10^{-3} + \frac{6}{2000} = 5 \text{ mA}$$

$$V_{o(NL)} = V_{CEQ} + I_{CQ} R' \quad \text{where } R' = R_C \quad V_{o(NL)} = 6 + 2 \times 10^{-3} (2000) = 10 \text{ Volts}$$

### AC Load Line (with Load)

$$I_{o(WL)} = I_{CQ} + \frac{V_{CEQ}}{R'} \quad \text{where } R' = R_C \parallel R_L \quad I_{o(WL)} = 2 \times 10^{-3} + \frac{6}{1000} = 8 \text{ mA}$$

$$V_{o(WL)} = V_{CEQ} + I_{CQ} R' \quad \text{where } R' = R_C \parallel R_L \quad V_{o(WL)} = 6 + 2 \times 10^{-3} (1000) = 8 \text{ Volts}$$

## Discussion

Reference Figure 6.2

The DC Operating Point sets the limits of the output signal swing.

All three load lines (DC, AC without Load, and AC with Load) pass through the operating point.

Note that the operating point is located at  $I_B = 20 \mu\text{A}$ . The maximum excursion of  $i_B$  is limited to  $20 \mu\text{A}$  below the operating point and  $20 \mu\text{A}$  above the operating point for a total of  $40 \mu\text{A}$  peak-peak, which results in a swing of  $i_C$  of  $4 \text{ mA}$  peak-peak and a corresponding swing of  $v_{CE}$  of  $8 \text{ V}$  peak-peak.

For fine grain values, refer to Figure 6.2. For the AC Load Line without Load, the relative values are  $i_C$   $1.9 \text{ mA}$  to  $2.1 \text{ mA}$  ( $4 \text{ mA}$  peak-peak) and  $v_{CE}$   $4.2 \text{ V}$  below  $V_{CEQ}$  ( $6.0 - 4.2 = 1.8$ ) to  $3.8 \text{ Volts}$  above  $V_{CEQ}$  ( $6.0 + 3.8 = 9.8 \text{ Volts}$  ( $8 \text{ Volts}$  peak-peak)).

For the AC Load Line with Load (see Figure 6.8), the same limits apply to  $i_B$ , but now due to a change in slope of the AC Load with Load this corresponds to  $1.9$  and  $2.3 \text{ mA}$  ( $4.2 \text{ mA}$  peak-peak) change in  $i_C$  and a  $2.3$  and  $1.9 \text{ V}$  ( $4.2 \text{ peak-peak}$ ) in  $v_{CE}$ .

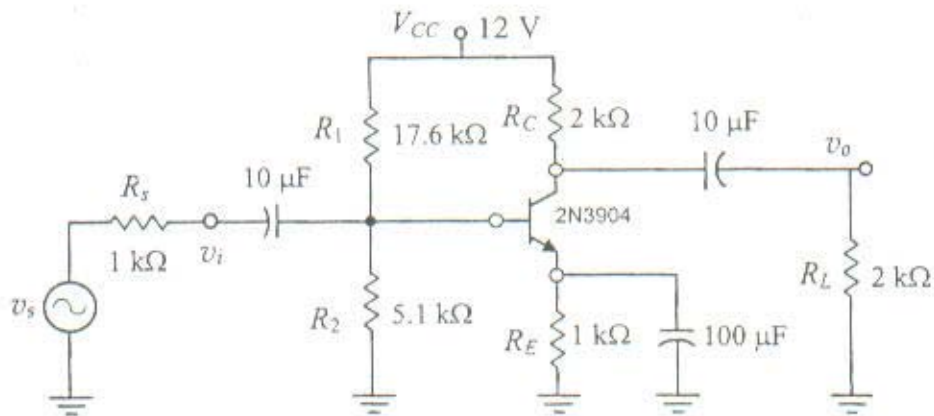


Figure 6-1: A voltage-divider biased common-emitter amplifier



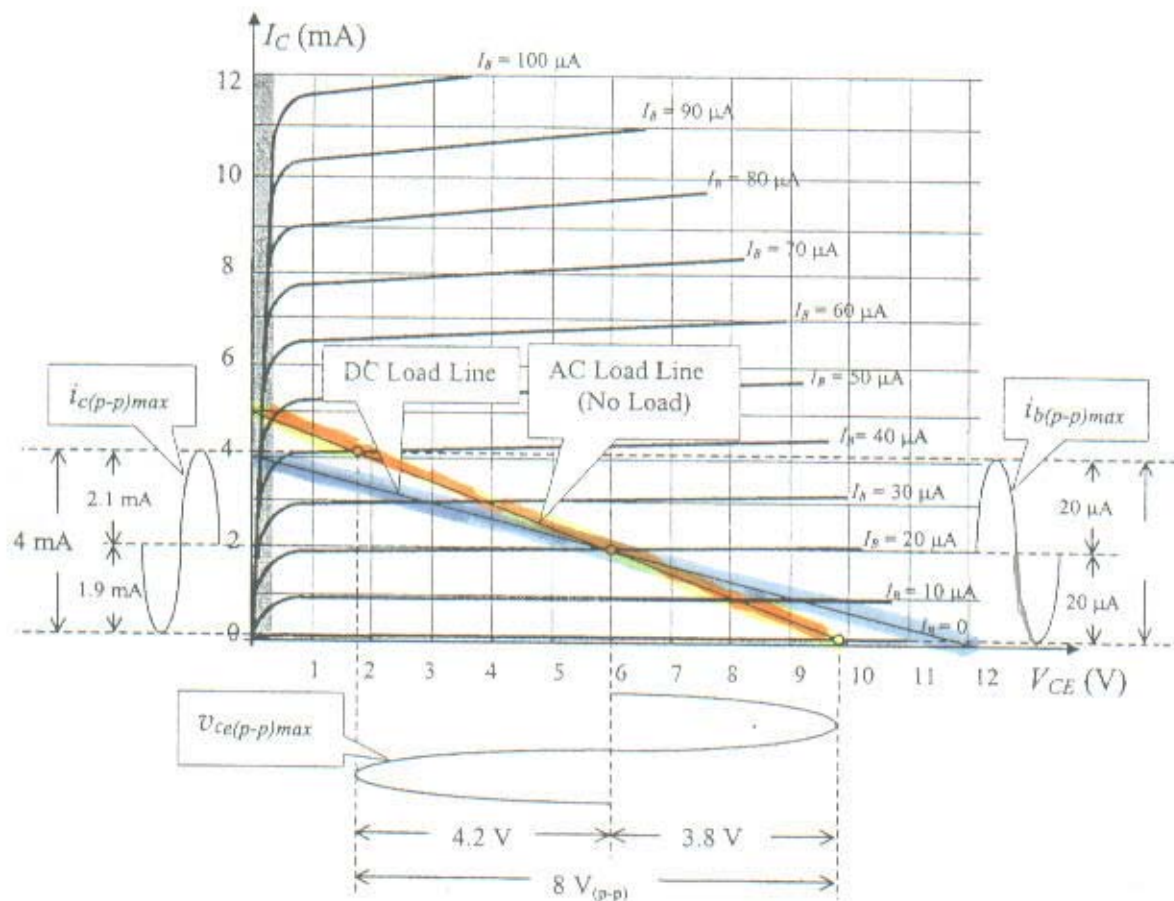


Figure 6-2: DC and AC load lines with the maximum input and output signals for the CE amplifier of Figure 6-1, with no load

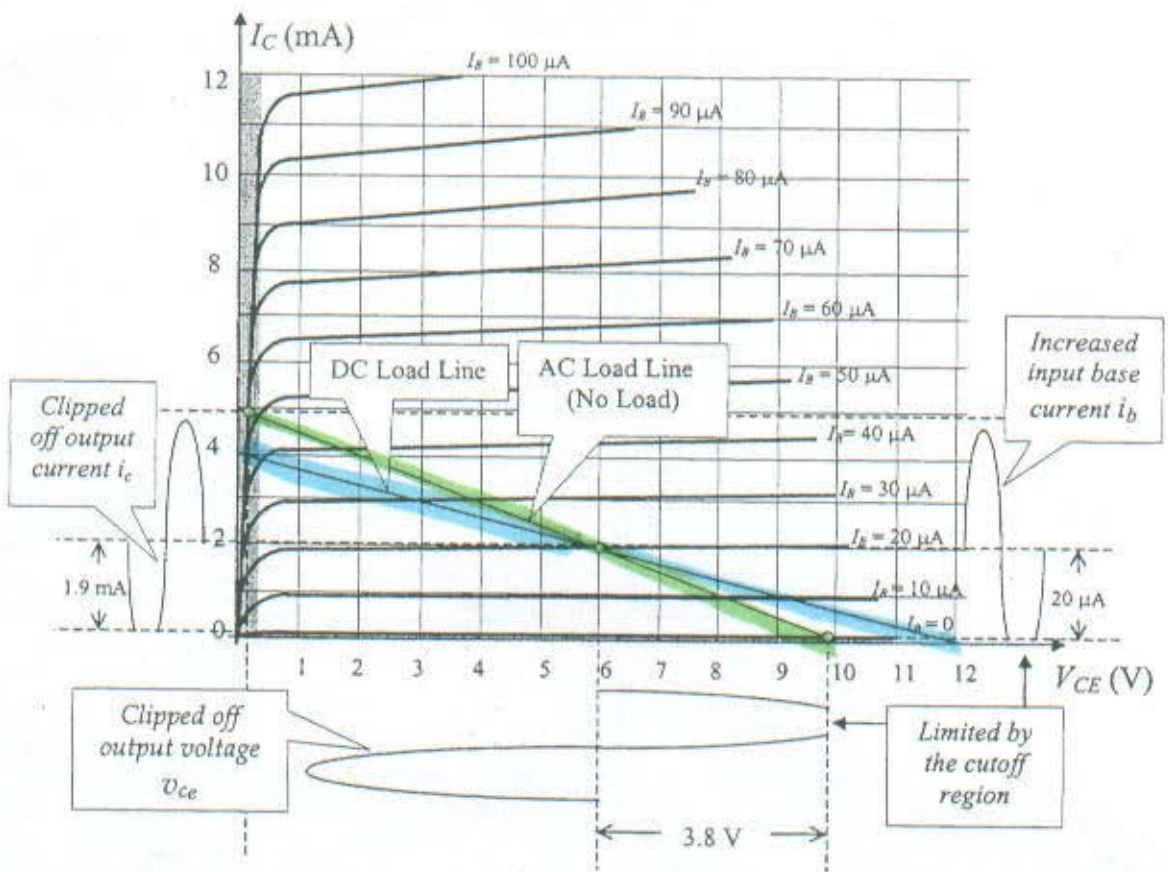

**Figure 6-3:** Output current and voltage signals with increased input signal  $i_b$  for the CE amplifier of Figure 6-1, without load

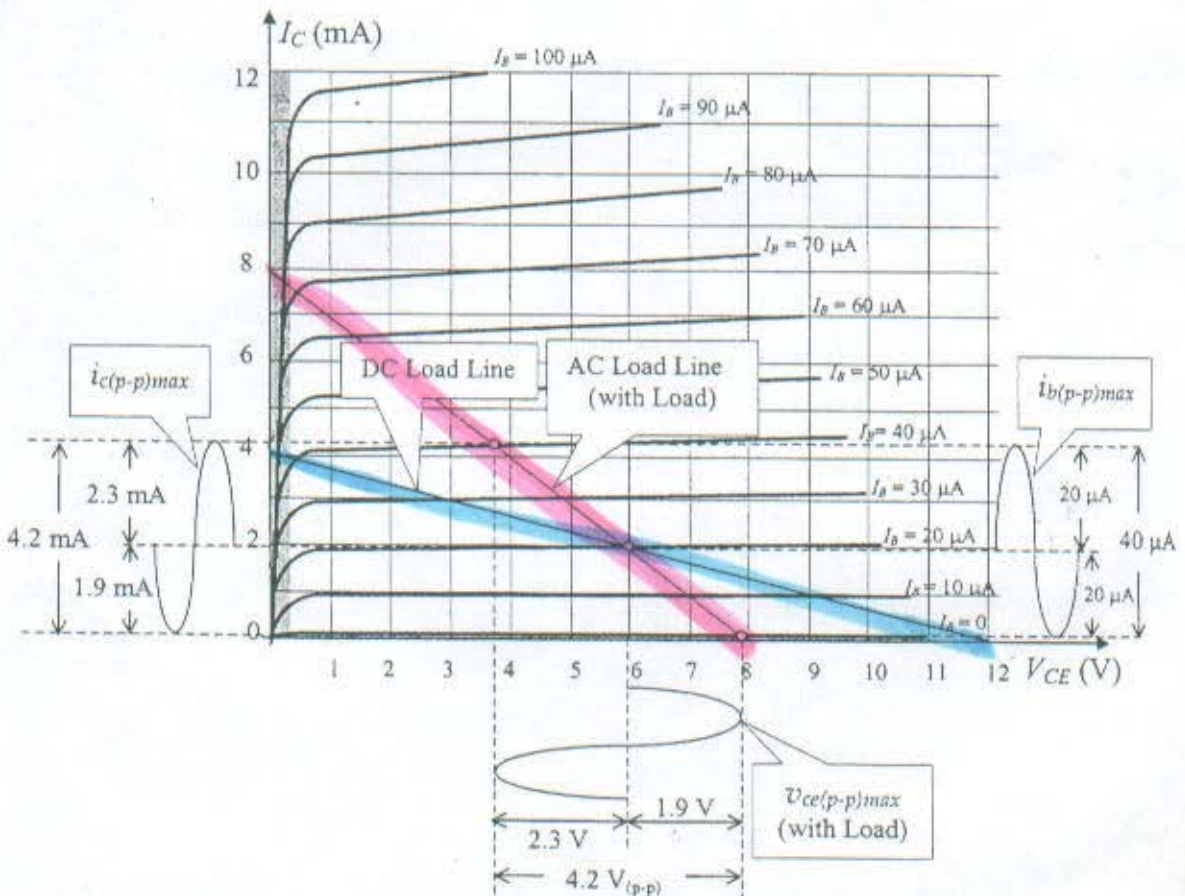

**Figure 6-8:** Maximum output current and voltage signals for the CE amplifier of Figure 6-1, with load