

## Bipolar Junction Transistors (BJT)

### PNP & NPN (Emitter Base Collector)

Note: NPN's are more commonly encountered due to greater ease of production.  
 Bipolar (majority and minority carriers)  
 Forward voltage characteristics of PN junction (approximately 0.2 volts for Ge and 0.7 volts for Si).

Biassing:

$$\text{NPN } V_c > V_e \quad V_{be} = +0.7 \qquad \text{PNP } V_e > V_c \quad V_{be} = -0.7$$

BJTs are current-controlled devices: Symbology and Voltage / Current Relationships:

$V_{BB}$	Base Bias Voltage	$I_e = I_c + I_b$
$V_{EE}$	Emitter Bias Voltage	$I_c = \alpha I_e$
$V_{CC}$	Collector Bias Voltage	$I_c = \beta I_b$
$V_{be}$	Voltage drop across Emitter Base Junction	$I_e = (1 + \beta) I_b$
$V_{cb}$	Voltage drop across Collector Base Junction	$I_b = (1 - \alpha) I_e$
$V_{ce}$	Voltage drop from Collector to Emitter	$\beta = \alpha(1 - \alpha)$
		$\alpha = \beta(1 + \beta)$
		$\alpha \approx 1 \quad \beta = 20 - 2000 \quad (100 - 400)$

Three Regions of BJT operations and required biasing for each:

Active (Linear) { Amplification }	Base Emitter Forward, Collector Base Reverse
Cut-Off { Open Switch - No Current Flow }	Base Emitter Reverse, Collector Base Reverse
Saturation { Closed Switch - High Current Flow }	Base Emitter Forward, Collector Base Forward

Active Region Linear Amplification (High Fidelity - No Distortion)

Emitter/Base Forward Bias  
 Collector/Base Reverse Bias

Cut-Off Region

Both junctions reversed biased  
 Emitter/Base voltage insufficient to cause emitter current flow  
 Zero current (same as open switch)

Saturation Region

Both junctions forward biased  
 Heavy current conduction (same as closed switch)

Configurations and Characteristics:

Common Base

Unity Current Gain  
 High Voltage Gain  
 No phase shift

Common Emitter

180° Phase Shift  
 High Power Gain (Both High Current and High Voltage Gains)  
 Most frequently used configuration




Common Collector (Emitter Follower)

Unity Voltage Gain  
 No phase shift  
 High Input Impedance & Low Output Impedance


## BJT Amplifiers

	Voltage Gain ( $A_v$ )	Current Gain ( $A_i$ )	Power Gain ( $A_p = A_v A_i$ )	Input Impedance	Output Impedance	Phase Shift
Ideal	Infinite	Infinite	Infinite	Infinite	Zero	N/A
Common Emitter	100 - 1000	100 - 1000	> 1000	1 - 10K Ohm	1 - 10K Ohm	180°
Common Collector (Emitter Follower)	< 1	100 - 1000	< $A_i$	> 10K Ohm	< 1K Ohm	0°
Common Base	100 - 1000	< 1	< $A_v$	< 1K Ohm	> 10K Ohm	0°

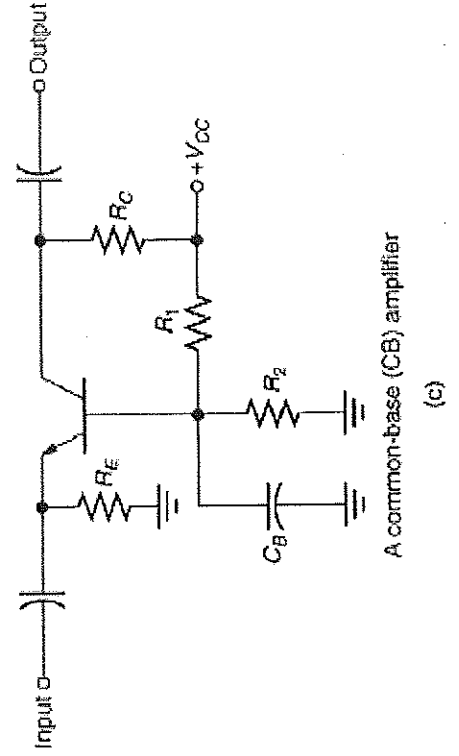 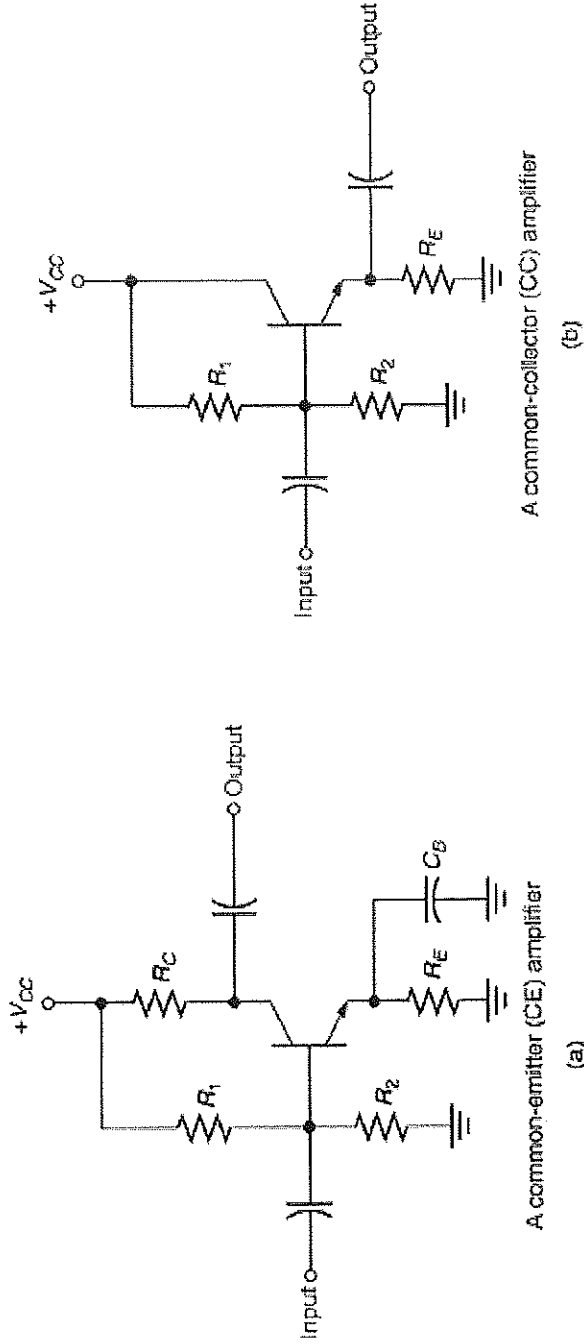
Ideal  
Common Emitter  
Common Collector (Emitter Follower)  
Common Base




## BJT Amplifier Configurations

 


**Common Base-Biased BJT Amplifier**

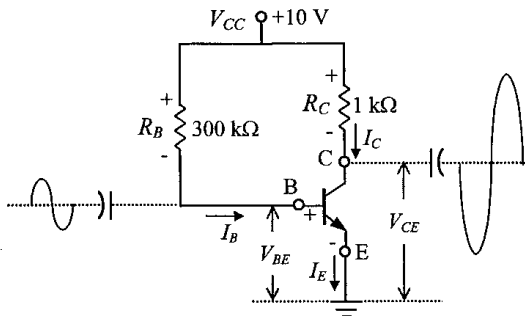

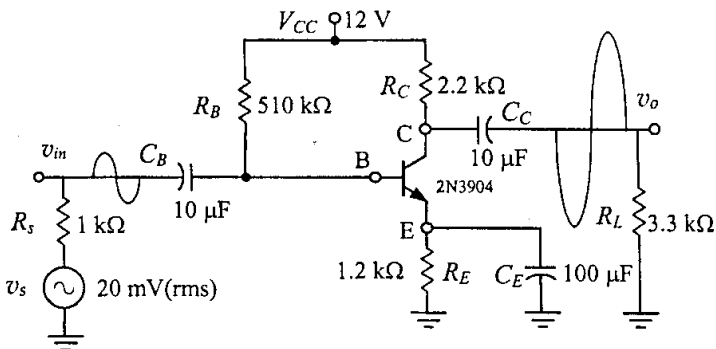**Base-Biased Common Emitter BJT Amplifier**




 **Emitter-Biased Common Emitter BJT Amplifier**




**Emitter-Biased Common Collector BJT Amplifier**

# Transistor Switch

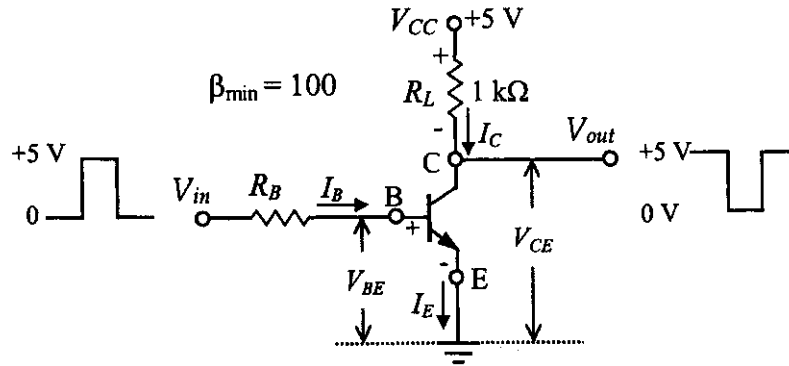

The BJT Inverter

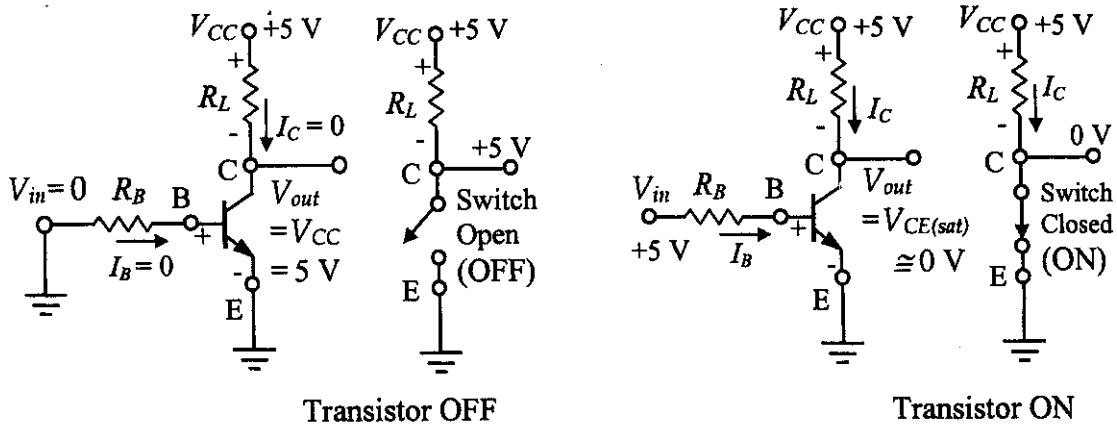

## Field Effect Transistors (FET)

FET (JFET & MOSFET)

P-type & N-type (Source, Drain, Gate)

Unipolar (majority carriers only)

JFETs are voltage-controlled devices:  $v_o = av_i$

Forward Bias with respect Source & Drain

P Channel: Source + and Drain - (conventional current flow Source to Drain  $I_D$ )

N Channel: Source - and Drain + (conventional current flow Drain to Source  $I_D$ )

Reverse Bias with respect to Source & Gate (Max current flow  $I_D$  when  $V_{gs} = 0$ )

P Channel: Gate more positive than Source causes a decrease in  $I_D$  current flow

N Channel: Gate more negative than Source causes a decrease in  $I_D$  current flow

Terminology:

$V_P$  (Pinch-Off Voltage)

The  $V_{DS}$  voltage at which the current  $I_D$  levels off ( $V_{GS} = 0$ )

$I_{DSS}$  (Drain-Source Saturation Current)

Maximum current flow with  $V_{DS} > V_P$  and  $V_{GS} = 0$ .

$V_{GS(off)}$  (Gate-to-Source Cutoff Voltage) Note:  $V_P = |V_{GS(off)}|$

The value of  $V_{GS}$  which results in total channel depletion, and hence zero current flow ( $I_D = 0$ ).

Quiescent (Operating Points)

$I_{DQ}$

$V_{DSQ}$

Equations:

Self Biased

$$I_D = \frac{-V_{GS}}{R_S}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$


Voltage Divider

$$I_D = \frac{V_G - V_{GS}}{R_S}$$


$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

## Field Effect Transistors (FETS)


N-CHANNEL JFET

 


N-CHAN CURVES

 

P-CHANNEL JFET

 

P-CHAN CURVES

 

**DRAIN CURRENT  
(OHMIC REGION)**

$$I_D = I_{DSS} \left[ 2 \left( 1 - \frac{V_{GS}}{V_{GS,off}} \right) \frac{V_{DS}}{-V_{GS,off}} - \left( \frac{V_{DS}}{V_{GS,off}} \right)^2 \right]$$

**DRAIN CURRENT  
(ACTIVE REGION)**

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS,off}} \right)^2$$

**DRAIN-SOURCE  
RESISTANCE**

$$R_{DS} = \frac{V_{DS}}{i_D} = \frac{V_{GS,off}}{2I_{DSS}(V_{GS} - V_{GS,off})} = \frac{1}{g_m}$$

**ON RESISTANCE**

$$R_{DS,on} = \text{constant}$$

**DRAIN-SOURCE  
VOLTAGE**

$$V_{DS} = V_D - V_S$$

**TRANSCONDUCTANCE**

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS}} = \frac{1}{R_{DS}}$$

$$= g_{m0} \left( 1 - \frac{V_{GS}}{V_{GS,off}} \right) = g_{m0} \sqrt{\frac{I_D}{I_{DSS}}}$$

**TRANSCONDUCTANCE  
FOR SHORTED GATE**

$$g_{m0} = \frac{2I_{DSS}}{V_{GS,off}}$$

Typical JFET values:

$I_{DSS}$ : 1 mA to 1 A

$V_{GS,off}$ :

-0.5 to -10 V (n-channel)

0.5 to 10 V (p-channel)

$R_{DS,on}$ : 10 to 1000  $\Omega$

$BV_{DS}$ : 6 to 50 V

$g_m$  at 1 mA:

500 to 3000  $\mu\text{mho}$

**OHMIC REGION** JFET is just beginning to resist. It acts like a variable resistor.




**SATURATION REGION** JFET is most strongly influenced by gate-source voltage, hardly at all influenced by the drain-source voltage.

**CUTOFF VOLTAGE ( $V_{GS,off}$ )** Particular gate-source voltage where JFET acts like an open circuit (channel resistance is at its maximum).

**BREAKDOWN VOLTAGE ( $BV_{DS}$ )** The voltage across the drain and source that caused current to "break through" the JFET's resistive channel.

**DRAIN-CURRENT FOR ZERO BIAS ( $I_{DSS}$ )** Represents the drain current when gate-source voltage is zero volts (or gate is connected to source,  $V_{GS} = 0$  V).

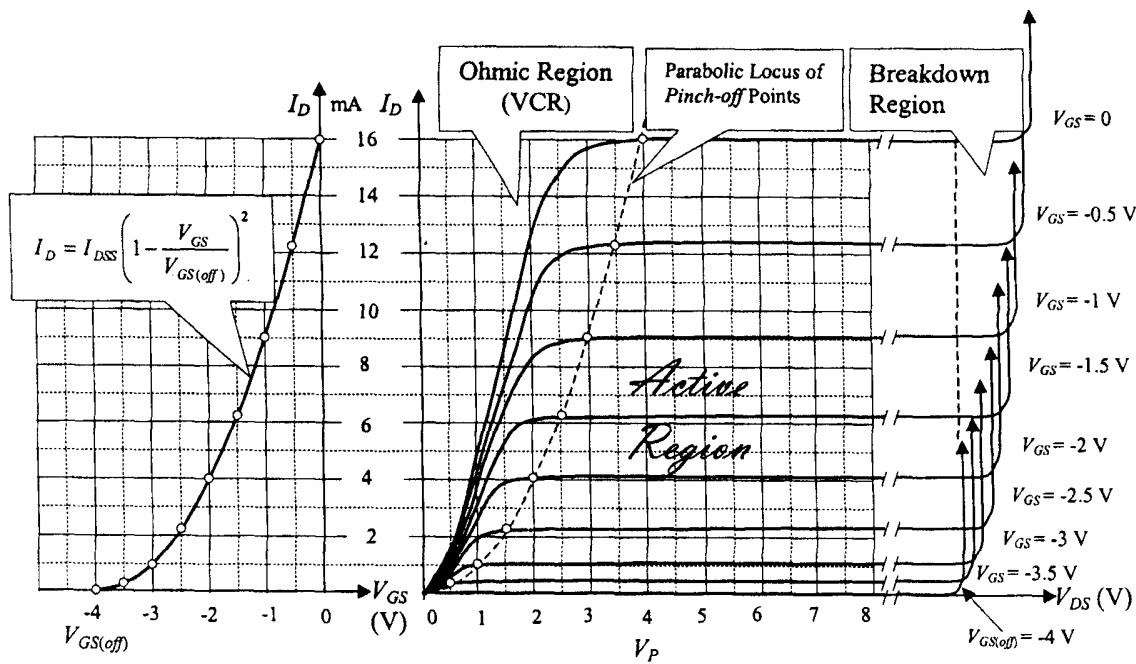  **TRANSCONDUCTANCE ( $g_m$ )** Represents the rate of change in the drain current with the gate-source voltage when the drain-to-source voltage is fixed for a particular  $V_{DS}$ . It is analogous to the transconductance ( $1/R_t$ ) for bipolar transistors.



(b) Transfer Characteristics

(a) Drain Characteristics

**Figure 7-8:** Plot of Drain and Transfer Characteristics for an  $n$ -channel JFET

Figures 7-6,7, 8. Kazimierzuk Electronic Devices

Source: Electronic Devices a design approach. Ali Aminian and Marian Kazimierzuk, 2004


## Junction Field Effect Transistors JFET

Three Terminals: Drain, Source, Gate

Majority Carriers Only (Unipolar)

N Channel Electrons

 By convention, always draw with **Drain** at the top



N Type Channel Arrow Pointing **IN**

Forward Bias Source to Drain  $V_{DD}$

For N Channel

+ to Drain

- to Source

Conventional Current Flow  $I_D$  (From Drain to Source)

Reverse Bias Gate to Source  $I_G = 0$

- to Gate

+ to Source

$V_G$  is the Gate to Ground Voltage

$V_{GS}$  is the Gate to Source Voltage

$V_P$  (Pinch-Off Voltage) The  $V_{DS}$  voltage at which the current  $I_D$  levels off (for  $V_{GS} = 0$ )

$V_{GS(off)}$  (Gate-to-Source Cutoff Voltage  $I_D = 0$ )  $V_P = |V_{GS(off)}|$

$I_{DSS}$  (Drain-Source Saturation Current) Maximum current flow with  $V_{GS} = 0$ .

Quiescent (Operating Points)

$I_{DQ}$

$V_{DSQ}$

Shockley's Equation

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

Notes:

$V_{GS}$  and  $V_{GS(off)}$  are always the same algebraic sign, so  $V_{GS} / V_{GS(off)}$  will always be positive.

For N Channel,  $V_{GS(off)}$  is negative,  $V_P = |V_{GS(off)}|$ , so  $I_D = I_{DSS} \left( 1 + \frac{V_{GS}}{V_P} \right)^2$

Biasing N Channel JFETs i.e., calculating Quiescent (Operating Points),  $I_{DQ}$  and  $V_{DSQ}$

$I_{DSS}$  and  $V_{GS(off)}$  are from readily obtainable from Transfer Characteristics Charts

For Fixed Biased,  $V_{GS} = V_{GG}$  (since reversed bias,  $I_G = 0$ ,  $V_{RG} = 0$ ,  $V_{GS} = V_{GG}$ )

For Self Biased and Voltage Divider Biased,  $V_{GS}$  is the solution of a quadratic equation.


For BME 3512,  $I_{DSS}$ ,  $V_{GS(off)}$ ,  $V_{GS}$  will be given.



**Examples Biasing N Channel JFETs** Determine Quiescent (Operating Points),  $I_{DQ}$  and  $V_{DSQ}$

 **Fixed Biased**

$$I_{DSS} = 12 \text{ mA} \quad V_{GS(off)} = -4 \text{ V}$$



**A fixed bias circuit**

Given:  $I_{DSS} = 12 \text{ mA}$      $V_{GS(off)} = -4 \text{ V}$

Since Gate to Source is reverse biased,  $I_G = 0$ , hence  $V_{R_g} = I_G R_g = 0$

And     $V_{GG} = I_G R_g + V_{GS}$

$$V_{GG} = 0 + V_{GS}$$

$$V_{GS} = V_{GG} = -1 \text{ V}$$

From Shockley's Equation


$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = 12 \times 10^{-3} \times \left( 1 - \frac{-1}{-4} \right)^2 = 6.75 \text{ mA}$$

$$V_{DD} = V_{DS} + I_D R_D \quad \rightarrow \quad V_{DS} = V_{DD} - I_D R_D = 12 - 6.75 \times 10^{-3} (1 \times 10^{-3}) = 5.25 \text{ V}$$

Answers:  $I_{DQ} = 6.8 \text{ mA}$     and     $V_{DSQ} = 5.3 \text{ V}$

 **Self-Biased**

$$I_{DSS} = 16 \text{ mA} \quad V_{GS(off)} = -4 \text{ V}$$



A self-biased circuit

Given:  $I_{DSS} = 16 \text{ mA}$        $V_{GS(off)} = -4 \text{ V}$        $V_{GS} = \text{see below}$

The  $I_D$  current through  $R_S$  will develop a voltage across  $R_S$  such that the Source is at a positive potential with respect to Ground. If any current  $I_G$  flows at all, the Gate will be at a negative potential with respect to Ground and hence the Gate to Source will be reversed bias resulting in  $I_G = 0$ , hence  $V_{Rg} = I_G R_g = 0$ , and therefore  $V_G$  (Gate to Ground) = 0.

But  $V_G = V_{GS} + I_D R_S$

$$0 = V_{GS} + I_D R_S$$

$$I_D = -V_{GS} / R_S$$

$$\text{From } I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 \text{ and } I_D = -V_{GS} / R_S \rightarrow \frac{-V_{GS}}{R_S} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

Solve for  $V_{GS}$  (see page 5 Summary of FET Biasing Equations) Note:


For BME 3512 the value of  $V_{GS}$  will be given.  $V_{GS} = -2.44 \text{ V}$

$$I_D = -V_{GS} / R_S = -(-2.44) / 1 \times 10^3 = 2.44 \text{ mA}$$

$$V_{DD} = V_{DS} + I_D (R_D + R_S) \rightarrow V_{DS} = V_{DD} - I_D (R_D + R_S) = 15 - 2.44 \times 10^{-3} (1500 + 1000) = 8.9 \text{ V}$$

Answers:  $I_{DQ} = 2.4 \text{ mA}$  and  $V_{DSQ} = 8.9 \text{ V}$

**Voltage Divider Biased**

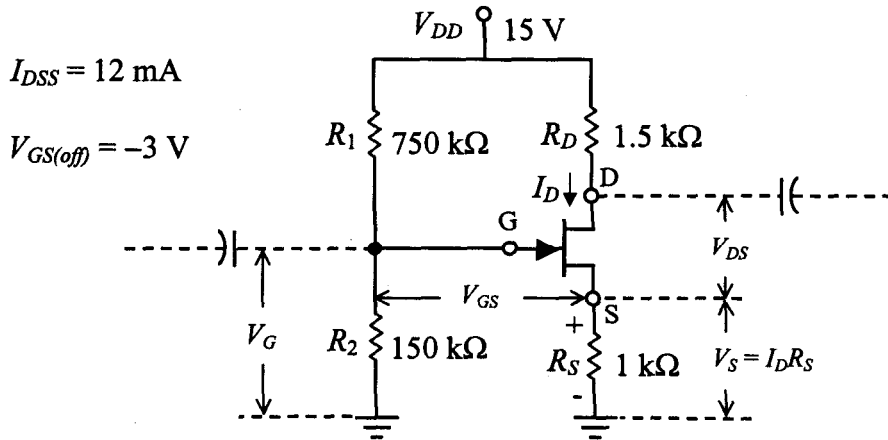

A voltage-divider biased JFET amplifier circuit

Given:  $I_{DSS} = 12 \text{ mA}$        $V_{GS(off)} = -3 \text{ V}$        $V_{GS} = \text{see below}$

From the voltage divider network:  $V_G = V_{DD} \frac{R_2}{R_1 + R_2}$

By definition:  $V_{GS} = V_G - V_S = V_G - I_D R_S$

Hence  $I_D = (V_G - V_{GS}) / R_S$

From  $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2$  and  $I_D = (V_G - V_{GS}) / R_S \rightarrow \frac{V_G - V_{GS}}{R_S} = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2$

Solve for  $V_{GS}$  (see page 5 Summary of FET Biasing Equations)

Note: For BME 3512 the value of  $V_{GS}$  will be given.  $V_{GS} = -1.31 \text{ V}$

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2} = 15 \frac{150 \text{ K}}{750 \text{ K} + 150 \text{ K}} = 2.50 \text{ V}$$

$$I_D = (V_G - V_{GS}) / R_S = [2.5 - (-1.31)] / 1000 = 3.81 \text{ mA}$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S) = 15 - 3.81 \times 10^{-3} (1500 + 1000) = 5.48 \text{ V}$$

Answers:  $I_{DQ} = 3.8 \text{ mA}$  and  $V_{DSQ} = 5.5 \text{ V}$

## Summary of Equations for the Analysis of Self-Biased and Voltage-Divider Biased JFET Amplifier

**Self-bias:**

$$V_{GS} \Big|_{n\text{-channel}} = \frac{-b + \sqrt{b^2 - 4ac}}{2a}$$

$$V_{GS} \Big|_{p\text{-channel}} = \frac{+b - \sqrt{b^2 - 4ac}}{2a}$$

where,

$$a = \frac{I_{DSS} R_S}{V_P^2} \qquad b = \frac{2I_{DSS} R_S}{|V_P|} + 1 \qquad c = I_{DSS} R_S$$

$$I_D = \frac{-V_{GS}}{R_S}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

**Voltage-divider bias:**

$$V_{GS} \Big|_{n\text{-channel}} = \frac{-b + \sqrt{b^2 - 4ac}}{2a}$$

$$V_{GS} \Big|_{p\text{-channel}} = \frac{+b - \sqrt{b^2 - 4ac}}{2a}$$

where,

$$a = \frac{I_{DSS} R_S}{V_P^2} \qquad b = \frac{2I_{DSS} R_S}{|V_P|} + 1 \qquad c = I_{DSS} R_S - |V_G|$$

$$I_D = \frac{V_G - V_{GS}}{R_S}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$