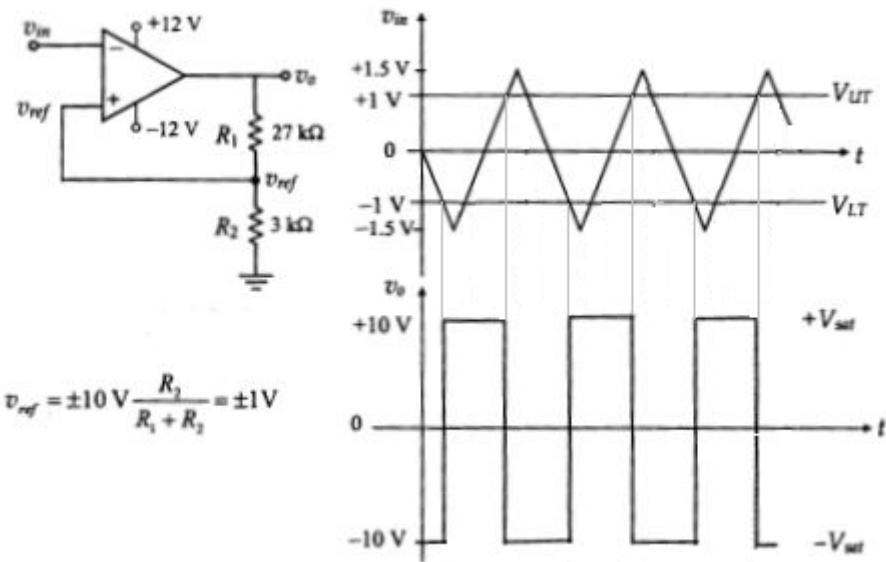


Schmitt Trigger Bi-Referenced Comparators

Schmitt Trigger (Assume at power on, Vout is negative).



Positive Feedback

$$V_{out} = V_{sat} = V_{cc} \pm 2 \text{ Volts} = \pm 10 \text{ Volts}$$

From Voltage Divider

$$V_{ref} = V_{out} (R_2 / (R_1 + R_2)) = 10(3000 / (27000 + 3000)) = 1 \text{ Volt}$$

If $V_{out} = +10 \text{ V}$ then $V_{ref} = +1 \text{ V}$

If $V_{out} = -10 \text{ V}$ then $V_{ref} = -1 \text{ V}$

If $V^- > V^+$ then $V_{out} = -V_{sat}$

If $V^- < V^+$ then $V_{out} = +V_{sat}$

$$V^- = V_{in} \text{ and } V^+ = V_{ref}$$

So if $V_{in} > V_{ref}$ then $V_{out} = -10 \text{ V}$

And if $V_{in} < V_{ref}$ then $V_{out} = +10 \text{ V}$

At start up, when power is first applied to the circuit, suppose $V_{out} = -10 \text{ V}$, then $V_{ref} = -1 \text{ V}$.

If $V_{in} > V_{ref} (-1 \text{ V})$ then $V_{out} = -10 \text{ V}$ OKAY!

When $V_{in} < V_{ref} (-1 \text{ V})$ then V_{out} switches to $+10 \text{ V}$ and V_{ref} switches to $+1 \text{ V}$.


As long as $V_{in} < V_{ref}$ (i.e., $V_{in} < +1 \text{ V}$) then $V_{out} = +10 \text{ V}$.

When $V_{in} > V_{ref} (+1 \text{ V})$ then V_{out} switches to -10 V and V_{ref} switches to -1 V .

As long as $V_{in} > V_{ref}$ (i.e., $V_{in} > -1 \text{ V}$) then $V_{out} = -10 \text{ V}$.

And the cycle repeats!

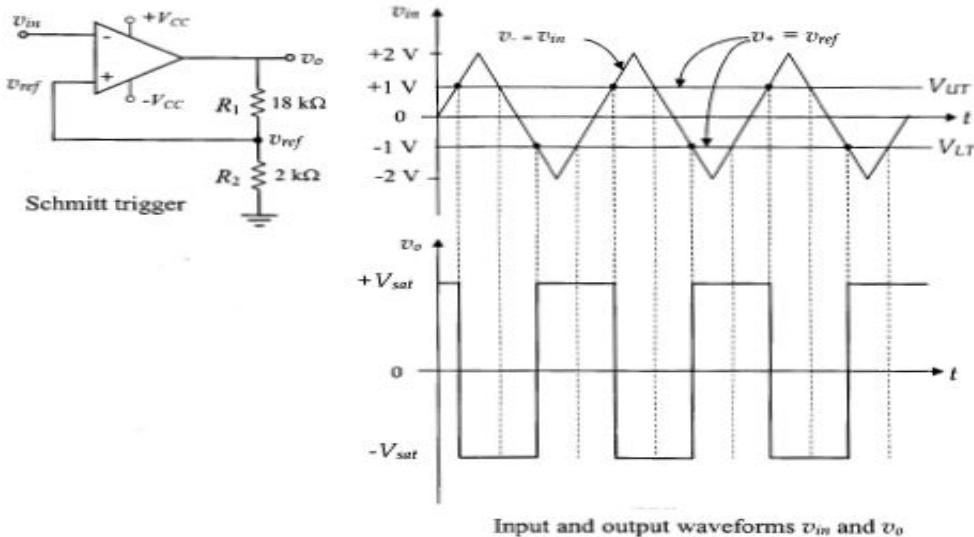Schmitt Trigger (Assume at power on, Vout is positive).



Input and output waveforms v_{in} and v_o

Applying the voltage-divider rule, the reference voltage v_{ref} at the non-inverting terminal is determined in terms of R_1 and R_2 , as follows:

$$v_{ref} = v_o \frac{R_2}{R_1 + R_2} \quad v_{ref} = \pm V_{sat} \frac{R_2}{R_1 + R_2} = v_+$$

Positive Feedback

$V_{out} = V_{sat} = V_{cc} \pm 2 \text{ Volts} = \pm 10 \text{ Volts}$

From Voltage Divider

$$V_{ref} = V_{out} (R_2 / (R_1 + R_2)) = 10(2000 / (18000 + 2000)) = 1 \text{ Volt}$$

If $V_{out} = +10 \text{ V}$ then $V_{ref} = +1 \text{ V}$

If $V_{out} = -10 \text{ V}$ then $V_{ref} = -1 \text{ V}$

If $V^- > V^+$ then $V_{out} = -V_{sat}$

If $V^- < V^+$ then $V_{out} = +V_{sat}$

$V^- = V_{in}$ and $V^+ = V_{ref}$

So if $V_{in} > V_{ref}$ then $V_{out} = -10 \text{ V}$

And if $V_{in} < V_{ref}$ then $V_{out} = +10 \text{ V}$

At start up, when power is first applied to the circuit, suppose $V_{out} = +10 \text{ V}$, then $V_{ref} = +1 \text{ V}$.

If $V_{in} < V_{ref} (+1 \text{ V})$ then $V_{out} = +10 \text{ V}$ OKAY!

When $V_{in} > V_{ref} (+1 \text{ V})$ then V_{out} switches to -10 V and V_{ref} switches to -1 V .

As long as $V_{in} > V_{ref}$ (i.e., $V_{in} > -1 \text{ V}$) then $V_{out} = -10 \text{ V}$.

When $V_{in} < V_{ref} (-1 \text{ V})$ then V_{out} switches to $+10 \text{ V}$ and V_{ref} switches to $+1 \text{ V}$.

As long as $V_{in} < V_{ref}$ (i.e., $V_{in} < +1 \text{ V}$) then $V_{out} = +10 \text{ V}$.

And the cycle repeats!