


## Op-Amp Homework Problems

Note: These op-amp review problems maybe configured slightly differently from the schematics we discussed in class; however, the methodology and solutions are the same.

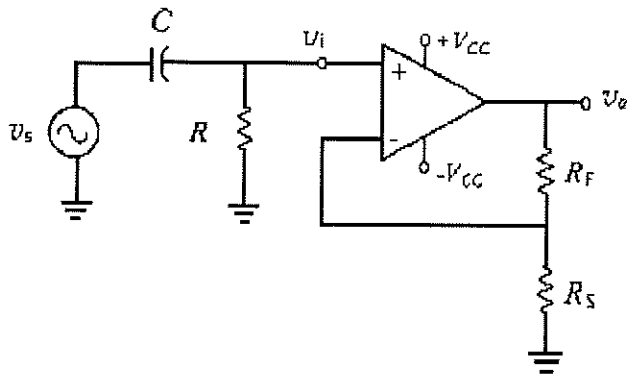1. Calculate pass band gain and the cut-off frequency for a 1st order high pass active filters.

Identify type of filter and calculate the cut-off frequency and pass band gain for

$$\begin{aligned} R &= 4.7 \text{ K}\Omega \\ C &= 0.01 \text{ }\mu\text{f} \\ R_F &= 91 \text{ K}\Omega \\ R_S &= 5.1 \text{ K}\Omega \end{aligned}$$




Answers:

High Pass Filter  
Cut-Off Freq = 3.38 KHz  
Pass Band Gain = 22.5 dB

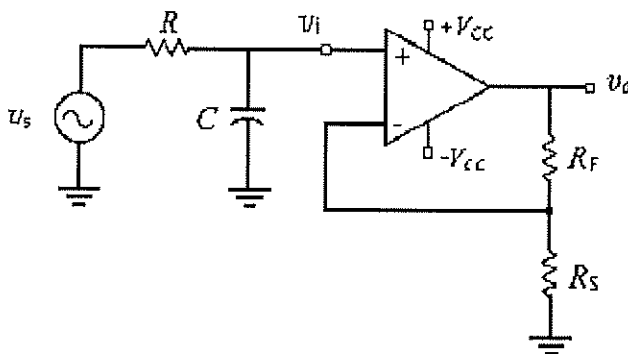2. Calculate pass band gain and the cut-off frequency for a 1st order low pass active filters.

Identify type of filter and calculate the cut-off frequency and pass band gain for

$$\begin{aligned} R &= 5.1 \text{ K}\Omega \\ C &= 0.01 \text{ }\mu\text{f} \\ R_F &= 33 \text{ K}\Omega \\ R_S &= 4.7 \text{ K}\Omega \end{aligned}$$



Answers:

Low Pass Filter  
Cut-Off Freq = 3.12 KHz  
Pass Band Gain = 18 dB

## Op-Amp Homework Solutions

### Problems 1 & 2 Active Op-Amp Filters

The input is connected to  $V_+$  indicating a non-inverter configuration.

The negative feedback loop from  $V_{out}$  to  $V_-$  has a gain of  $(1 + R_f/R_s)$  for non-inverting input.

The input represents a voltage divider  $V_s$ ,  $X_c$ ,  $R$ .

Cut-Off Frequency for both Low Pass and High Pass Filters:  $f_c = 1 / (2\pi RC)$

Pass Band Gain (in dB) =  $20\log(1 + R_f/R_s)$

1.  $V_i$  is the voltage across the resistor  $R$ , so

$$V_i = V_s (R / (R + X_c)) \text{ where } X_c = 1/j\omega C$$

$$V_i = V_s (R / (R + 1/j\omega C)) \text{ dividing by } R \text{ yields}$$

$$V_i = V_s (1 / (1 + 1/j\omega RC)) \text{ and}$$

$$V_{out} = (1 + R_f/R_s) * V_i = (1 + R_f/R_s) * V_s (1 / (1 + 1/j\omega RC))$$

$$V_{out}/V_s = (1 + R_f/R_s) * (1 / (1 + 1/j\omega RC))$$

Let  $A = (1 + R_f/R_s)$  and  $T = RC$  or  $V_{out}/V_s = A * (1 / (1 + 1/j\omega T))$   
which is the same as we deduced in class for a High-Pass Filter,  
although we multiplied by  $j\omega T$  and wrote it as:  $A * (j\omega T / (1 + j\omega T))$ .

Why high pass? If  $\omega=0$  then  $V_{out}/V_s = 0$ .

If  $\omega$  becomes very large, then  $V_{out}/V_s$  approaches  $A$ .

Hence, the circuit blocks low frequencies and passes high frequencies.

2.  $V_i$  is the voltage across the capacitor  $C$ , so

$$V_i = V_s (X_c / (R + X_c)) \text{ where } X_c = 1/j\omega C$$

$$V_i = V_s (1/j\omega C / (R + 1/j\omega C)) \text{ multiplying by } j\omega C \text{ yields}$$

$$V_i = V_s (1 / (j\omega RC + 1)) = V_s (1 / (1 + j\omega RC)) \text{ and}$$

$$V_{out} = (1 + R_f/R_s) * V_s (1 / (1 + j\omega RC))$$

$$V_{out}/V_s = (1 + R_f/R_s) / (1 + j\omega RC)$$

Let  $A = (1 + R_f/R_s)$  and  $T = RC$  or  $V_{out}/V_s = A / (1 + j\omega T)$   
which is the same as we deduced in class for a Low-Pass Filter.

Why low pass? If  $\omega=0$  then  $V_{out}/V_s = A / (1 + 0) = A$ .

If  $\omega$  becomes very large, then  $V_{out}/V_s$  becomes very small.

Hence, the circuit passes low frequencies and blocks high frequencies.