

## Understanding the Behavior of Complex Impedances

Understanding the Behavior of Complex Impedances at very low frequency (i.e.,  $f \approx 0$ ) and at very high frequency (i.e.,  $f \gg 0$  or  $f \approx \infty$ ).

For Inductive Reactance,  $X_L = \omega L$

If  $\omega = 0$ , then  $X_L = \omega L = 0$

If  $\omega \gg 0$ , then  $X_L = \omega L \gg 0 \approx \infty$

For Capacitive Reactance,  $X_C = 1 / \omega C$

If  $\omega = 0$ , then  $X_C = 1 / \omega C \gg 0 \approx \infty$

If  $\omega \gg 0$ , then  $X_C = 1 / \omega C \approx 0$

$R = R$  regardless of  $\omega$ .


From Ohm's Law for Alternating Current, Impedance  $Z = v(t) / i(t)$

$Z = R + j(X)$  where  $X$  is the reactant component due to circuit capacitors and inductors at a given frequency.


If  $Z = 0$ , then **Short**, i.e., like a wire conductor, very high current ( $I = V/Z$ ).

If  $Z \gg 0$  ( $Z \approx \infty$ ), then **Open**, i.e., like an open switch, no current.

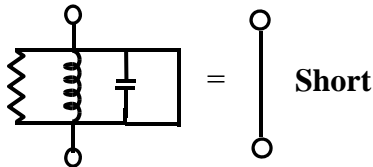
A **Short** in parallel with any other number of elements appears as a Short overall; i.e., just a wire conductor.



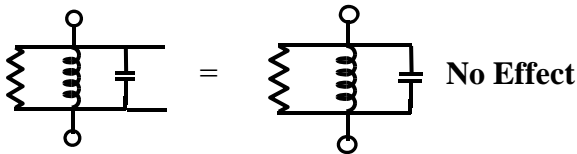An **Open** in parallel with another element can be considered to be no existent, i.e., no effect.



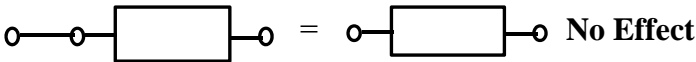A **Short** in series with another element can be considered to be just a wire conductor.



An **Open** in series with another number of elements appears as an Open Switch.



## Understanding the Behavior of Complex Impedances - continued

If  $\omega = 0$ , then  $X_L = \omega L = 0$  and  $X_C = 1 / \omega C \gg 0$ .

If  $\omega \gg 0$ , then  $X_L = \omega L \gg 0$  and  $X_C = 1 / \omega C = 0$ .

$R = R$  regardless of  $\omega$ .


If  $Z = 0$ , then Short, i.e., like a wire conductor, very high current ( $I = V/R$ ).

If  $Z \gg 0$  ( $Z \approx \infty$ ), then Open, i.e., like an open switch, no current.

For series:  $Z + 0 = Z$  and  $Z + \infty = \infty$  (Open)

For parallel,  $Z \parallel 0 = \frac{Z(0)}{Z+0} = 0$  (Short) and  $Z \parallel \infty = \frac{Z(\infty)}{Z+\infty} = \frac{Z(\infty)}{\infty} = Z$
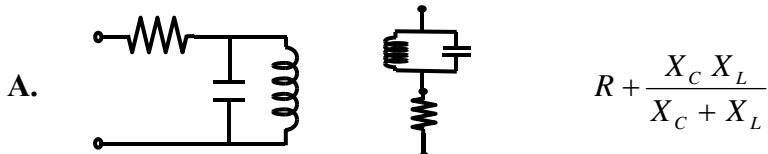
### From Complex Impedance Quiz & BME/ISE 3511 Fall 2015 Test Four




$$R + \frac{X_C X_L}{X_C + X_L}$$

if  $\omega = 0$ , then  $R + \frac{X_C X_L}{X_C + X_L} \approx R + 0 = R$  (Note:  $X_L = 0$ )

**Overall Effect = Resistive**

if  $\omega \gg 0$ , then  $R + \frac{X_C X_L}{X_C + X_L} \approx R + 0 = R$  (Note:  $X_C = 0$ )

**Overall Effect = Resistive**

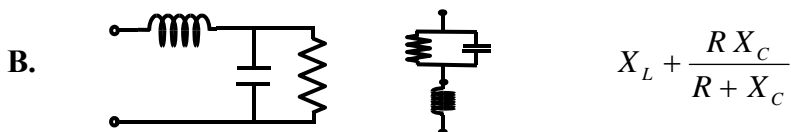


$$X_L + \frac{R X_C}{R + X_C}$$

if  $\omega = 0$ , then  $X_L + \frac{R X_C}{R + X_C} \approx 0 + \frac{R X_C}{R + X_C} \approx 0 + \frac{R X_C}{X_C} = 0 + R = R$  (Note:  $X_L = 0$  and  $X_C \gg 0$ )

**Overall Effect = Resistive**

if  $\omega \gg 0$ , then  $X_L + \frac{R X_C}{R + X_C} = \infty + 0 = \infty$  Open (Note:  $X_L = \infty$  and  $X_C = 0$ )

**Overall Effect = Open**

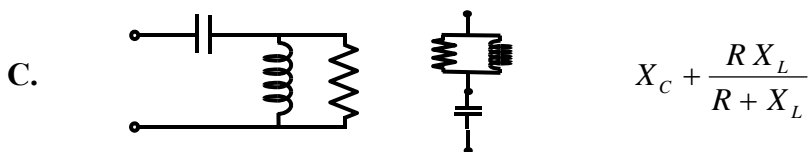

$$X_C + \frac{R X_L}{R + X_L}$$

if  $\omega = 0$ , then  $X_C + \frac{R X_L}{R + X_L} \approx \infty + \frac{R(0)}{R+0} \approx \infty + 0 = \infty$  Open (Note:  $X_C \gg 0$  and  $X_L = 0$ )

**Overall Effect = Open**

if  $\omega \gg 0$ , then  $X_C + \frac{R X_L}{R + X_L} \approx 0 + \frac{R X_L}{R + X_L} \approx 0 + \frac{R X_L}{X_L} = 0 + R = R$  (Note:  $X_C = 0$  and  $X_L \gg 0$ )

**Overall Effect = Resistive**