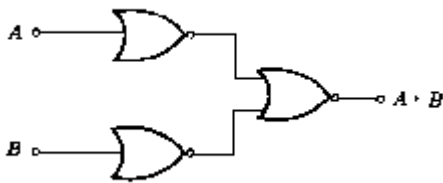


- Convert binary 10110110 to decimal equivalent.
- Convert decimal 249 to binary equivalent.
- Add binary 01100111  
00100110  
Check your work by converting to decimal equivalents.
- Construct the True Tables for AND OR XOR EQV NAND NOR.
- Prove DeMorgan's Theorem using truth tables.
- Use Truth Tables to show that  $\overline{A \text{ XOR } B} = A \text{ EQV } B$ .
- Use Boolean equations to show that three NOR gates produce a single AND gate.



- Design AND OR XOR EQV gates using only NAND gates (simple inverters are okay as needed).
- Suppose P is True and Q is False (Use P = 1 and Q = 0, if you wish).

Find

$$P \text{ AND } Q$$

$$P \text{ AND } \overline{Q}$$

$$\overline{P} \text{ OR } \overline{Q}$$

$$\overline{P} \text{ XOR } Q$$

$$\overline{P} \text{ EQV } Q$$