

BME 3511 Laboratory 3 Resistors in Series

Student Name: _____ Date Submitted: _____

Lab Partner(s): _____

Lab Procedure: Set up the follow circuits in series. Measure the resistances individually as well as the total resistance. Assume voltage source of 5 Volts. Calculate equivalent resistance, current, and voltage across each resistor. *Measure* and *record* the voltages as indicated.

Resistors	Measured Resistance	Calculated Current	Calculated Voltage	Measured Voltage
R1 = 1.2 kΩ R2 = 1.2 kΩ	R1 = R2 = RTotal =	I _{R1} = I _{R2} =	V _{R1} = V _{R2} = Total =	V _{R1} = V _{R2} = Total =
R1 = 1.2 kΩ R2 = 560 Ω	R1 = R2 = RTotal =	I _{R1} = I _{R2} =	V _{R1} = V _{R2} = Total =	V _{R1} = V _{R2} = Total =
R1 = 680 Ω R2 = 360 Ω R3 = 1.2 kΩ	R1 = R2 = R3 = RTotal =	I _{R1} = I _{R2} = I _{R3} =	V _{R1} = V _{R2} = V _{R3} = Total =	V _{R1} = V _{R2} = V _{R3} = Total =
R1 = 220 Ω R2 = 470 Ω R3 = 1.2 kΩ	R1 = R2 = R3 = RTotal =	I _{R1} = I _{R2} = I _{R3} =	V _{R1} = V _{R2} = V _{R3} = Total =	V _{R1} = V _{R2} = V _{R3} = Total =
R1 = 680 Ω R2 = 15 kΩ R3 = 560 Ω	R1 = R2 = R3 = RTotal =	I _{R1} = I _{R2} = I _{R3} =	V _{R1} = V _{R2} = V _{R3} = Total =	V _{R1} = V _{R2} = V _{R3} = Total =