

BME 3511 Laboratory 5 Combination Series & Parallel Circuits

Objective:

The objective of this exercise is to use the understanding of how to connect resistors in series and parallel while using the NI myDAQ to measure resistance and voltage. Upon the completion of this lab, the student will:

- Connect resistors in series and parallel in the same circuit.
- Measure individual resistance as well as equivalent resistance.
- Measure voltage across a combination circuit.

Background:

When resistors are connected in series, then they have the following properties:

- The current at all points of the circuit is equivalent since there is only one path for the current to travel.
- The equivalent resistance of a series circuit is obtained by adding all the resistances. Here is a generic formula for the equivalent resistance across a circuit:

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

- The voltage in a series circuit varies across each resistive component and can be calculated using ohms law:

$$\text{Total Voltage: } V=I \cdot R_{eq}$$

$$\text{Voltage across resistor } n: V=I \cdot R_n$$

When resistors are connected in parallel, then they have the following properties:

- The voltage at all points of the circuit is equivalent since the potential difference between any two points in the circuit is the same.
- The equivalent resistance of a parallel circuit is obtained by following formula:


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots \dots$$

Now we will do an example of how to measure these values using the NI myDAQ. The first step is to open the DMM on the computer and assemble your myDAQ components.


Lab Procedure:

- 1) Set up the first circuit using your bread board and the appropriate resistors as shown. The NI myDAQ will be used as a 5V power source in this lab.

Circuit 1

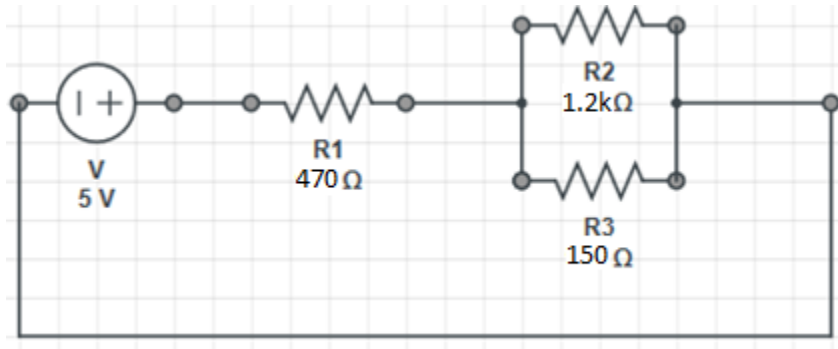

Circuit 2

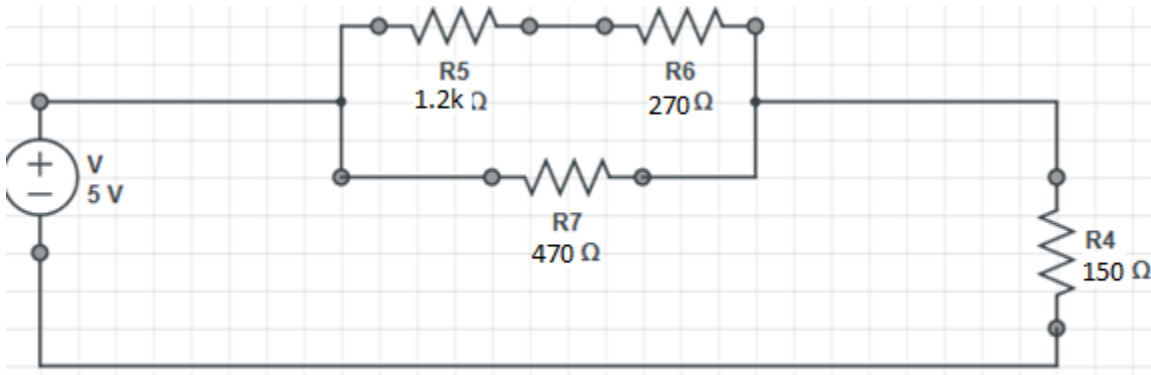

NOTE: Be sure to have a TA check your circuit before continuing.

- 2) Measure the individual resistance of all of the resistors as well as the equivalent resistance. Then, using the measured values of the individual resistances calculate what the equivalent resistance should be.
- 3) Given the source of 5 volts calculate the total current through the circuit.

NOTE: Keep in mind that this may not be the current through each individual resistor.

- 4) Measure the voltage across each resistor as well as the total voltage in the circuit.
- 5) Calculate the current that would pass through each resistor.

HINT: Remember Kirchoff's Node Law.


BME 3511 Laboratory 5 Combination Series & Parallel Circuits

Student Name: _____


Date Submitted: _____

Lab Partner(s): _____

Data Collection:

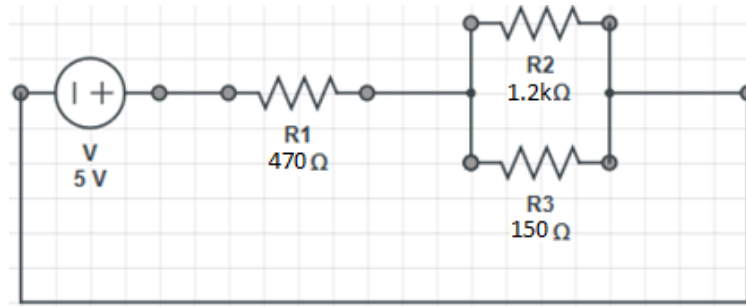

Circuit 1					
R₁		Total Current (I)		V_s	
R₂		I₁		V_{total}	
R₃		I₂		V₁	
R_{eq}(calculated)		I₃		V₂	
				V₃	

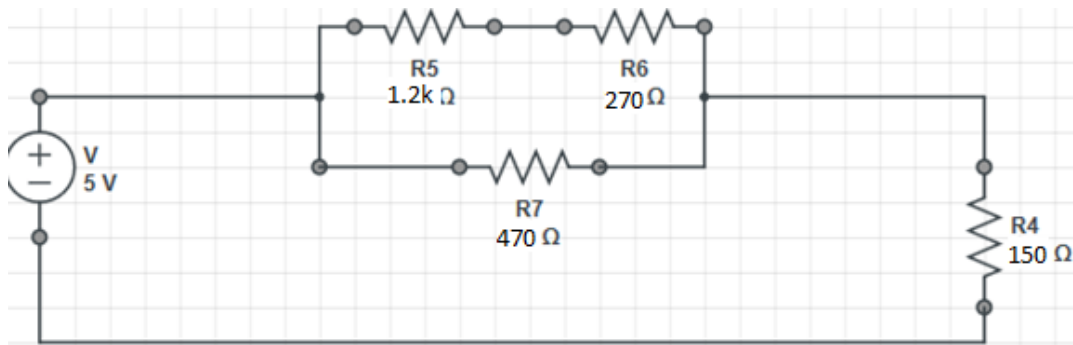

Circuit 2					
R₄		Total Current (I)		V_s	
R₅		I₄		V_{total}	
R₆		I₅		V₄	
R₇		I₆		V₅	
R_{eq}(calculated)		I₇		V₆	
				V₇	