

Digital Logic Gates Practice Problems

Develop Truth Tables for each of the diagrams (Figures A, B, C, D).
 Use True Tables to simplify the logic gate implementation where possible (See Figure A).

