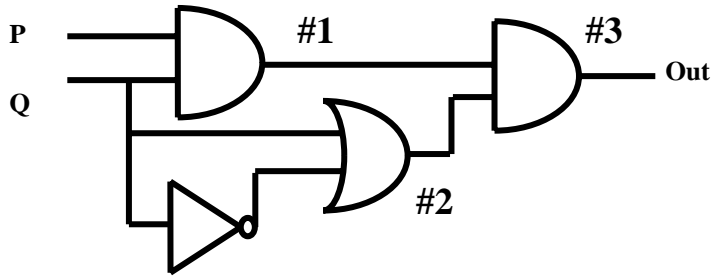


Answers (Truth Tables) to Logic Diagram Review Problems


Figure B.



P Q	#1 $P \cdot Q$	#2 $Q + \bar{Q}$	#3 $(\#1) \cdot (\#2)$
00	0	1	0
01	0	1	0
10	0	1	0
11	1	1	1

Answer:  $P \cdot Q$


Figure C.

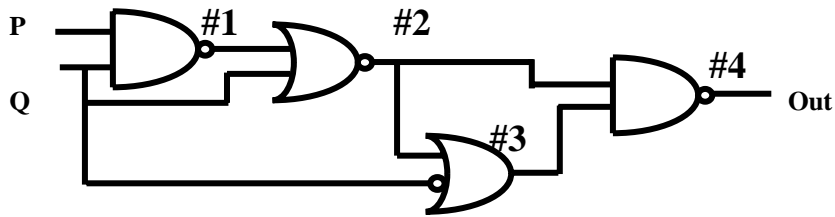

P Q	#1 $\overline{P \cdot Q}$	#2 $\overline{\#1 + Q}$	#3 $\#2 + \bar{Q}$	#4 $\overline{(\#2) \cdot (\#3)}$
00	1	0	1	1
01	1	0	0	1
10	1	0	1	1
11	0	0	0	1

Answer: 1


Figure D.

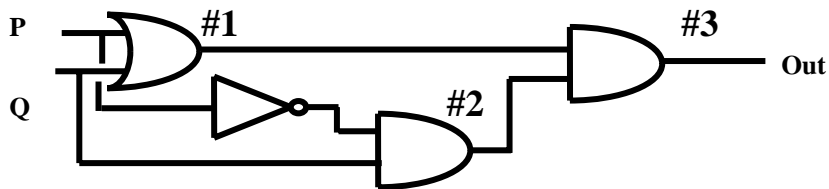

P Q	#1 $P + Q$	#2 $\bar{P} \cdot Q$	#3 $\#1 \cdot \#2$
00	0	0	0
01	1	1	1
10	1	0	0
11	1	0	0

Answer:  $\bar{P} \cdot Q$
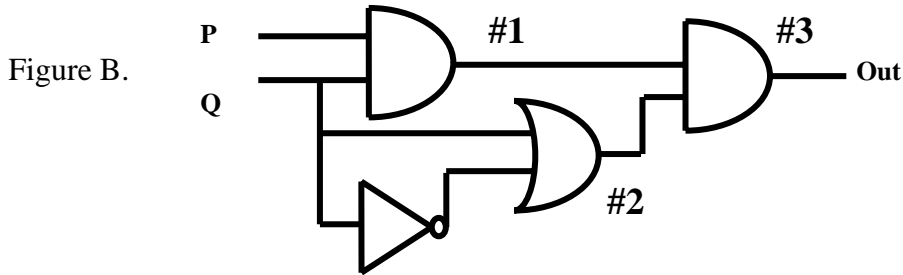
## Answers (Boolean Equations) to Logic Diagram Review Problems




#1  $P \cdot Q$

#2  $Q + \bar{Q} = 1$

#3  $(P \cdot Q) \cdot (1) = P \cdot Q$

**Answer:  $P \cdot Q$**

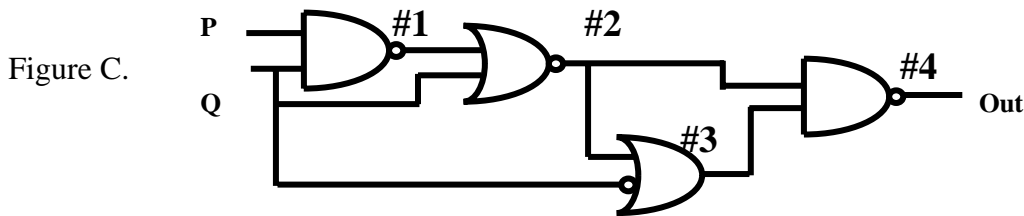


#1  $\overline{P \cdot Q}$

#2  $\overline{P \cdot Q} + Q = (P \cdot Q) \cdot \bar{Q} = P \cdot Q \cdot \bar{Q} = P \cdot 0 = 0$

#3  $0 + \bar{Q} = \bar{Q}$

#4  $0 \cdot \bar{Q} = 1 + Q = 1$

**Answer: 1**

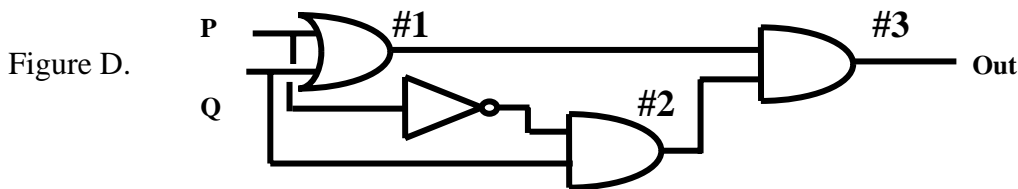

#1  $P + Q$

#2  $\bar{P} \cdot Q$

\*\*\* #3  $(P + Q) \cdot (\bar{P} \cdot Q) = (\bar{P} \cdot Q) \cdot (P + Q) = (\bar{P} \cdot Q) \cdot P + (\bar{P} \cdot Q) \cdot Q = \bar{P} \cdot P \cdot Q + \bar{P} \cdot Q \cdot Q = 0 \cdot Q + \bar{P} \cdot Q = 0 + \bar{P} \cdot Q = \bar{P} \cdot Q$

\*\*\* From Boolean Algebra Properties:  $A(B + C) = AB + AC$

$A(B + C) = AB + AC$  where  $A = \bar{P} \cdot Q$   $B = P$   $C = Q$

$(\bar{P} \cdot Q) \cdot (P + Q) = (\bar{P} \cdot Q) \cdot P + (\bar{P} \cdot Q) \cdot Q = \bar{P} \cdot P \cdot Q + \bar{P} \cdot Q \cdot Q = 0 \cdot Q + \bar{P} \cdot Q = 0 + \bar{P} \cdot Q = \bar{P} \cdot Q$       **Answer:  $\bar{P} \cdot Q$**