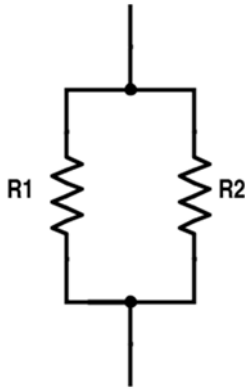


## Equivalent Resistance



$$R_{EQ} = \frac{R_1 R_2}{R_1 + R_2}$$

Example 1:

$$R_1 = 100 \quad R_2 = 300$$

$$R_{EQ} = \frac{100 \times 300}{100 + 300} = \frac{30,000}{400} = \frac{300}{4} = 75$$

Example 2:

$$R_1 = 2700 \quad R_2 = 2700$$

$$R_{EQ} = \frac{2700 \times 2700}{2700 + 2700} = \frac{2700 \times 2700}{2(2700)} = \frac{2700}{2} = 1350$$

Example 3:

$$R_1 = 100 \quad R_2 = 10M$$


$$R_{EQ} = \frac{100 \times 10^6}{100 + 1,000,000} = \frac{10^8}{1,000,100} \approx \frac{10^8}{10^6} = 10^2 = 100$$

Example 4:

$$R_1 = 5000 \quad R_2 = 0$$

$$R_{EQ} = \frac{5000 \times 0}{5000 + 0} = 0$$
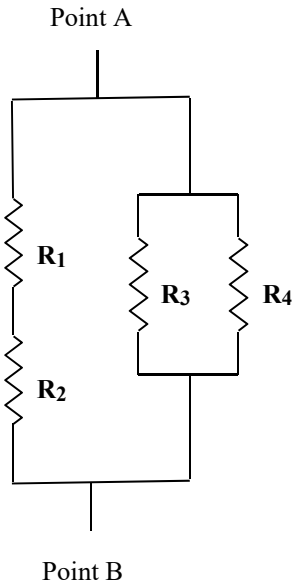
## Series and Parallel Resistor Example Problems



Given the configuration above, calculate the equivalent resistance from Point A to Point B.

$$R_1 = 100 \, \Omega \quad R_2 = 300 \, \Omega \quad R_3 = 100 \, \Omega \quad R_4 = 400 \, \Omega$$

If the current through R4 is 100 mA;

What is the voltage across R2?

What is the current through R1?

What is the total current from Point A to Point B?

Equivalent Resistance from Point A to Point B	66.7 $\Omega$
Voltage across R2	30 V
Current through R1	100 mA
Total current from Point A to Point B	600 mA

What if  $I_{R4} = 100 \text{ mA}$ :

Find  $I_{R3}$ ,  $V_{R2}$ ,  $I_{R1}$ ,  $V_{AB}$ , Total Current

$$I_{R3} = 400 \text{ mA}$$


$$V_{R2} = 30 \text{ V}$$

$$I_{R1} = 100 \text{ mA}$$

$$V_{AB} = 40 \text{ V}$$


$$\text{Total Current} = 600 \text{ mA}$$
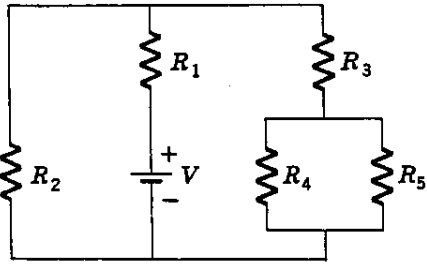
## Circuit Analysis by Equivalent Resistors




$$\begin{aligned} R_1 &= 270 \\ R_2 &= 500 \\ R_3 &= 720 \\ R_4 &= 400 \\ R_5 &= 600 \\ V &= 9 \text{ VDC} \end{aligned}$$

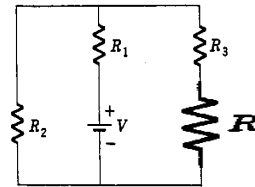
$$R_4 \parallel R_5 = (400 \times 600) / (400 + 600) = 240000 / 1000 = 240$$



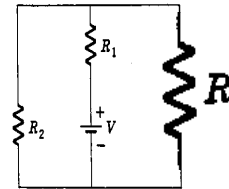
$$R_3 + R_4 \parallel R_5 = 720 + 240 = 960$$


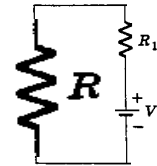
$$R_2 \parallel (R_3 + R_4 \parallel R_5) = 500 \parallel 960 = (500 \times 960) / (500 + 960) = 330$$


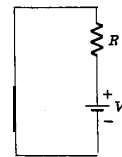
$$R_{eq} = R_1 + 330 = 270 + 330 = 600 \text{ Ohms}$$




$$I_{R1} = V / 600 = 9 / 600 = 1.5 \times 10^{-2} = 0.015 \text{ A} = 15 \text{ milliamps}$$

$$V_{R1} = R_1 \times I_{R1} = 270 \times 0.015 = 4 \text{ V}$$

$$V_{R2} = V - V_{R1} = 9 - 4 = 5 \text{ V}$$

## Circuit Analysis by Equivalent Resistors

### Additional Analysis

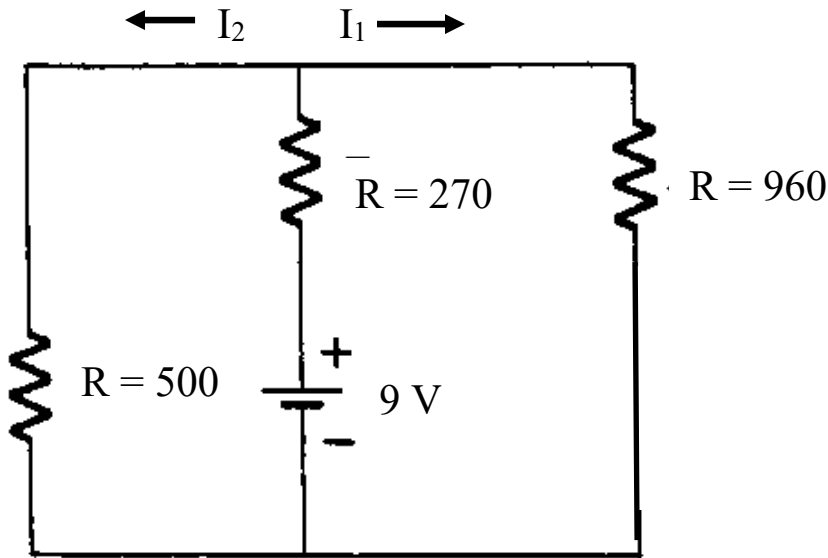

See Page One for equivalent resistances

Loop Currents

$$\text{Loop \#1} \quad 9 = (i_1 + i_2)R_1 + i_1R_2$$

$$\text{Loop \#2} \quad 9 = (i_1 + i_2)R_1 + i_1R_{EQ}$$

$$R_{EQ} = R_3 + R_4 \parallel R_5 = 720 + \frac{400 \times 600}{400 + 600} = 720 + 240 = 960$$

From #1 and #2

$$(i_1 + i_2)R_1 + i_1R_2 = (i_1 + i_2)R_1 + i_1R_{EQ}$$

$$i_1R_2 = i_1R_{EQ}$$

$$i_1 = i_2 \frac{R_{EQ}}{R_2} = i_2 \frac{960}{600} = 1.92i_2$$

From #1

$$9 = (i_1 + i_2)R_1 + i_1R_2$$

$$9 = (1.92i_2 + i_2)270 + 1.92i_2(500)$$

$$9 = 2.92i_2(270) + 1.92i_2(500)$$

$$9 = i_2(2.92 \times 270 + 1.92 \times 500)$$


$$i_2 = \frac{9}{788 + 960} = \frac{9}{1748} = .0052$$

$$i_1 = 1.92 \times .0052 = 0.0099$$

$$i_1 = 0.010\text{A} \quad i_2 = 0.005\text{A}$$

$$I_{R_1} = 0.010 + 0.005 = 0.015\text{A}$$
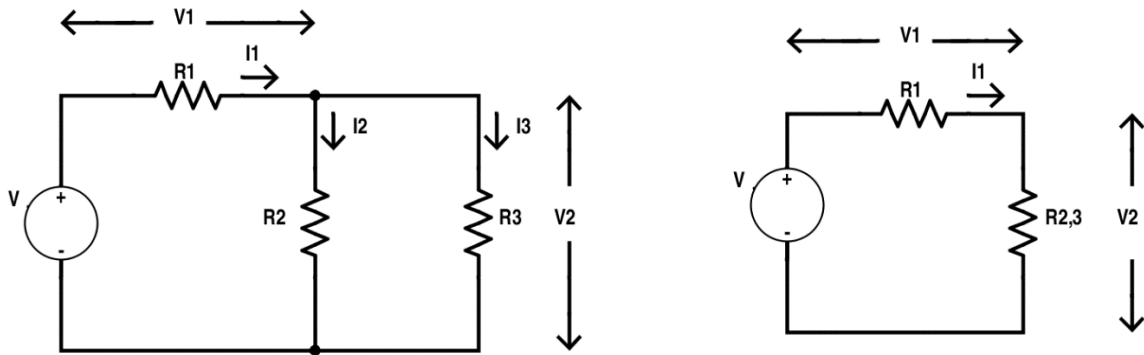
$$V_{R_1} = I_{R_1} R_1 = 0.015 \times 270 = 4.05\text{V}$$



Find  $V_1$ ,  $V_2$ ,  $I_2$ ,  $I_3$

Given:  $V = 10\text{V}$       $R_1 = 22\text{k}\Omega$       $R_2 = 47\text{k}\Omega$       $R_3 = 180\text{k}\Omega$

$$R_{2,3} = \frac{R_2 R_3}{R_2 + R_3} = \frac{47 \times 180}{47 + 180} = 37.26\text{k}\Omega$$

$$V = I_1 (R_1 + R_{2,3})$$

$$I_1 = \frac{V}{R_1 + R_{2,3}} = \frac{10}{(22 + 37.26) \times 10^3} = 0.168\text{mA}$$

Use the voltage divider rule

$$V_1 = \left[ \frac{R_1}{R_1 + R_{2,3}} \right] V = \left[ \frac{22}{22 + 37.26} \right] \times 10 = 3.71\text{V}$$

$$V_2 = \left[ \frac{R_{2,3}}{R_{2,3} + R_1} \right] V = \left[ \frac{37.26}{37.26 + 22} \right] \times 10 = 6.288\text{V}$$

Use the current divider rule

$$I_2 = \left[ \frac{R_3}{R_2 + R_3} \right] I_1 = \left[ \frac{180}{47 + 180} \right] \times 0.168 = 0.133\text{mA}$$

$$I_3 = \left[ \frac{R_2}{R_3 + R_2} \right] I_1 = \left[ \frac{47}{180 + 47} \right] \times 0.168 = 0.034\text{mA}$$