



Electrical Current Flow

Electron Flow - From excess to deficient
 Conventional Current Flow
 Internal to Source (Battery)
 Negative to Positive
 External from Source (Battery)
 Positive to Negative
 Voltage Drop - Across a Resistor + to -
 Negative Current - Assumed Direction Reversed



Electrical Theory

Ohm's Law
 $I = V/R$ (DC) $I = V/Z$ (AC)

Series Parallel
 $R_{eq} = R_1 + R_2 + R_3$ $1/R_{eq} = 1/R_1 + 1/R_2 + 1/R_3$

Kirchoff's Law
 Sum of Loop Voltages = 0
 Sum of Node Currents = 0

Joule's Law
 $P = IE = I^2R$ (I Squared R Loss)




Equivalent Circuits

Thevenin
 Two Terminal Resistor and Battery Circuit
 Series Voltage Source and Equivalent Resistor
 Voltage Source = Open Circuit Voltage
 Equivalent Resistor = $V / \text{Short Circuit Current}$

Norton
 Two Terminal Resistor and Battery Circuit
 Parallel Voltage Source and Equivalent Resistor
 Current Source = Short Circuit Current
 Equivalent Resistor = $V / \text{Short Circuit Current}$

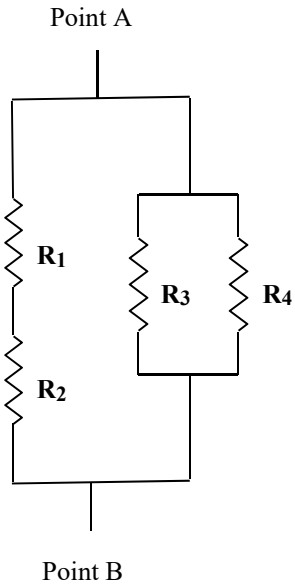Series and Parallel Resistor Example Problems



Given the configuration above, calculate the equivalent resistance from Point A to Point B.

$$R_1 = 100 \, \Omega \quad R_2 = 300 \, \Omega \quad R_3 = 100 \, \Omega \quad R_4 = 400 \, \Omega$$

If the current through R₄ is 100 mA;


What is the voltage across R₂?

What is the current through R₁?


What is the total current from Point A to Point B?

Equivalent Resistance from Point A to Point B	66.7 Ω
Voltage across R ₂	30 V
Current through R ₁	100 mA
Total current from Point A to Point B	600 mA

Simple Voltage and Current Dividers

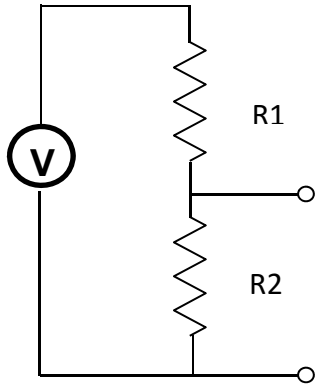

$$V_{R_2} = V \frac{R_2}{R_1 + R_2}$$

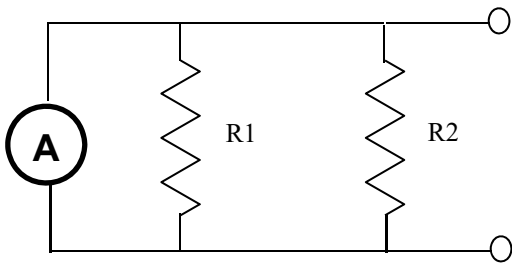

$$I_{R_2} = I \frac{R_1}{R_1 + R_2}$$

Equivalent Circuits

Thevenin's Theorem

Any network of resistors and batteries having two output terminals, may be replaced by a series combination of a voltage source V_{eq} and a resistance R_{eq} .

The equivalent emf V_{eq} is the potential at the output terminals when the output current is zero (open-circuit voltage).

The equivalent resistance R_{eq} is the ratio of the V_{eq} to the output current when R_{Load} is zero (short-circuit current).

Norton's Theorem

Any network of resistors and batteries having two output terminals, may be replaced by a parallel combination of a current source I_{eq} and a resistance R_{eq} .

The current source I_{eq} is the short-circuit current in the output terminals, and the resistance R_{eq} is the same as for Thevenin's Theorem.

