

Delta & Y Configurations, Principles of Superposition, Resistor Voltage Divider Designs

Use following techniques to solve for current through and voltage across a network resistor:

- Equivalent Resistances
- Kirchoff's Voltage Law
- Kirchoff's Current Law
- Principle of Superposition
- Thevenin Equivalent
- Norton Equivalent

Sketch Series Resistors Voltage Divider (including voltage source)

Calculate voltage across load resistor

Voltage Divider (Resistors in Series with Voltage Source) $V_2 = V (R_2 / (R_1 + R_2))$

Sketch Parallel Resistors Current Divider (including current source)

Calculate current through load resistor

Current Divider (Resistors in Parallel with Current Source) $I_2 = I (R_1 / (R_1 + R_2))$

Design Voltage Divider Network (10% rule for two resistors and voltage source) given output requirements

Convert Delta configuration to equivalent Wye configuration

Convert Wye configuration to equivalent Delta configuration

Solve Voltage Source & Current Source Circuit Network Problems (using Superposition)

Attachments:

Delta & Y Configurations and Conversions (Figures & Equations)

Five Resistor Equivalent


Y to Delta & Delta to Y Practice Conversion Problems

Principle of Superposition Example Problem

Principle of Superposition (Figure 30-3 Giorgio Rizzoni 2009).pdf

Voltage Divider Design Notes & Practice Problem

Y to Delta & Delta to Y Conversions

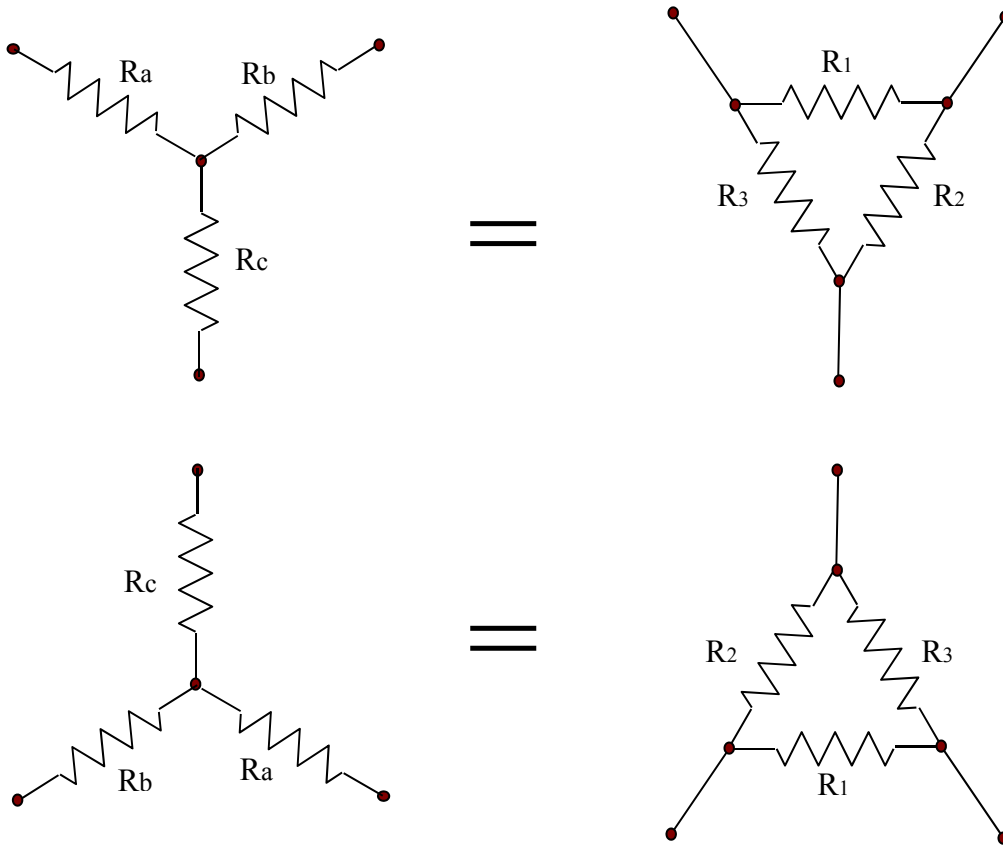

Y to Delta Conversion

$$R_1 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_c}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_a}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_b}$$

Delta to Y Conversion

$$R_a = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

Calculate the equivalent resistance for a five resistor network (See Figure 1.)


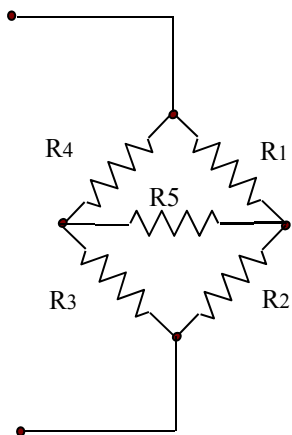



Figure 1.

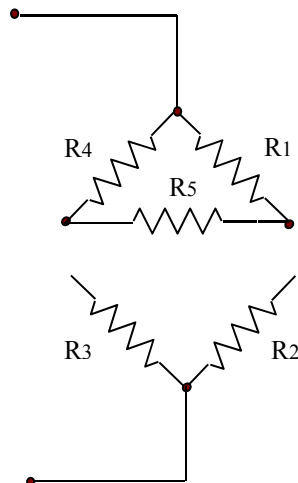Step 1. Divide into two parts.
Delta(R1 R5 R4) and "V"(R2 R3)




Step 2. Convert Delta(R1 R5 R4)

to Y(Rc Ra Rb)

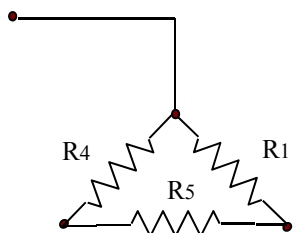

=

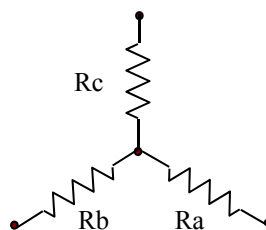


Step 2. Delta(R1 R5 R4) to Y(Rc Ra Rb) - continued
Note: Rotated and Reflected Labeling

Step 3. Combine Delta(R1 R5 R4) with "V"(R2 R3)

$$R_c = \frac{R_1 R_4}{R_1 + R_4 + R_5}$$

$$R_b = \frac{R_4 R_5}{R_1 + R_4 + R_5}$$
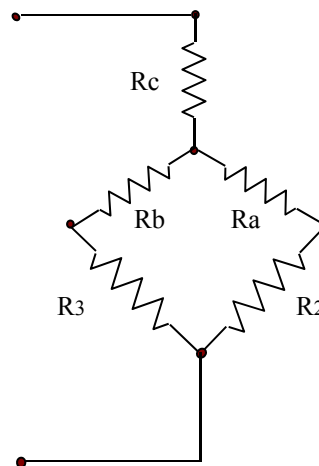
$$R_a = \frac{R_1 R_5}{R_1 + R_4 + R_5}$$



Step 4.

Rb in Series with R3 therefore $R_b R_3 = R_b + R_3$

Ra in Series with R2 therefore $R_a R_2 = R_a + R_2$

Step 5.

$$R_b R_3 \text{ in Parallel with } R_a R_2 = \frac{(R_b R_3) \times (R_a R_2)}{(R_b R_3) + (R_a R_2)}$$

Step 6.

Rc in Series with Parallel $R_b R_3 \parallel R_a R_2$

Step 7. $R_{eq} = R_c + \text{Parallel } R_b R_3 \parallel R_a R_2$

Y to Delta & Delta to Y Practice Problem Conversions

1. Write closed-form solutions for each of the following configurations.

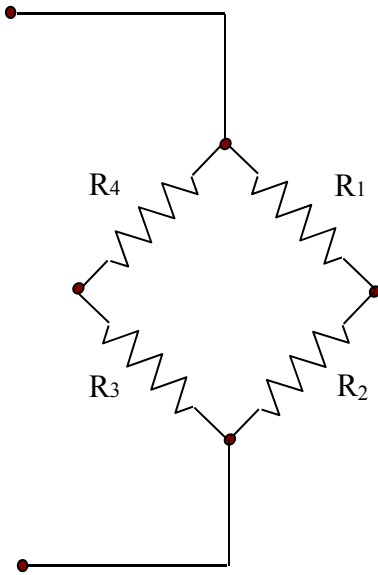


Figure A

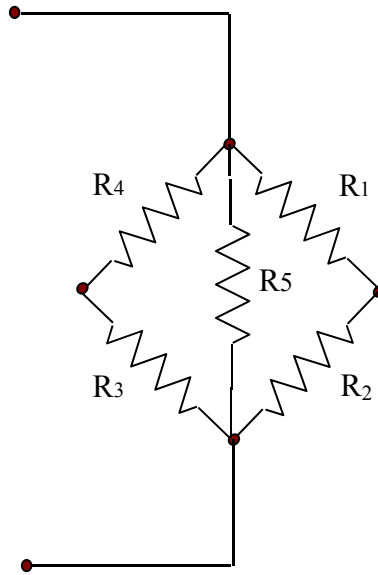


Figure B

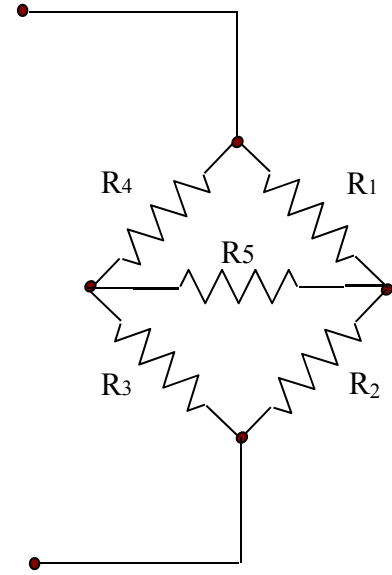


Figure C

2. For Figures A, B, C,

Find single equivalent resistive values for $R_1 = 5$, $R_2 = 7$, $R_3 = 8$, $R_4 = 3$, $R_5 = 4$

3. Answers:

Figure A. $R_{eq} = 5.74$

Figure B. $R_{eq} = 2.36$

Figure C. $R_{eq} = 5.66$

Solving Voltage and Current Circuit Problems Using the Theory of Superposition

The overall effect for two or more stimuli to a linear system is equal to the sum of individual effects.

Refer to Figure 1.

Objective:

- Calculate $V_{R_{Load}}$
- Calculate $I_{R_{Load}}$

Given:

$$I = 3 \text{ A}$$

$$V = 9 \text{ V}$$

$$R_1 = 3 \ \Omega$$

$$R_2 = 4 \ \Omega$$

$$R_{Load} = 2 \ \Omega$$

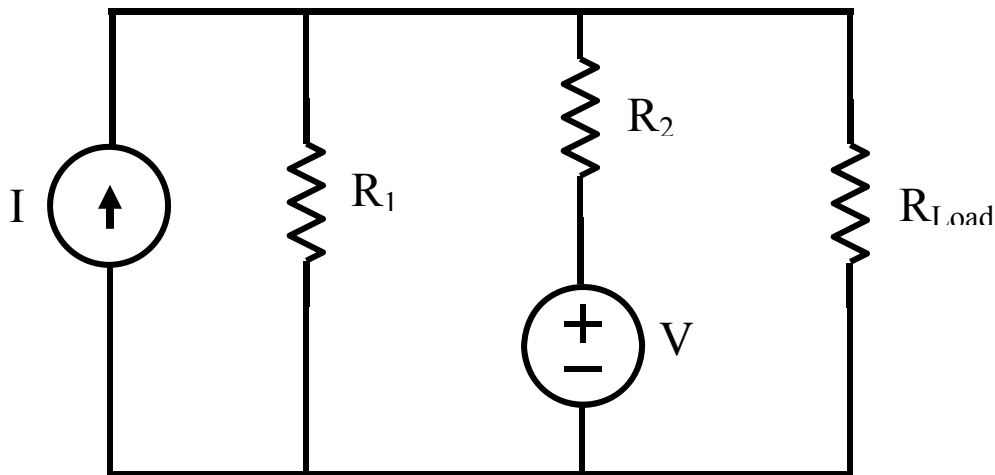


Figure 1.

Procedure:

- Short all Voltage Sources Calculate $V_{R_{Load}}$ (Generated by Current Sources) $V_{R_{Load}} = 2.77 \text{ V}$
- Open all Current Sources Calculate $V_{R_{Load}}$ (Generated by Voltage Sources) $V_{R_{Load}} = 2.08 \text{ V}$
- Calculate overall results by adding results from Step I and Step II $V_{R_{Load}} = 2.77 + 2.08 = 4.85 \text{ Volts}$

$$\text{Calculate } I_{R_{Load}} = V_{R_{Load}} / R_{Load} = 4.85 \text{ V} / 2 \ \Omega = 2.43 \text{ Amps}$$

Principle of Superposition


Problem

Determine the voltage across resistor R in the circuit of Figure 3.30.

Solution


Known Quantities: The values of the voltage sources and of the resistors in the circuit of Figure 3.30 are $I_B = 12\text{ A}$; $V_G = 12\text{ V}$; $R_B = 1\ \Omega$; $R_G = 0.3\ \Omega$; $R = 0.23\ \Omega$.

Find: The voltage across R .

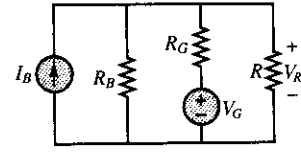

(a)

Figure 3.30 (a) Circuit used to demonstrate the principle of superposition

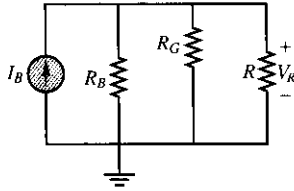

(b)

Figure 3.30 (b) Circuit obtained by suppressing the voltage source

Analysis: Specify a ground node and the polarity of the voltage across R . Suppress the voltage source by replacing it with a short circuit. Redraw the circuit, as shown in Figure 3.30(b), and apply KCL:

$$-I_B + \frac{V_{R-I}}{R_B} + \frac{V_{R-I}}{R_G} + \frac{V_{R-I}}{R} = 0$$

$$V_{R-I} = \frac{I_B}{1/R_B + 1/R_G + 1/R} = \frac{12}{1/1 + 1/0.3 + 1/0.23} = 1.38\text{ V}$$


Suppress the current source by replacing it with an open circuit, draw the resulting circuit, as shown in Figure 3.30(c), and apply KCL:

$$\frac{V_{R-V}}{R_B} + \frac{V_{R-V} - V_G}{R_G} + \frac{V_{R-V}}{R} = 0$$

$$V_{R-V} = \frac{V_G/R_G}{1/R_B + 1/R_G + 1/R} = \frac{12/0.3}{1/1 + 1/0.3 + 1/0.23} = 4.61\text{ V}$$

Finally, we compute the voltage across R as the sum of its two components:
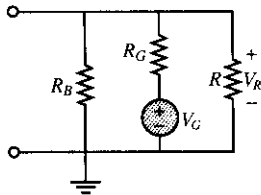
$$V_R = V_{R-I} + V_{R-V} = 5.99\text{ V}$$




(c)

Figure 3.30 (c) Circuit obtained by suppressing the current source

Voltage Divider Design Note (10% Rule) - Minimizes I²R Heat Loss

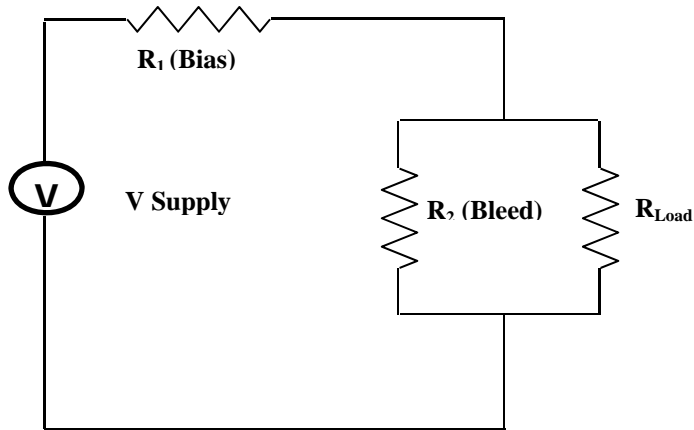Given values for voltage source and R_{Load} voltage and current specifications (V_{Load} & I_{Load}); Determine values for Bias Resistor (R₁) and Bleed Resistor (R₂).



Step 1. Calculate Load Resistor ($= V_{Load} / I_{Load}$)

Step 2. Calculate I_2 (Bleed Current) = 10% I_{Load}

Step 3. Select R_2 (Bleed Resistor) based on I_2 such that $R_2 = V_{R2} / I_2$ (Note: $V_{R2} = V_{R_{Load}}$)

Step 4. Calculate $I_{Total} = I_{Load} + I_2$

Step 5. Calculate R_1 (Bias Resistor) = $(V_S - V_{Load}) / (I_{Total})$

Example Problem:

Given:

$$V_S = 12 \text{ volts}$$

$$V_{Load} = 7.5 \text{ V @ } 50 \text{ mA}$$

Find:

$$R_{Load} = 150 \text{ Ohms}$$

$$\text{Bleed Resistor} = 1500 \text{ Ohms}$$

$$\text{Bias Resistor} = 82 \text{ Ohms}$$

Check Results:

Note - by design

$$I_{Total} = 1.1 \times I_{Load} = 55 \text{ mA}$$

$$I_{Bleed} = 0.1 \times I_{Load} = 5 \text{ mA}$$

$$R_{Bleed} = 10 \times R_{Load} = 1500 \text{ Ohms}$$

$$V_{RBleed} = R_{Bleed} \times I_{Bleed} = 1500 \times 5 \times 10^{-3} = 7.5 \text{ V}$$

$$\text{Sanity Check: } V_{RBleed} = V_{Load} = 7.5 \text{ V} \text{ !!!!!}$$

$$\text{Sanity Check: } V_{RBias} = V_S - V_{RBleed} = 12 - 7.5 = 4.5 \text{ V}$$

$$V_{RBias} = I_{Total} \times R_{Bias} = 55 \times 10^{-3} \times 82 = 4.5 \text{ V} \text{ !!!!!!!!!}$$

Short Cut Closed Form:

$$R_{Bias} = (V_S - V_{Load}) / (1.1 \times I_{Load}) = (12 - 7.5) / (1.1 \times 0.050) = 4.5 / 0.055 = 82 \text{ Ohms}$$

$$R_{Bleed} = V_{Load} / (0.1 \times I_{Load}) = 7.5 / (0.1 \times 0.050) = 7.5 / 0.005 = 1500 \text{ Ohms}$$