

# Diode Characteristics

Source: James Brophy, Basic Electronics for Scientists, 5<sup>th</sup> Edition

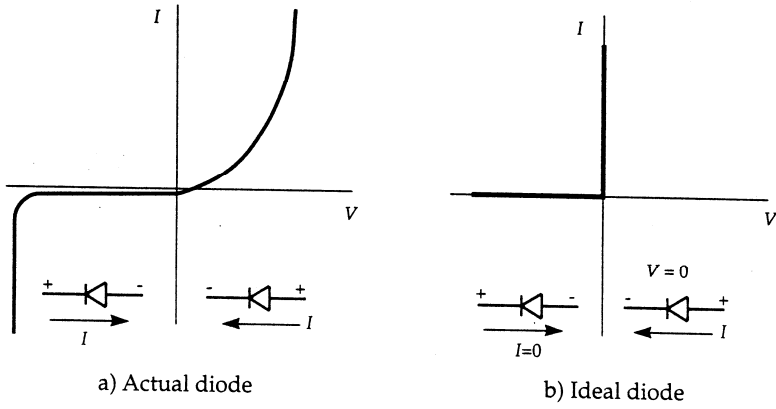


Figure 6.18 Characteristics of a diode.

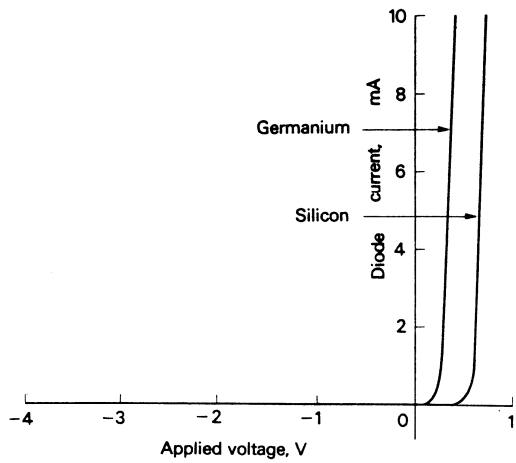


Figure 3-2 Current-voltage characteristics of germanium and silicon junction diodes.


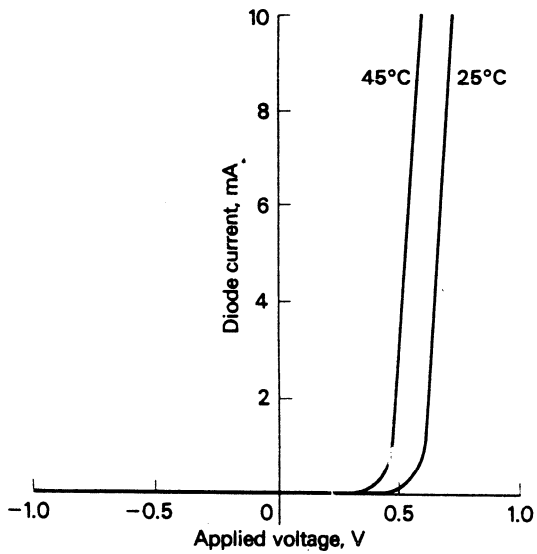


Figure 3-3 Effect of temperature on current-voltage characteristics of silicon junction diode.


# Semiconductors, P-Type, and N-Type Materials

## Forward and Reverse Biasing of the PN Junction

Reference: Aminian and Kazimierczuk, *Electronic Devices: A Design Approach*, 2004

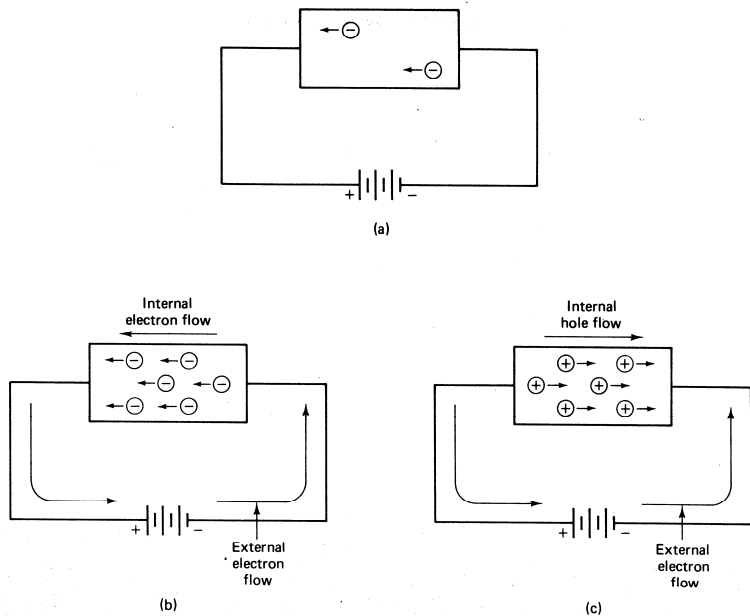

**Figure 1-6** Conduction in semiconductor materials: (a) very little current flow in pure silicon; (b) electron flow in *n*-type material; (c) hole flow in *p*-type material.

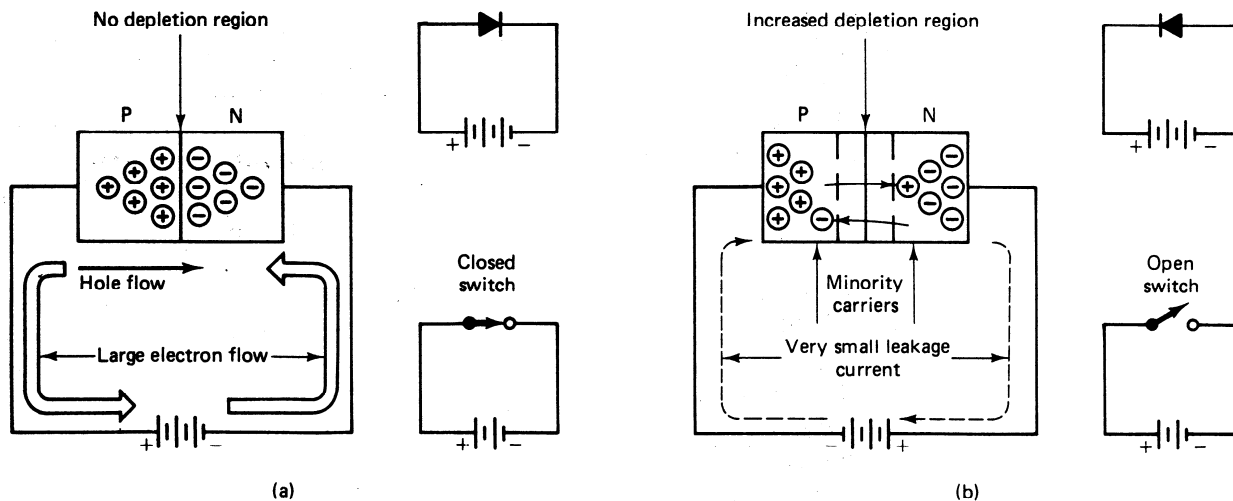

**Biasing the diode: (a) forward bias; (b) reverse bias.**

# Forward and Reverse Biasing of the PN Junction - continued

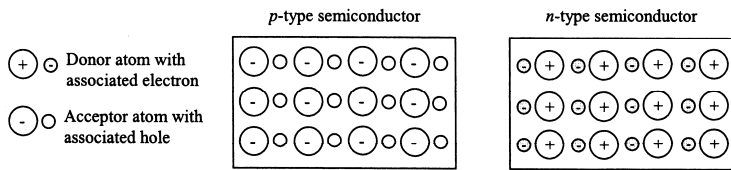


Figure 1-9: Blocks of *p*-type and *n*-type semiconductors before they are joined

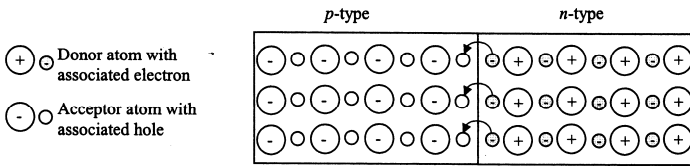


Figure 1-10: Blocks of *p*-type and *n*-type semiconductors at the instant they are joined

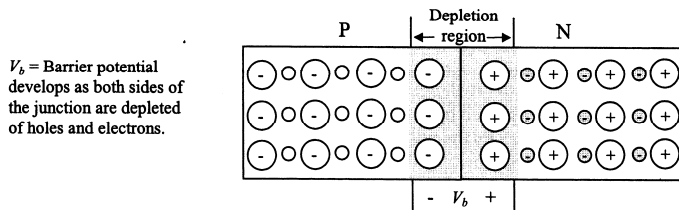


Figure 1-11: The *p-n* junction after recombination of electron-hole pairs

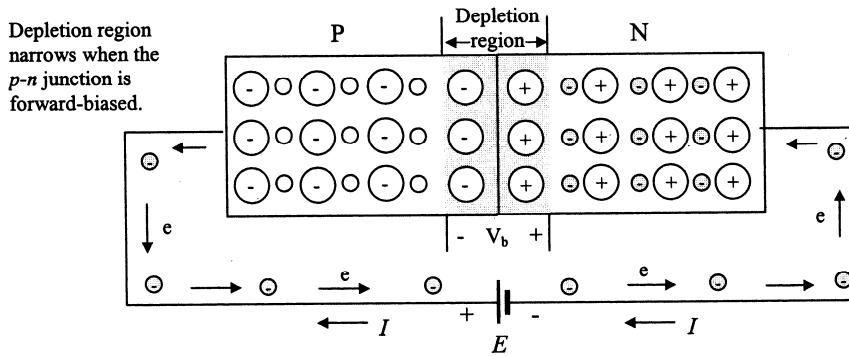


Figure 1-12: Forward biasing the *p-n* junction with an external source

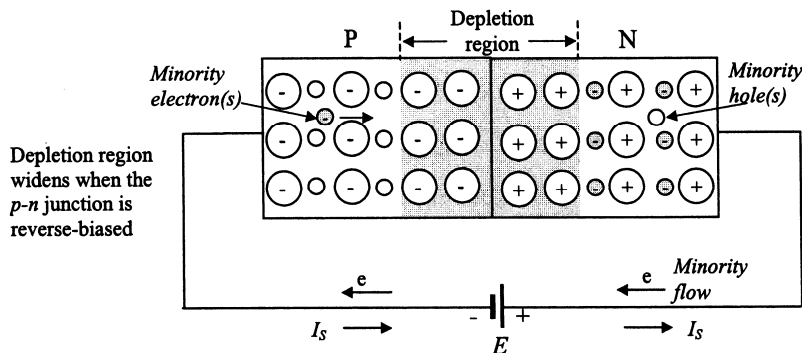


Figure 1-13: Reverse biasing the *p-n* junction with an external source

# Diode Rectifiers, Clippers, and Clamps

Source: James Brophy, Basic Electronics for Scientists, 5<sup>th</sup> Edition

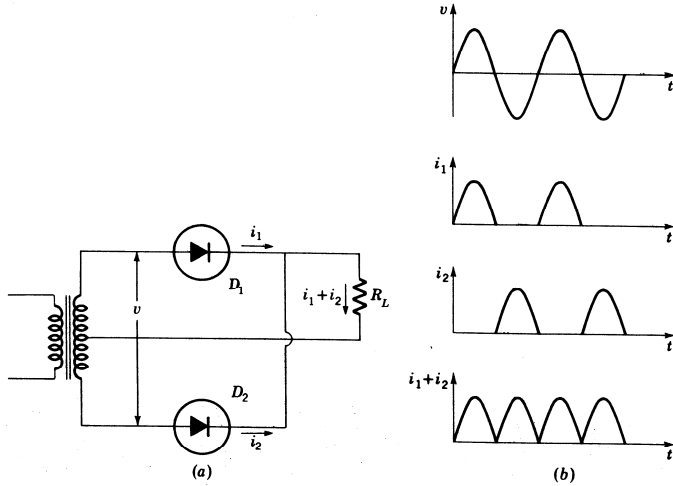


Figure 3-8 (a) Full-wave rectifier and (b) waveforms.

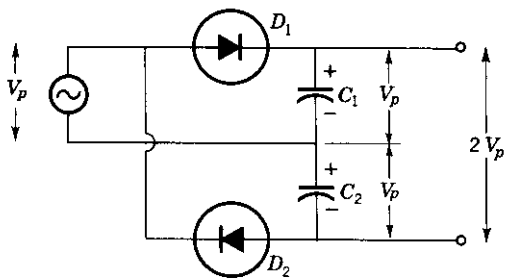


Figure 3-10 Voltage-doubler rectifier yields dc output voltage equal to twice peak input voltage.

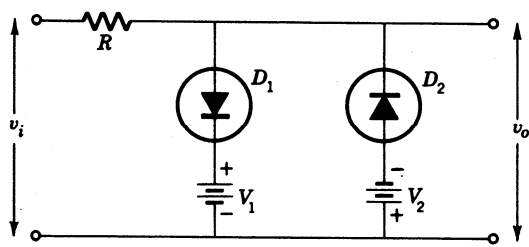


Figure 3-22 Diode clipper.

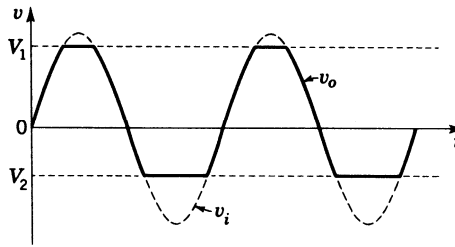


Figure 3-23 Maximum amplitudes in output waveform of diode clipper are limited to values of bias voltage.

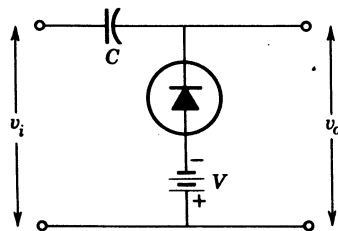


Figure 3-24 Diode clamp.

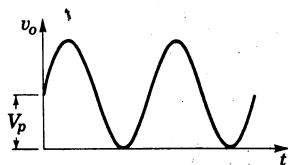


Figure 3-25 Negative peak of output waveform is clamped at zero when  $V = 0$  in diode clamp circuit of Fig. 3-24.

## Diode Circuits

### Example

Calculate  $V_0$

$$V = 0.7 + I_D R_1 + 0.7 + I_D R_2$$

$$V - 0.7 - 0.7 = I_D (R_1 + R_2)$$


$$I_D = [V - (0.7 + 0.7)] / (R_1 + R_2)$$

$$I_D = 14.6 / (2000 + 1000)$$

$$I_D = 4.9 \text{ mA}$$

$$V_0 = 0.7 + I_D R_2$$

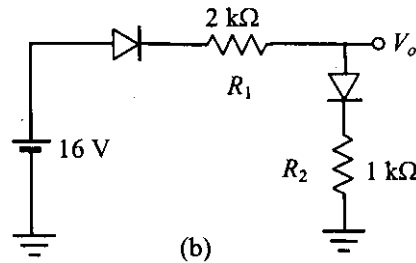
$$V_0 = 0.7 + 0.0049 \times 1000 = 0.7 + 4.9 = 5.6 \text{ V}$$


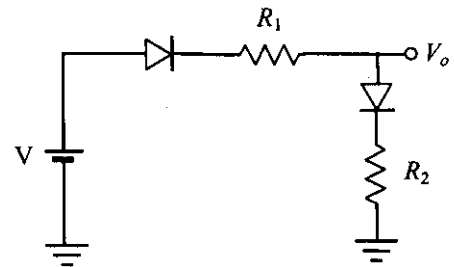
### Exercise

Calculate  $V_0$  for  $V = 15 \text{ V}$ ,  $R_1 = 2200 \Omega$ ,  $R_2 = 3300 \Omega$

Answer:  $I_D = 2.5 \text{ mA}$     $V_0 = 8.9 \text{ V}$



### Example

Calculate  $V_0$

$$+15 = 0.7 + I_D R_1 + 0.7 + I_D R_2 - 5$$

$$20 - 0.7 - 0.7 = I_D (R_1 + R_2)$$


$$I_D = 18.6 / (R_1 + R_2)$$

$$I_D = 18.6 / (2200 + 3300)$$

$$I_D = 3.38 \text{ mA}$$

$$V_0 = 0.7 + I_D R_2 - 5.0$$

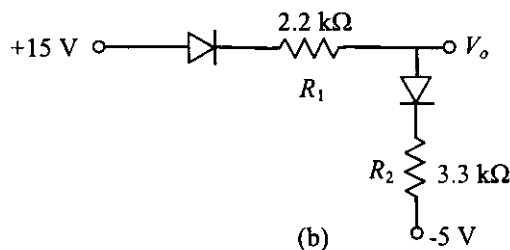
$$V_0 = 0.7 + 0.00338 \times 3300 - 5.0 = 0.7 + 11.2 - 5.0 = 6.9 \text{ V}$$


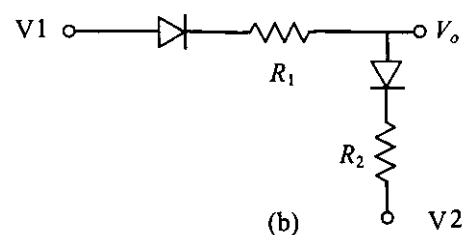
### Exercise

Calculate  $V_0$  for  $V_1 = +10 \text{ V}$     $V_2 = -5 \text{ V}$   
 $R_1 = 1100 \Omega$     $R_2 = 2200 \Omega$

Answer:  $I_D = 4.1 \text{ mA}$     $V_0 = 4.8 \text{ V}$



## Diode Circuits - continued

**Example** (Refer to the Diode Circuit Lecture Notes)

Calculate the Current  $I_D$

1. Remove Diode (Replace by  $V_{TH}$ )

For Voltage Divider  $V_{TH} = V [ R_2 / (R_1 + R_2) ]$

$$V_{TH} = 16 [ 4700 / (5100 + 4700) ] = 7.67 \text{ V}$$

2. Short  $V_{source}$  ( $R_1$  in parallel with  $R_2$ )


$$R_{EQ} = (R_1 \times R_2) / (R_1 + R_2)$$

$$R_{EQ} = (5100 \times 4700) / (5100 + 4700) = 2446 \Omega$$

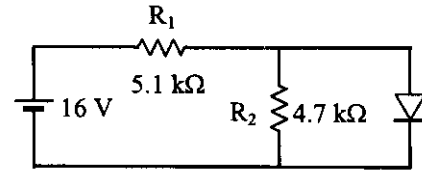3. Redraw with  $V_{TH}$ ,  $R_{EQ}$ , Diode

$$V_{TH} = I_D R_{EQ} + V_D \quad I_D = (V_{TH} - V_D) / R_{EQ}$$

$$I_D = (7.67 - 0.7) / 2446 = 2.85 \text{ mA}$$



### Alternative Solution Method

$$V_{R2} = V_D = 0.7 \text{ V}$$

$$I_{R2} = V_{R2} / R_2 = 0.7 / 4700 = 0.15 \text{ mA}$$

$$I_{R1} = (V - V_{R2}) / R_1 = (16.0 - 0.7) / 5100 = 3.0 \text{ mA}$$


$$I_{Total} = I_{R1}$$

$$I_D = I_{Total} - I_{R2} = 3.00 - 0.15 = 2.85 \text{ mA}$$



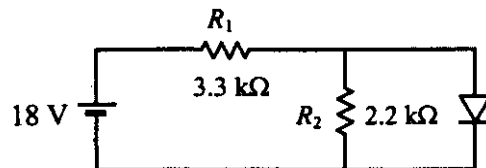
### Exercise

Calculate the Current  $I_D$


Answer:  $I_D = 4.9 \text{ mA}$     $V_D = 0.7 \text{ V}$




# Light Emitting Diode LED

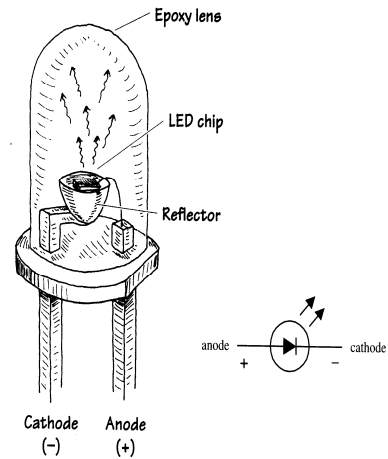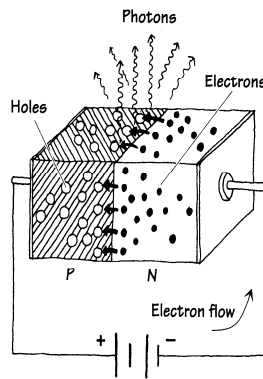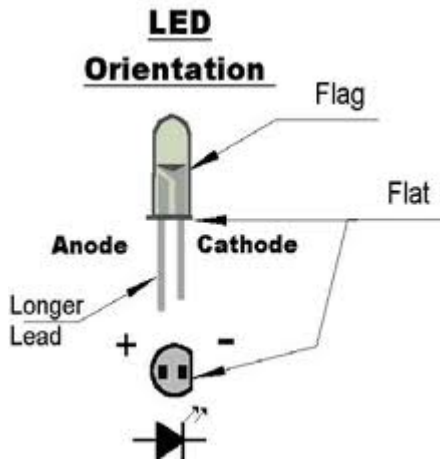

# PhotoResistor

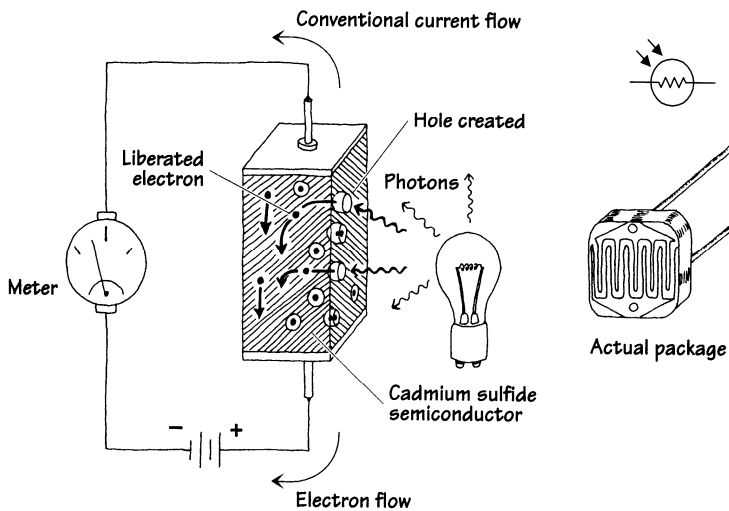


## Light-Sensitive Voltage Divider

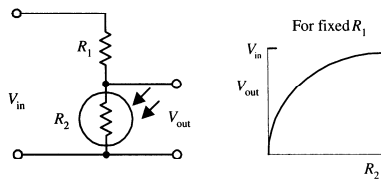


$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

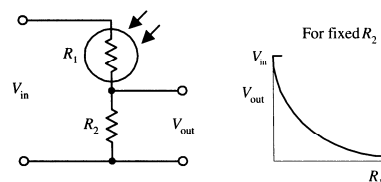
As the intensity of light increases, the resistance of the photoresistor decreases, so  $V_{out}$  in the top circuit gets smaller as more light hits it, whereas  $V_{out}$  in the lower circuit gets larger.



# PhotoDiode

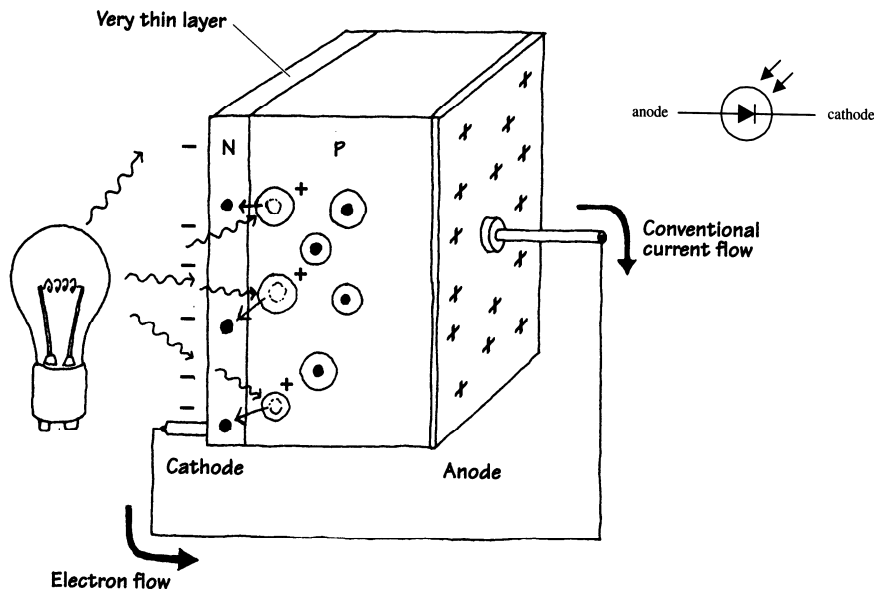


# PhotoTransistors

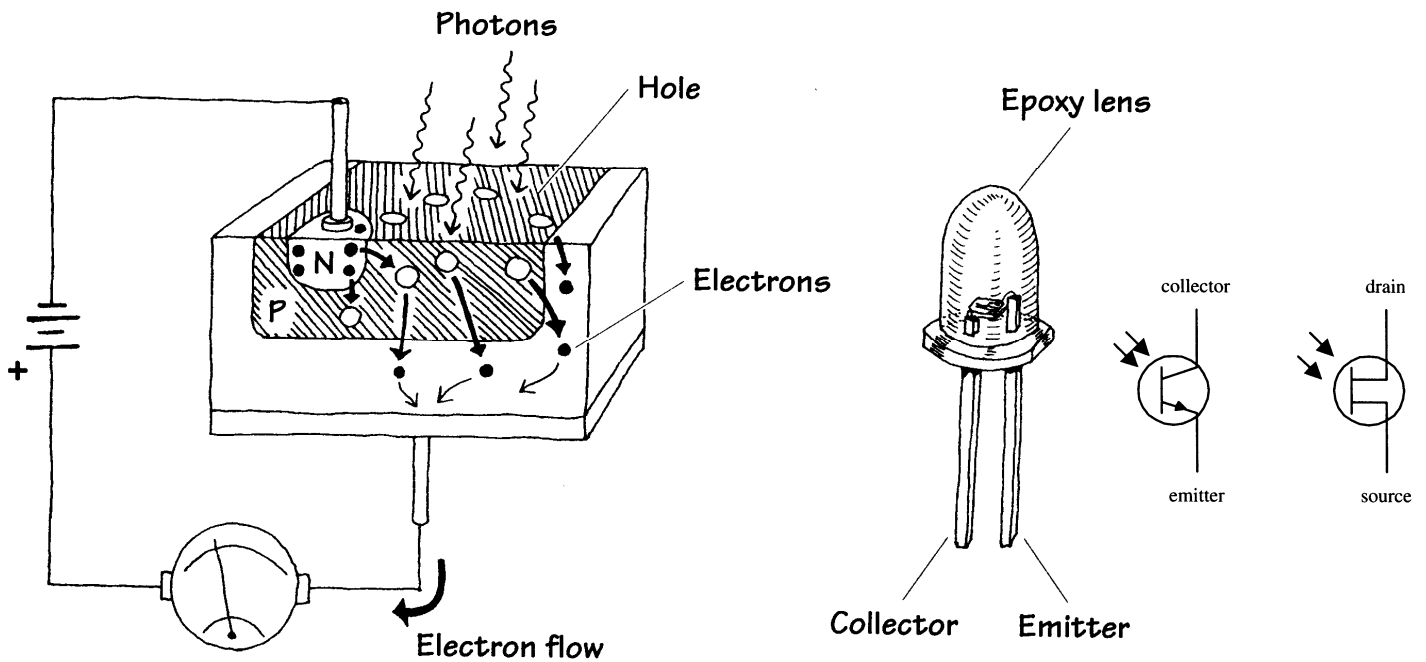


Source: Scherz, Practical Electronics for Inventors, 2nd & 3rd Editions



## LED Current Limiting

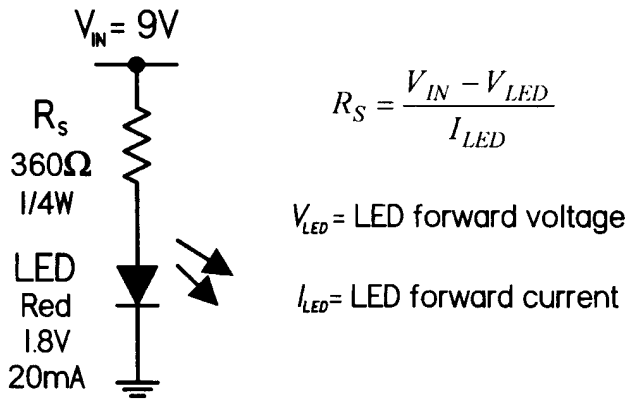


## LEDs in Series

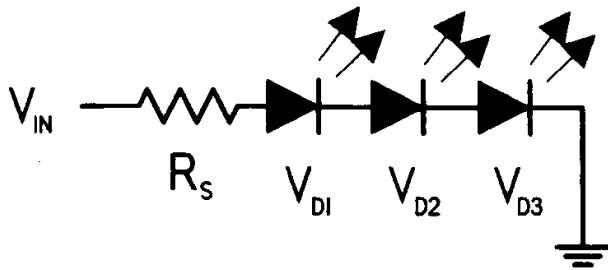


$$R_S = \frac{V_{IN} - (V_{D1} + V_{D2} + V_{D3})}{I_{D,max}}$$

## LEDs in Parallel

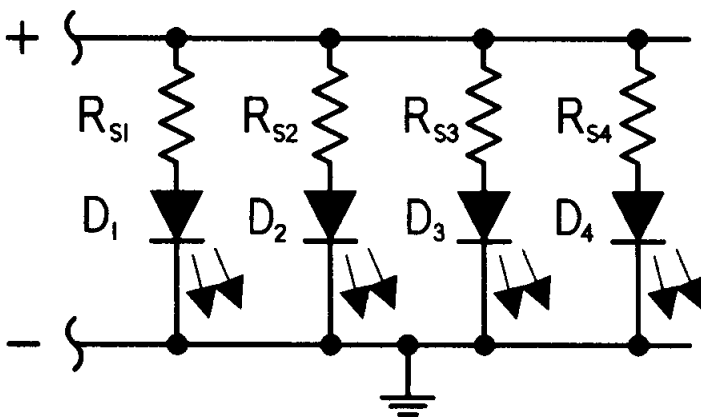


Reference: Scherz, Practical Electronics for Inventors, 2nd & 3rd Editions

## AC-DC Polarity Indicator

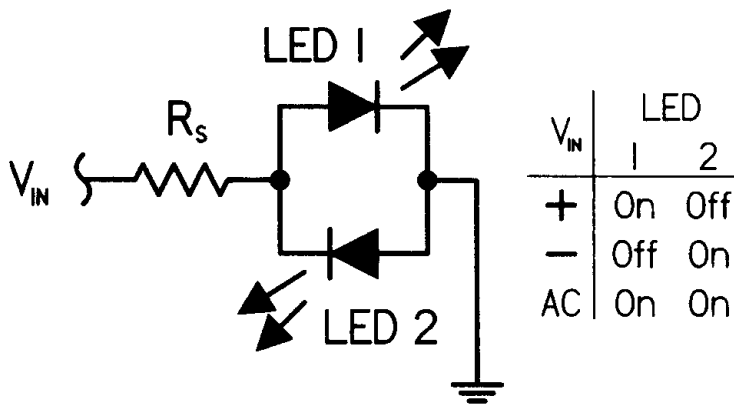


## Voltage-Level Indicator

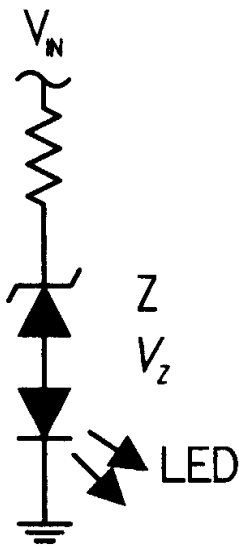

$$R_S = \frac{V_{In} - [V_Z + V_{LED}]}{I_{LED}}$$

$$V_{In(\text{Minimum})} = R_S I_{LED} + V_Z + V_{LED}$$


## Driving LEDs from 120VAC

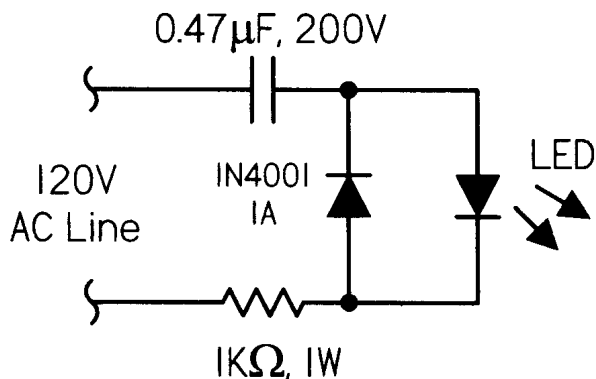


Reference: Scherz, Practical Electronics for Inventors, 2nd & 3rd Editions

### Voltage Dropper



DC application

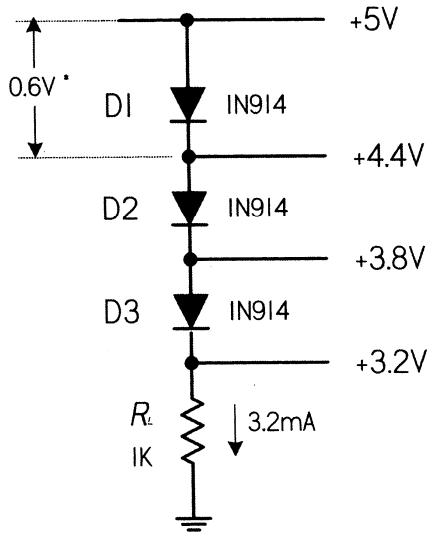

### Voltage Regulator

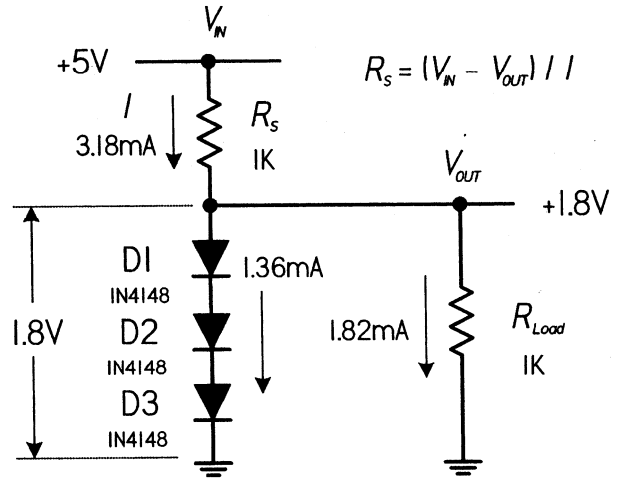

### Light-Sensitive Voltage Divider

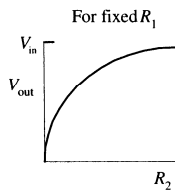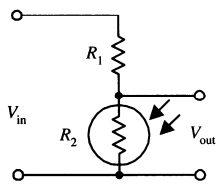

$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

As the intensity of light increases, the resistance of the photoresistor decreases, so  $V_{out}$  in the top circuit gets smaller as more light hits it, whereas  $V_{out}$  in the lower circuit gets larger.

