

Diode Circuits

Example

Calculate V_0

$$V = 0.7 + I_D R_1 + 0.7 + I_D R_2$$

$$V - 0.7 - 0.7 = I_D(R_1 + R_2)$$

$$I_D = [V - (0.7 + 0.7)] / (R_1 + R_2)$$

$$I_D = 14.6 / (2000 + 1000)$$

$$I_D = 4.9 \text{ mA}$$


$$V_0 = 0.7 + I_D R_2$$

$$V_0 = 0.7 + 0.0049 \times 1000 = 0.7 + 4.9 = 5.6 \text{ V}$$

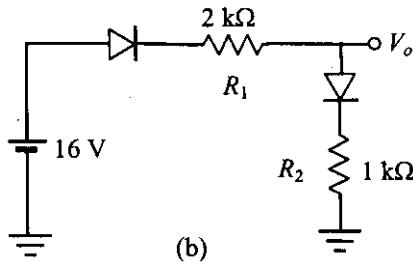Exercise

Calculate V_0 for $V = 15 \text{ V}$, $R_1 = 2200 \Omega$, $R_2 = 3300 \Omega$

$$\text{Answer: } I_D = 2.5 \text{ mA} \quad V_0 = 8.9 \text{ V}$$



Example

Calculate V_0

$$+15 = 0.7 + I_D R_1 + 0.7 + I_D R_2 - 5$$

$$20 - 0.7 - 0.7 = I_D(R_1 + R_2)$$

$$I_D = 18.6 / (R_1 + R_2)$$

$$I_D = 18.6 / (2200 + 3300)$$

$$I_D = 3.38 \text{ mA}$$



$$V_0 = 0.7 + I_D R_2 - 5.0$$

$$V_0 = 0.7 + 0.00338 \times 3300 - 5.0 = 0.7 + 11.2 - 5.0 = 6.9 \text{ V}$$

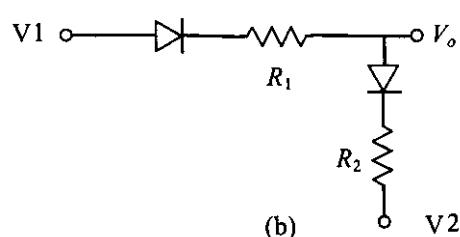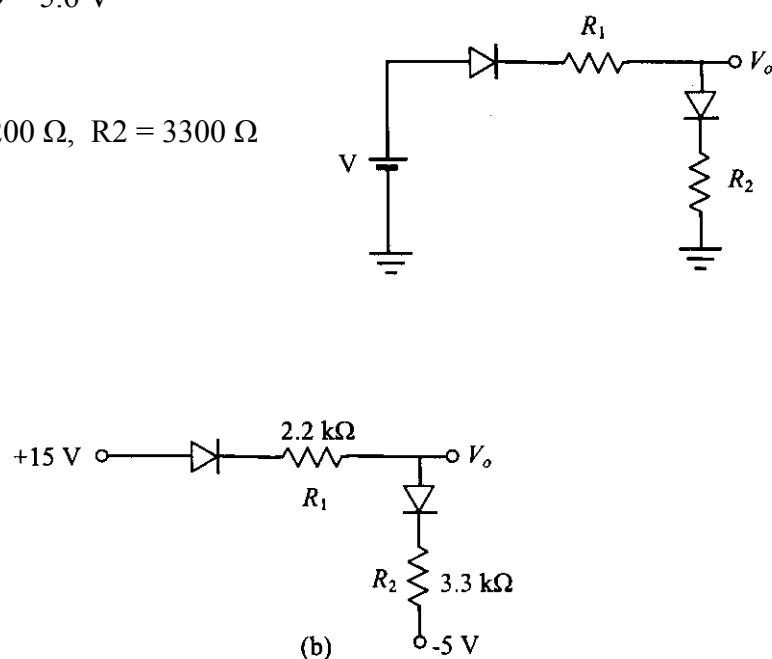Exercise

Calculate V_0 for $V1 = +10 \text{ V}$, $V2 = -5 \text{ V}$
 $R1 = 1100 \Omega$, $R2 = 2200 \Omega$

$$\text{Answer: } I_D = 4.1 \text{ mA} \quad V_0 = 4.8 \text{ V}$$



Diode Circuits - continued

Example (Refer to the Diode Circuit Lecture Notes)

Calculate the Current I_D

1. Remove Diode (Replace by V_{TH})

$$\text{For Voltage Divider } V_{TH} = V [R_2 / (R_1 + R_2)]$$

$$V_{TH} = 16 [4700 / (5100 + 4700)] = 7.67 \text{ V}$$

2. Short V_{source} (R_1 in parallel with R_2)

$$R_{EQ} = (R_1 \times R_2) / (R_1 + R_2)$$

$$R_{EQ} = (5100 \times 4700) / (5100 + 4700) = 2446 \Omega$$

3. Redraw with V_{TH} , R_{EQ} , Diode

$$V_{TH} = I_D R_{EQ} + V_D \quad I_D = (V_{TH} - V_D) / R_{EQ}$$

$$I_D = (7.67 - 0.7) / 2446 = 2.85 \text{ mA}$$

Alternative Solution Method

$$V_{R2} = V_D = 0.7 \text{ V}$$

$$I_{R2} = V_{R2} / R_2 = 0.7 / 4700 = 0.15 \text{ mA}$$

$$I_{R1} = (V - V_{R2}) / R_1 = (16.0 - 0.7) / 5100 = 3.0 \text{ mA}$$


$$I_{Total} = I_{R1}$$

$$I_D = I_{Total} - I_{R2} = 3.00 - 0.15 = 2.85 \text{ mA}$$

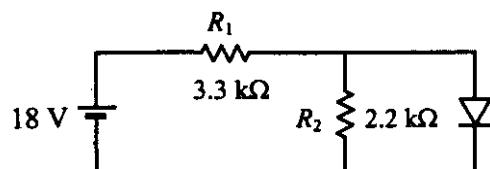Exercise

Calculate the Current I_D

$$\text{Answer: } I_D = 4.9 \text{ mA} \quad V_D = 0.7 \text{ V}$$



Zener Diodes


Note: Zener diodes operate in the reverse biased mode.

Example ($V = 12 \text{ V}$, $R = 1000 \Omega$, $V_Z = 3.3 \text{ V}$)

$$V = I_Z R + V_Z$$

$$12 = I_Z \times 1000 + 3.3$$
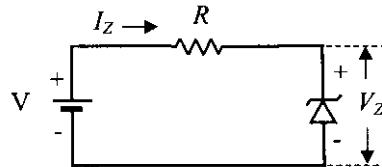
$$I_Z = (12.0 - 3.3) / 1000 = 8.7 \text{ mA}$$



If $V_{\text{Source}} > V_Z$ then V_0 maintained at V_Z , else $V_0 = 0$


Example (Refer to the Diode Circuit Notes and Zener Diode Lecture Notes)

For $V_Z = 5.1 \text{ V}$, Calculate I_{Total} and I_{R2} and I_Z

1. Calculate V_{TH}

$$V_{\text{TH}} = 20 (3300 / (1100 + 3300))$$

$$V_{\text{TH}} = 15 \text{ V}$$

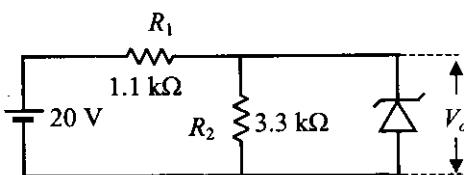

2. Calculate R_{EQ}

$$R_{\text{EQ}} = (1100 \times 3300) / (1100 + 3300)$$

$$R_{\text{EQ}} = 825 \Omega$$

3. Calculate I_{Total} and I_{R2} and I_Z

$$V_{\text{TH}} = I_{\text{Total}} R_{\text{EQ}} + V_Z$$

$$I_Z = (V_{\text{TH}} - V_Z) / R_{\text{EQ}}$$

$$I_Z = (15 - 5.1) / 825 = 12 \text{ mA}$$

$$I_{R2} = V_{R2} / R_2 = V_D / R_2 = 5.1 / 3300 = 1.55 \text{ mA}$$

$$I_{\text{Total}} = I_Z + I_2 = 12 + 1.6 = 13.55 \text{ mA}$$

Alternative Solution Method

$$V_{R2} = V_Z = 5.1 \text{ V}$$

$$I_{R2} = V_{R2} / R_2 = 5.1 / 3300 = 1.55 \text{ mA}$$

$$I_{R1} = (V - V_{R2}) / R_1 = (20.0 - 5.1) / 1100 = 13.55 \text{ mA}$$

$$I_{\text{Total}} = I_{R1} = 13.55 \text{ mA}$$

$$I_Z = I_{\text{Total}} - I_{R2} = 13.55 - 1.55 = 12 \text{ mA}$$

Exercise


For $V = 21$, $R_1 = 1000$, $R_2 = 2000$, $V_Z = 7.5 \text{ V}$

Calculate I_Z and I_{R2} and I_{Total}

Answers:

$$V_{\text{TH}} = 14 \text{ V}, \quad R_{\text{EQ}} = 666 \Omega, \quad V_0 = V_Z = 7.5 \text{ V}$$
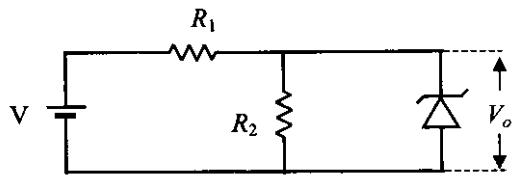
$$I_Z = 9.75 \text{ mA}, \quad I_{R2} = 3.75, \quad I_{\text{Total}} = 13.5 \text{ mA}$$



Ideal Transformer Relations (Equations)

Definitions:

Primary Winding (input - subscript 1)

Secondary Winding (output - subscript 2)

Turns Ratio = n_1 / n_2 (number of turns on primary winding / number of turns on secondary winding)

Voltage Ratio: $V_1 / V_2 = n_1 / n_2$ (Directly Proportional)

Current Ratio: $I_1 / I_2 = n_2 / n_1$ (Inversely Proportional)

Power Ratio: 1 to 1 (Power Out = Power In) Ideal

Power Out = $e \times$ Power In where e is the Efficiency Factor ($e < 1$)

Impedance Ratio: $Z_1 / Z_2 = (n_1 / n_2)^2$

For additional information, refer to



Practical Electronics for Inventors, 3ed & 4ed, pp 374 - 396.

Transformer Problems and Questions

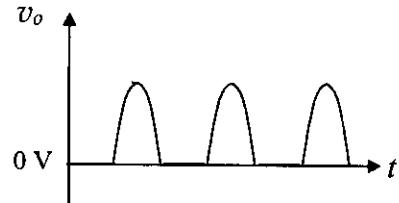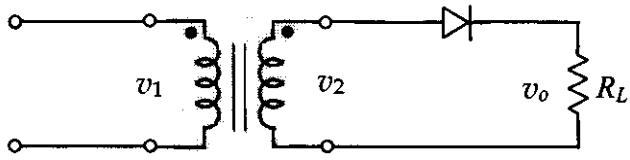1. Given an ideal transformer with primary turns = 9600 and secondary turns = 480, assume 100% efficiency. For input voltage = 120 VAC and output impedance = 16 ohms;
 - a. Calculate output voltage
 - b. Calculate output current
 - c. Calculate output power
 - b. Calculate input current
 - c. Calculate input power
 - b. Calculate input impedance
2. Determine the turns ratio for an impedance matching transformer where the first stage input impedance is 50 ohms and the second stage output impedance is 8 ohms.

Half-Wave & Full Wave Rectifiers, Filtering, Regulated Power Supply

Half-Wave Rectifier Equivalent DC Output Voltage



Example

Given:

$$v_{\text{in(RMS)}} = 110 \text{ V (60 HZ)}$$

Turns Ratio 10:1

Find: $V_{\text{out(DC Effective)}}$

$$v_{\text{in(Peak)}} = 1.414 \quad v_{\text{in(RMS)}} = 1.414 \times 110 = 155.5 \text{ V}$$

$$v_{\text{out(Peak)}} = 1/10 \quad v_{\text{in(Peak)}} = 1/10 \times 155.5 = 15.6 \text{ V}$$

$$V_{\text{Diode}} = 15.6 - 0.7 = 14.9 \text{ V}$$

$$V_{\text{out(DC Effective)}} = 0.318 \quad V_{\text{Diode}} = 0.318 \times 14.9 \approx 4.7 \text{ VDC}$$

Exercise #1

Given: $v_{\text{in(RMS)}} = 110 \text{ V (60 HZ)}$ Turns Ratio 5:1

Find: $V_{\text{out(DC Effective)}}$

Answer: 9.7 VDC



Exercise #2

Given: $v_{\text{in(RMS)}} = 120 \text{ V (60 HZ)}$ Turns Ratio 5:1

Find: $V_{\text{out(DC Effective)}}$

Answer: 10.6 VDC

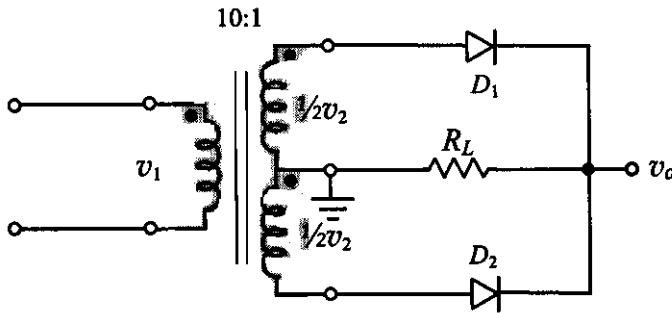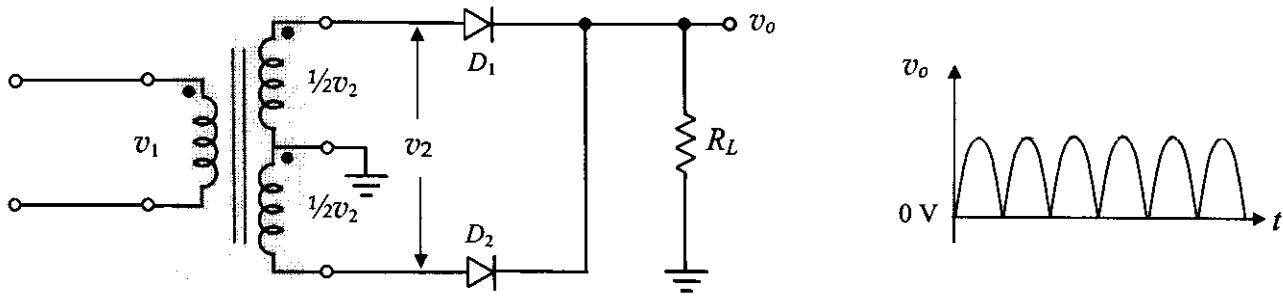Full-Wave Center-Tapped Rectifier Equivalent DC Output Voltage



Example

Given:

$$v_{\text{in(RMS)}} = 110 \text{ V (60 Hz)}$$

Turns Ratio 10:1

Find: $V_{\text{out(DC Effective)}}$

$$v_{\text{in(Peak Center)}} = 1.414 \text{ } v_{\text{in(RMS)}} = 1.414 \times 110 = 155.5 \text{ V}$$

$$v_{\text{out(Peak)}} = (1/2)(1/10) v_{\text{in(Peak)}} = 1/20 \times 155.5 = 7.8 \text{ V}$$

$$v_{\text{Diode}} = 7.8 - 0.7 = 7.1 \text{ V}$$

$$V_{\text{out(DC Effective)}} = 0.636 v_{\text{Diode}} = 0.636 \times 7.1 \approx 4.5 \text{ VDC}$$

Exercise #1

Given: $v_{\text{in(RMS)}} = 110 \text{ V (60 Hz)}$ Turns Ratio 5:1

Find: $V_{\text{out(DC Effective)}}$

Answer: 9.5 VDC


Exercise #2

Given: $v_{\text{in(RMS)}} = 120 \text{ V (60 Hz)}$ Turns Ratio 5:1

Find: $V_{\text{out(DC Effective)}}$

Answer: 10.4 VDC

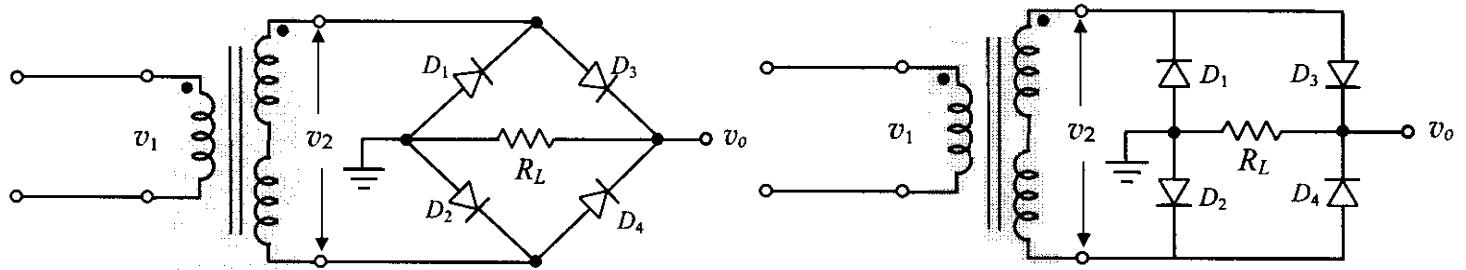Full-Wave Bridge Rectifier Equivalent DC Output Voltage



Example

Given:

$$v_{\text{in(RMS)}} = 110 \text{ V (60 Hz)}$$

Turns Ratio 10:1

Find: $V_{\text{out(DC Effective)}}$

$$v_{\text{in(Peak)}} = 1.414 \quad v_{\text{in(RMS)}} = 1.414 \times 110 = 155.5 \text{ V}$$

$$v_{\text{out(Peak)}} = 1/10 \quad v_{\text{in(Peak)}} = 1/10 \times 155.5 = 15.6 \text{ V}$$

$$v_{\text{Diode}} = 15.6 - 2(0.7) = 14.2 \text{ V}$$

$$V_{\text{out(DC Effective)}} = 0.636 \quad v_{\text{Diode}} = 0.636 \times 14.2 \approx 9 \text{ VDC}$$

Exercise #1

Given: $v_{\text{in(RMS)}} = 110 \text{ V (60 Hz)}$ Turns Ratio 5:1

Find: $V_{\text{out(DC Effective)}}$

Answer: 18.9 VDC



Exercise #2

Given: $v_{\text{in(RMS)}} = 120 \text{ V (60 Hz)}$ Turns Ratio 5:1

Find: $V_{\text{out(DC Effective)}}$

Answer: 20.7 VDC

Filtering

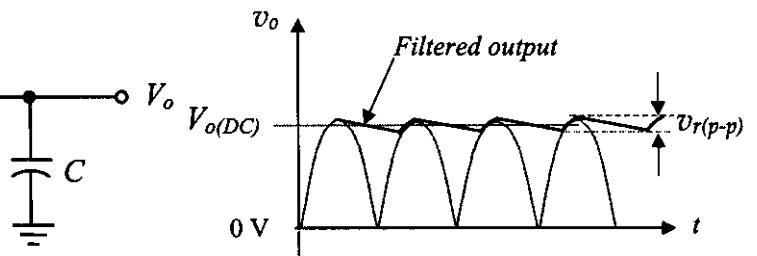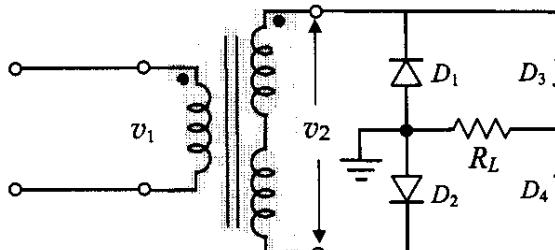

$$V_{\text{ripple(peak- peak)}} = I_{\text{out(DC)}} / 2fC$$

$$I_{\text{out(DC)}} = V_{\text{out(DC)}} / R_{\text{Load}}$$

Two Steps

1. Assume $V_{\text{out(DC)}}$ (Without filtering, i.e., use peak of the rectified wave, NOT the DC average value.)
2. Solve for $I_{\text{out(DC)}}$ and $V_{\text{ripple(peak- peak)}}$
3. Recalculate $V_{\text{out(DC)}}$ Load = $V_{\text{out(DC)}}$ (without filtering) - $[V_{\text{ripple(peak- peak)}}] / 2$

Example

Given:

$$v_{\text{in(RMS)}} = 110 \text{ V (60 HZ)}$$

Turns Ratio 10:1

$$R_{\text{Load}} = 100 \Omega \quad C = 1000 \mu\text{F} \quad f = 60 \text{ Hz}$$

Find: $V_{\text{out(DC)}}$ Load

From Full-Wave Bridge Rectifier (from Example page 3, above) $V_{\text{out(DC)}} \text{ (without filtering)} = 14.2 \text{ VDC}$

$$I_{\text{out(DC)}} = V_{\text{out(DC)}} / R_{\text{Load}} = 14.2 / 100 = 0.142 \text{ A} = 142 \text{ mA}$$

$$V_{\text{ripple(peak- peak)}} = I_{\text{out(DC)}} / 2fC = 0.142 / (2 \times 60 \times 1000 \times 10^{-6}) = 1.18 \text{ V}$$

$$V_{\text{out(DC)}} \text{ Load} = V_{\text{out(DC)}} \text{ (without filtering)} - [V_{\text{ripple(peak- peak)}}] / 2 = 14.2 - (1.18) / 2 = 13.6 \text{ VDC}$$

Exercise

Given:

$$v_{\text{in(RMS)}} = 120 \text{ V (60 HZ)} \quad \text{Turns Ratio 5:1}$$


$$R_{\text{Load}} = 240 \Omega \quad C = 470 \mu\text{F} \quad f = 60 \text{ Hz}$$

$$V_{\text{out(DC)}} \text{ (without filtering)} = 32.5 \text{ VDC} \text{ (from Problem, page 3, above. Note } 32.5 \text{ not } 32.5 \times .636 = 20.7)$$

Find: $V_{\text{out(DC)}}$ Load

$$\text{Answer: } I_{\text{out(DC)}} = 136 \text{ mA} \quad V_{\text{ripple(peak- peak)}} = 2.4 \text{ V} \quad V_{\text{out(DC)}} \text{ Load} = 31.3 \text{ VDC}$$

Regulated Power Supply

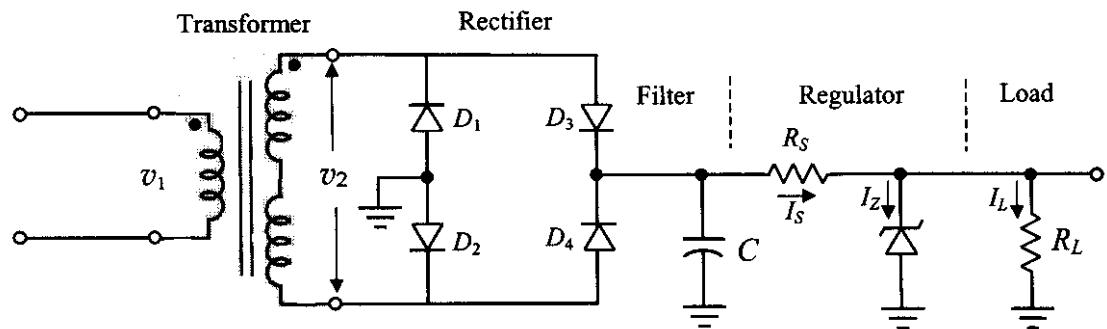

Scanned Images: Electronic Devices, Ali Aminian & Marian Kazimierczuk, Pearson-Prentice Hall, 2004