

Review materials include:

## Reading Assignments & Homework

### Topics

Zener Diodes

Rectification

Transformer Calculations (Turns, Current, Voltage, Impedance, Power, Phase Dots)

Power Supplies ( Calculate power supply current, voltage, component values)

### Course Notes

*Diode & Zener Diode Circuits, Examples, and Problems*

*Ideal Transformers*

*Power Supplies (Rectifiers)*

Diode Specifications: Practical Electronics for Inventors, 3ed & 4ed

Simple Diodes                      Table 4.1, p 411

LED Specifications:              Table 5.1, pp 503 - 504

Zener Diode Specifications:    Table 4.2, p 422

### Review Problems

*Additional Review Problems (Zeners, LED Applications) - See pages 2 - 4.*

Types of possible exam questions and problems:

Calculate Zener circuit current and voltage values (  $V_{Zener}$ ,  $I_{Zener}$ ,  $V_{Load}$ ,  $I_{Load}$ ,  $I_{Total}$  )


Calculate current limiting resistor values for simple LED circuits

Calculate minimum input voltage to activate LED voltage-level indicator circuits

Apply Transformer Equations (Turns, Input/Output Voltages, Currents, Power)

Solve Power Supply Design Problems (Output Voltages)

1. Given:

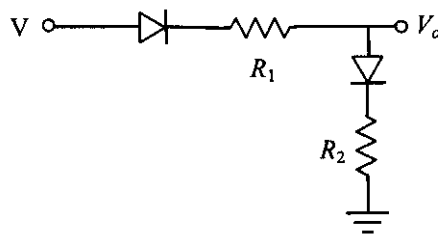
 $D_1$  and  $D_2$  silicon diodes $V = 18$  volts $R_1 = 1800 \Omega$  $R_2 = 470 \Omega$ 

Calculate:

Diode Currents

 $V_o$ 

2. Given:

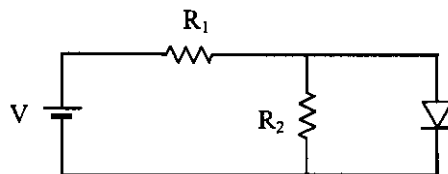
 $D_1$  silicon diode $V = 14$  volts $R_1 = 220 \Omega$  $R_2 = 750 \Omega$ 

Calculate:

Diode Current

 $V_{R1}$  $V_{R2}$  $I_{R1}$  $I_{R2}$ 


3. Given:

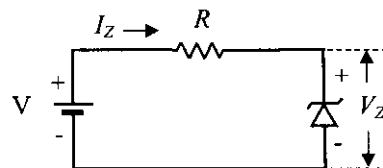 $V = 18$  volts $V_Z = 15.1$  volts $R = 620 \Omega$ 

Calculate:

 $I_Z$  $V_R$ 

4. Given:

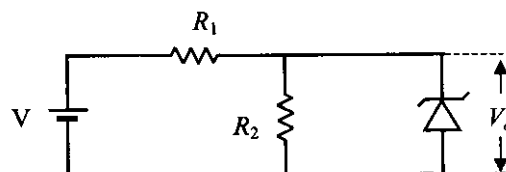
 $V = 24$  volts $V_Z = 3.3$  volts $R_1 = 680 \Omega$  $R_2 = 200 \Omega$ 

Calculate:

 $V_o$  $I_{R1}$  $I_{R2}$  $I_Z$  $I_{Total}$

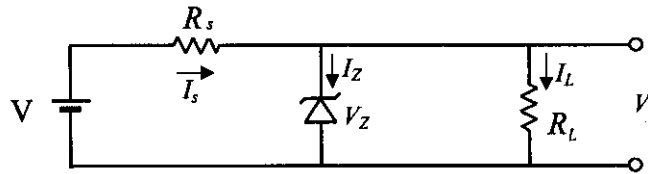5. Given:


- $V = 9$  volts
- $V_Z = 3.3$  volts
- $R_S = 180 \Omega$
- $R_L = 220 \Omega$



Calculate:

- $V_o$
- $I_L$
- $I_Z$
- $I_S$


6. Current Limiting Resistor

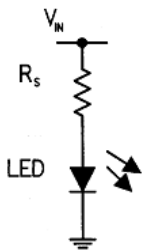

Calculate  $R_s$  for

- $V_{in} = 3$  V
- $V_{LED} = 1.2$  V
- $I_{LED} = 15$  mA


7. Voltage Indicator

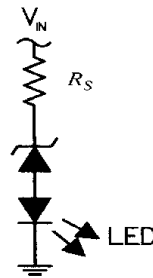

Calculate Minimum Input Voltage

- $R_s = 470$
- $V_{Zener} = 3.3$  V
- $V_{LED} = 1.2$  V
- $I_{LED} = 10$  mA

8. Voltage Indicator

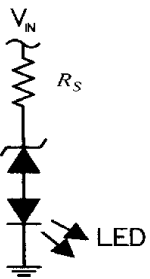

- $R_s = 220$
- $V_{LED} = 2.7$  V
- $I_{LED} = 15$  mA

Determine the required Zener Diode (i.e.,  $V_{Zener}$ ) such that the LED is lite at  $V_{in} = 11.5$  V

After determining the theoretical value for  $V_{Zener}$ , check your textbook or on-line for a real-world Zener diode value and recalculate the turn-on voltage.

Would  $R_s$  need to be increased or decreased to achieve  $V_{in} = 11.5$  goal using the real-world Zener diode?

## 1. Diode Circuit

$$\text{Diode Currents} = 7.3 \text{ mA}$$

$$V_0 = 4.1 \text{ V}$$

## 2. Diode Circuit

$$\text{Diode Current} = 59.5 \text{ mA}$$

$$V_{R1} = 13.3 \text{ V}$$

$$V_{R2} = 0.7 \text{ V}$$

$$I_{R1} = 60.4 \text{ mA}$$

$$I_{R2} = 0.93 \text{ mA}$$

## 3. Zener Circuit

$$I_Z = 4.7 \text{ mA}$$

$$V_R = 2.9 \text{ V}$$

## 4. Zener Circuit

$$V_o = 3.3 \text{ V}$$

$$I_{R1} = 30.4 \text{ mA}$$

$$I_{R2} = 16.5 \text{ mA}$$

$$I_Z = 13.9 \text{ mA}$$

$$I_{\text{Total}} = 30.4 \text{ mA}$$

## 5. Zener Circuit

$$V_o = 3.3 \text{ V}$$

$$I_L = 15 \text{ mA}$$

$$I_Z = 16.7 \text{ mA}$$

$$I_s = 31.7 \text{ mA}$$

## 6. Current Limiting Resistor

$$R_s = 120 \Omega$$

## 7. LED Voltage Indicator

$$V_{\text{in}} = 9.2 \text{ V}$$

## 8. LED Voltage Indicator

$$V_{\text{Zener (theoretical)}} = 5.5 \text{ V}$$

$$V_{\text{Zener (real world)}} = 5.6 \text{ V}$$

$R_s = V_{R_s}$  would need to be adjusted from  $(0.15 \times 220 - 3.3)$  to 3.2 volts;

so adjusted  $R_s = 3.2 / 0.015 = 213 \Omega$ .