

Alternating Current

Capacitive & Inductive Reactance and Complex Impedance

RC & RL Circuit Analyses (DC Transients, Time Constants, Steady State)

RC & RL Passive Filters

Electrical Theory (Alternating Current)Ohm's Law for AC $I_{RMS} = V_{RMS} / Z$ where Z is the Complex Impedance

$$|Z| = [(R^2 + (XL - XC)^2)^{1/2}$$

$$\theta = \tan^{-1} [(XL - XC) / R]$$

$$\text{Power Factor } \cos \theta = R / Z$$

$$\text{Joule's Law Average Power} = \frac{1}{2} V_{\text{peak}} I_{\text{peak}} \cos \theta = V_{RMS} I_{RMS} \cos \theta \quad \text{Watts}$$

$$\text{Purely Resistive Element } (\theta = 0, \cos \theta = 1) \text{ Average Power} = \frac{1}{2} V_{\text{peak}} I_{\text{peak}} = V_{RMS} I_{RMS} \quad (\text{Watts})$$

ELI the ICE man	<u>Component</u>	<u>Voltage / Current</u>
	Resistor	In Phase
	Capacitor	Lags
	Inductor	Leads

Capacitive & Inductive Reactance and Complex Impedance

$$\omega = 2\pi f \quad f = 0.159\omega$$

$$\text{Capacitive Reactance } X_C = 1 / \omega C = 1 / (2\pi f C) = 0.159 / f C$$

$$\text{Inductive Reactance } X_L = \omega L = 2\pi f L$$

Complex Impedance

$$\text{R in series with series CL } Z = R + j(2\pi f L - 1/(2\pi f C)) \quad \text{Impedance is a minimum at resonance}$$

$$\text{R in series with parallel CL } Z = R + j(2\pi f L / (1 - (2\pi f)^2 LC)) \quad \text{Impedance is a maximum at resonance}$$

Time Constants

$$\text{RC Circuit Time Constant} = R C$$

$$\text{RL Circuit Time Constant} = L / R$$

Equations and Relationships

Inductive Reactance $X_L = 2\pi f L$

Capacitive Reactance $X_C = \frac{1}{2\pi f C}$


	RC Circuit	RL Circuit	RCL Circuit
Cut-off Frequency Resonant Frequency	$f_0 = \frac{1}{2\pi RC}$	$f_0 = \frac{1}{2\pi L/R}$	$f_0 = \frac{1}{2\pi\sqrt{LC}}$
Time Constant	$t = RC$	$t = L/R$	$t = \frac{R\sqrt{C/L}}{2}$

RCL Series Impedance $Z = \sqrt{R^2 + (X_L - X_C)^2}$

R&CL Parallel Impedance $Z = \sqrt{R^2 + \left(\frac{X_L X_C}{X_L - X_C}\right)^2}$


RCL Parallel Impedance $Z = \frac{R X_L X_C}{X_L X_C - R(X_L - X_C)}$

Common Configuration


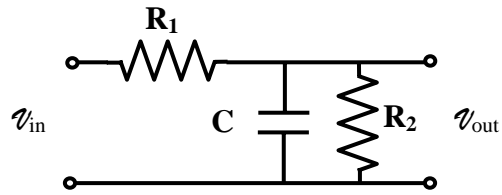


Notes:

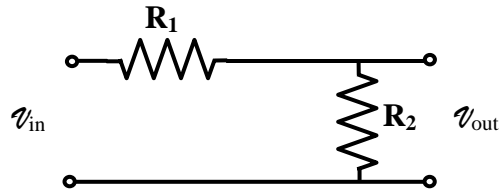When $\omega = 0$, $X_C \rightarrow \infty$, i.e., C appears as an open circuit, so that $V_{out} = \frac{R_2}{R_1 + R_2}$



When $\omega \gg 0$, $X_C = 0$, i.e., C appears as a short circuit, so that $V_{out} = 0$

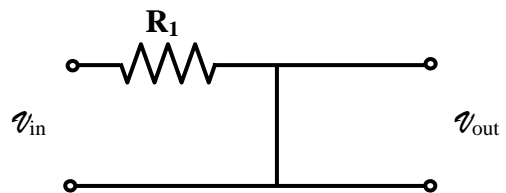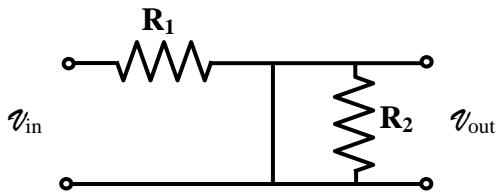


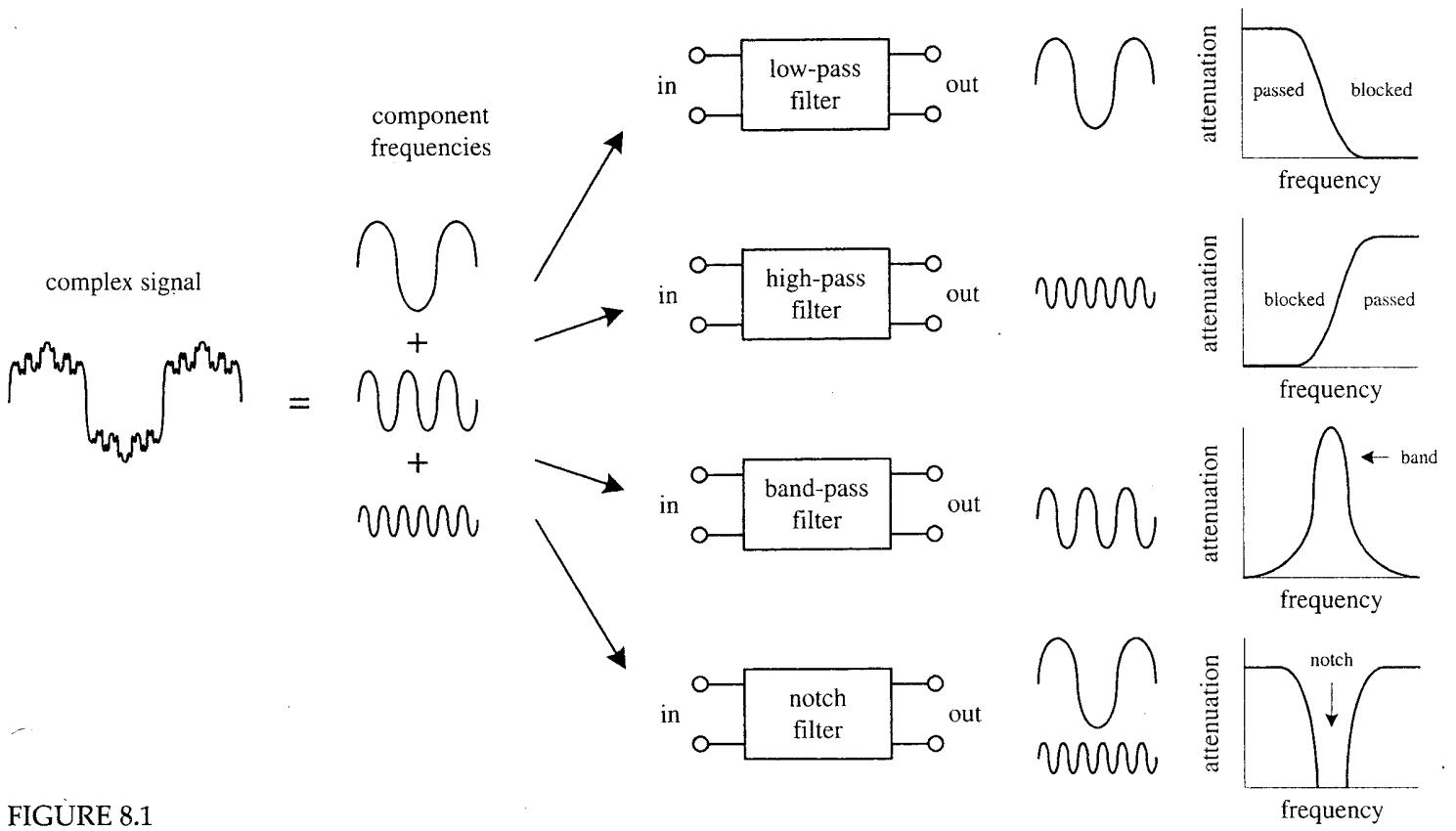
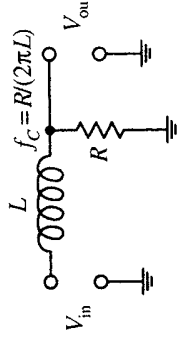


FIGURE 8.1

Low-pass filters

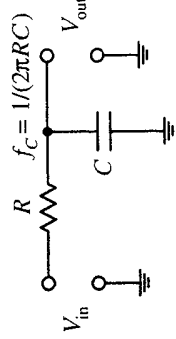

High-pass filters


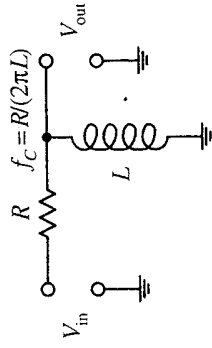
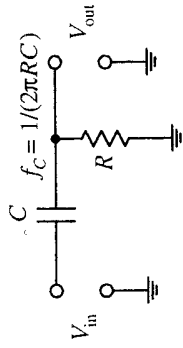



FIGURE 8.3

Bandpass filter

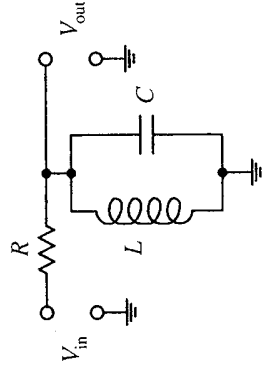

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Notch filters

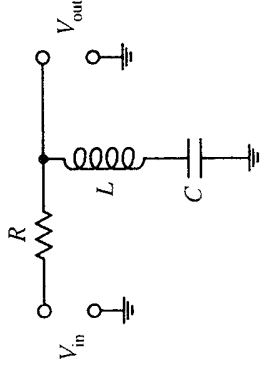

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

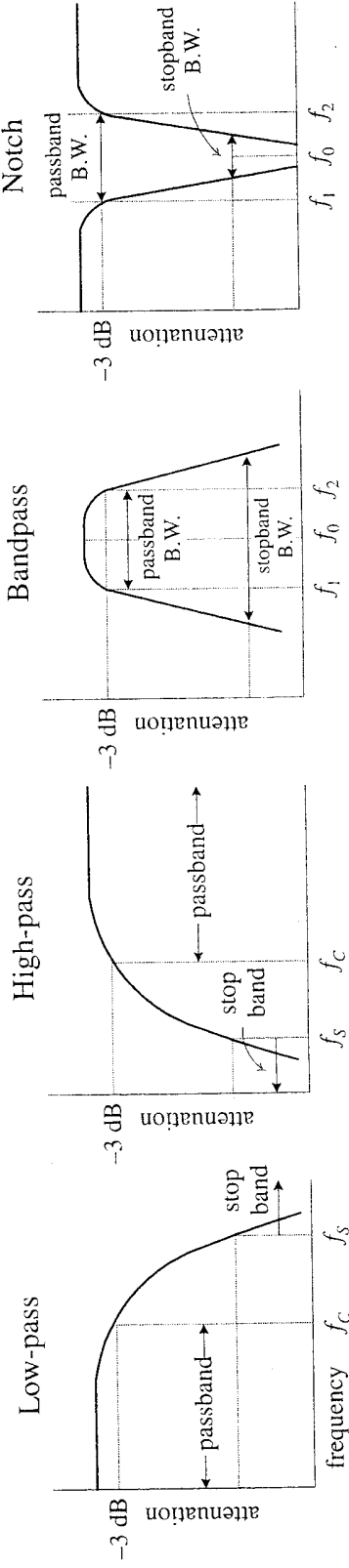


FIGURE 8.2