

## Test Seven Topics:

AC Reactance, Impedance, Power Factor

RCL Circuit Analysis

Calculate Series RCL Impedance

Calculate Series RCL Resonance Frequency

Determine whether Series RCL circuit at resonance has maximum or minimum current

Calculate Parallel RCL Impedance

Calculate Parallel RCL Resonance Frequency

Determine whether Parallel RCL circuit at resonance has maximum or minimum current

RCL Passive Filters

Using a schematic of a RC or RL circuit, determine if the circuit depicts a low pass filter or a high pass filter

Calculate the time constant

Calculate the filter's cut-off frequency

Sketch the  $V_{out}/V_{in}$  Curve

Label both axes, the horizontal asymptote, the cut-off frequency, and the  $\frac{1}{2}$  power point

## Review materials include:

Reading Assignments & Homework Problems

Course Notes

Additional Review Problems (Reactance, Filters)

Reactance & Filter Quizzes

## For the test, you may use:

a calculator,

two page of YOUR OWN self-generated review notes

*Note: Phones may **NOT** be used during the exam; NOT as calculators, NOT as Internet connections, NOT for resource retrieval (i.e., electronic copies of notes, files, tables, etc.), NOT for communications. If the exam proctor suspects the use of a phone during the exam, your test will be confiscated and zero points will be assigned.*

See following pages for additional reviews problems and quizzes.

Calculate Capacitive and Inductive Reactance and Complex Impedance

Calculate Series & Parallel Equivalent Impedance for Resistors, Capacitors, Inductors, Impedances

Determine Passive RC and RL Passive Filter Characteristics

1. Calculate Series & Parallel Impedance Frequency = 420 Hz.

RCL Series Configuration

$$R = 20 \Omega$$

$$C = 25 \mu\text{F}$$

$$L = 50 \text{ mH}$$

RCL Parallel Configuration

$$R = 20 \Omega$$

$$C = 25 \mu\text{F}$$

$$L = 50 \text{ mH}$$

Answers:

$$R = 20 \text{ Ohms}$$

$$X_C = 15.2 \text{ Ohms}$$

$$X_L = 131.9 \text{ Ohms}$$

RCL Series Configuration

$$Z = 20 + j 116.8$$

$$Z = 118.5 @ 80.3^\circ$$

RCL Parallel Configuration

$$Z = 8.46 - j 9.88$$

$$Z = 13.0 @ -49.4^\circ$$

2. For Figure A, calculate the circuit impedance if the excitation frequency is 1800 Hz. (Answer:  $Z = 300 + j 6428$ )

3. For Figure B, calculate the circuit impedance if the excitation frequency is 900 KHz. (Answer:  $Z = 3000 + j 186$ )

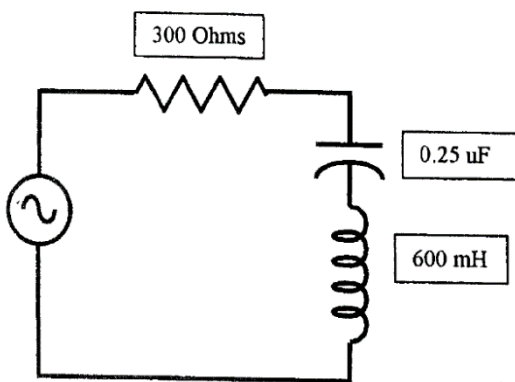


Figure A

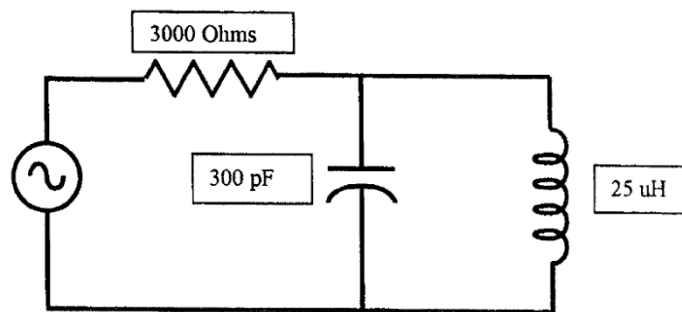


Figure B

4. Sketch RC Filter &  $V_{\text{out}}/V_{\text{in}}$  Curve

a. Calculate the cut-off frequency (half power point) if  $R = 1500 \text{ ohms}$  and  $C = 0.100 \mu\text{F}$ . (Answer  $f_0 = 1060 \text{ Hz}$ )

b. Calculate the time constant. (Answer  $t = 0.9 \text{ msec}$ )

c. Sketch the circuit for a RC low pass filter

d. Sketch the circuit for a RC high pass filter

5. Sketch RL Filter &  $V_{\text{out}}/V_{\text{in}}$  Curve

a. Calculate the cut-off frequency (half power point) if  $R = 1500 \text{ ohms}$  and  $L = 12 \text{ H}$ . (Answer  $f_0 = 20 \text{ Hz}$ )

b. Calculate the time constant. (Answer  $t = 8 \text{ msec}$ )

c. Sketch the circuit for a RL low pass filter

d. Sketch the circuit for a RL high pass filter

6. Passive Filter Recognition Quiz (see page 2).

## Passive Filter Quick Recognition Quiz

For each of the four schematics, indicate whether or not the configuration represents a *Low Pass Filter* or a *High Pass Filter*.

Hint: Consider the reactance when  $\omega = 0$ .

$$\begin{array}{lll} X_L = 0 & V_L = 0 & V_R = V_{in} \\ X_C \gg 0 & V_C = V_{in} & V_R = 0 \end{array}$$

If  $V_{out} = V_{in}$ , then since  $\omega = 0$ , passes low frequencies, hence Low Pass Filter.





If  $V_{out} = 0$ , then since  $\omega = 0$ , blocks low frequencies, hence passes only high frequencies, i.e., High Pass Filter.

Similarly: Consider the reactance when  $\omega \gg 0$ .

$$\begin{array}{lll} X_L \gg 0 & V_L = V_{in} & V_R = 0 \\ X_C = 0 & V_C = 0 & V_R = V_{in} \end{array}$$

If  $V_{out} = V_{in}$ , then since  $\omega \gg 0$ , passes high frequencies, hence High Pass Filter.

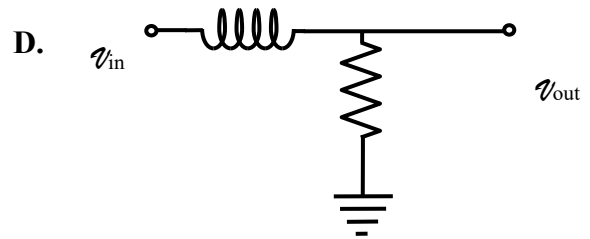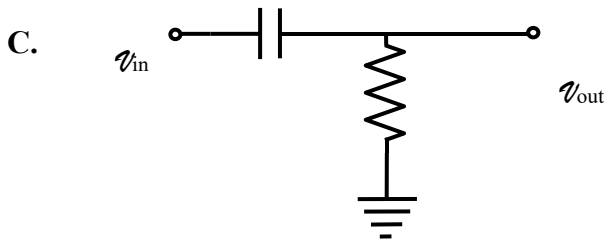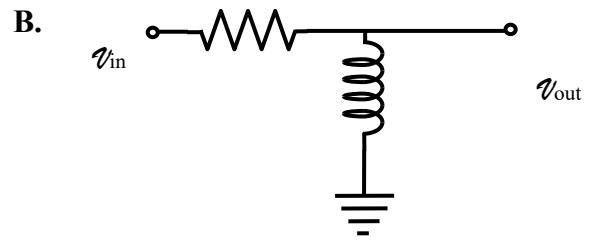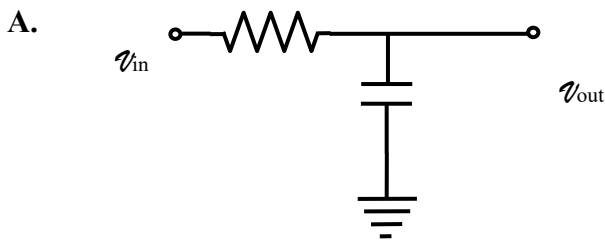If  $V_{out} = 0$ , then since  $\omega \gg 0$ , blocks high frequencies, hence passes only low frequencies, i.e., Low Pass Filter.



A. \_\_\_\_\_

B. \_\_\_\_\_

C. \_\_\_\_\_

D. \_\_\_\_\_

Answers on page 2.

## Passive Filter Quick Recognition Quiz - Answers

A. Low Pass

B. High Pass

C. High Pass

D. Low Pass