



Electrical Current Flow

Electron Flow - From excess to deficient

Conventional Current Flow

Internal to Source (Battery)

Negative to Positive

External from Source (Battery)

Positive to Negative

Voltage Drop - Across a Resistor + to -

Negative Current - Assumed Direction Reversed



Electrical Theory

Ohm's Law

$$I = V/R \text{ (DC)}$$

$$I = V/Z \text{ (AC)}$$

Series

$$R_{eq} = R_1 + R_2 + R_3$$

Parallel

$$1/R_{eq} = 1/R_1 + 1/R_2 + 1/R_3$$

Kirchoff's Law

Sum of Loop Voltages = 0

Sum of Node Currents = 0

Joule's Law

$$P = IE = I^2R \text{ (I Squared R Loss)}$$



Electrical Theory

<u>Quantity</u>	<u>Symbol</u>	<u>Unit</u>	<u>Equation</u>
Charge	Q	coulomb	$Q = \int i dt$ $Q = CV$
Current	I	ampere	$I = dQ/dt$
Voltage	V	volt	$V = dW/dQ$
Energy	W	joule	$W = \int V dQ = \int P dt$
Power	P	watt	$P = dW/dt = IV$



Equivalent Circuits

Thevenin

Two Terminal Resistor and Battery Circuit

Series Voltage Source and Equivalent Resistor

Voltage Source = Open Circuit Voltage

Equivalent Resistor = $V / \text{Short Circuit Current}$

Norton

Two Terminal Resistor and Battery Circuit

Parallel Voltage Source and Equivalent Resistor

Current Source = Short Circuit Current

Equivalent Resistor = $V / \text{Short Circuit Current}$