

Diode Characteristics

Source: James Brophy, Basic Electronics for Scientists, 5th Edition

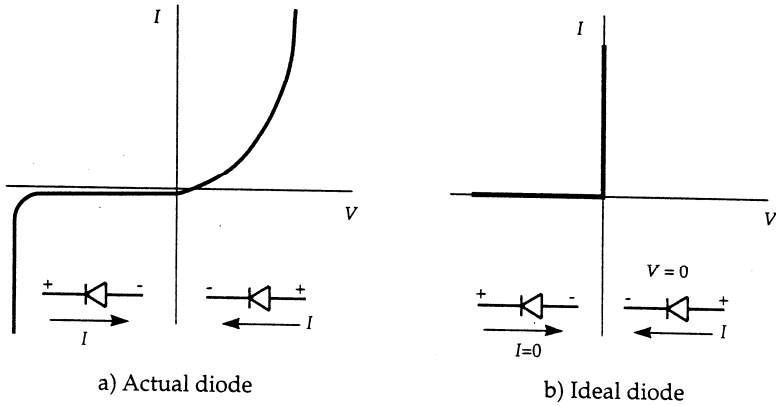


Figure 6.18 Characteristics of a diode.

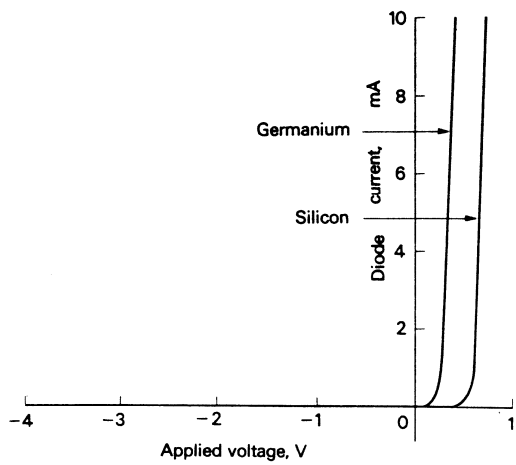


Figure 3-2 Current-voltage characteristics of germanium and silicon junction diodes.

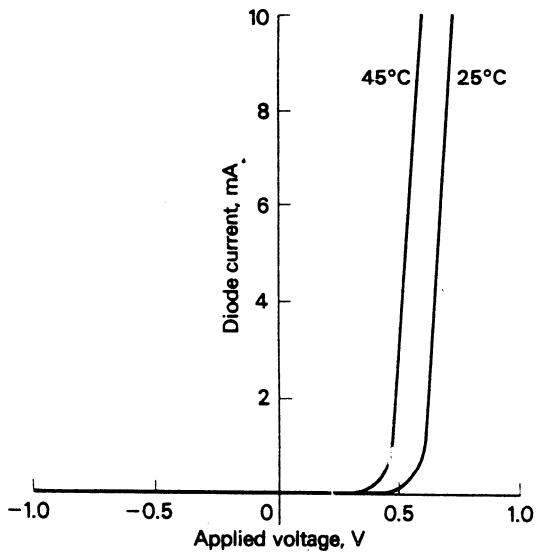


Figure 3-3 Effect of temperature on current-voltage characteristics of silicon junction diode.

Semiconductors, P-Type, and N-Type Materials

Forward and Reverse Biasing of the PN Junction

Reference: Aminian and Kazimierczuk, *Electronic Devices: A Design Approach*, 2004


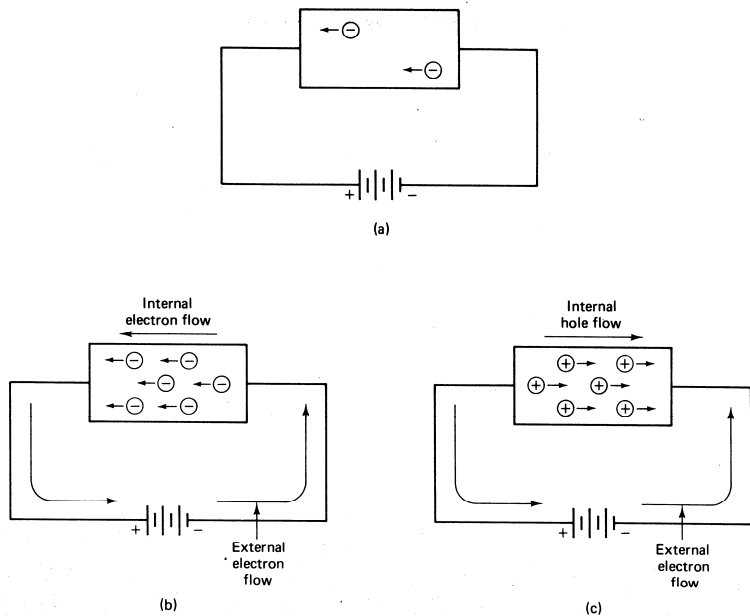


Figure 1-6 Conduction in semiconductor materials: (a) very little current flow in pure silicon; (b) electron flow in *n*-type material; (c) hole flow in *p*-type material.

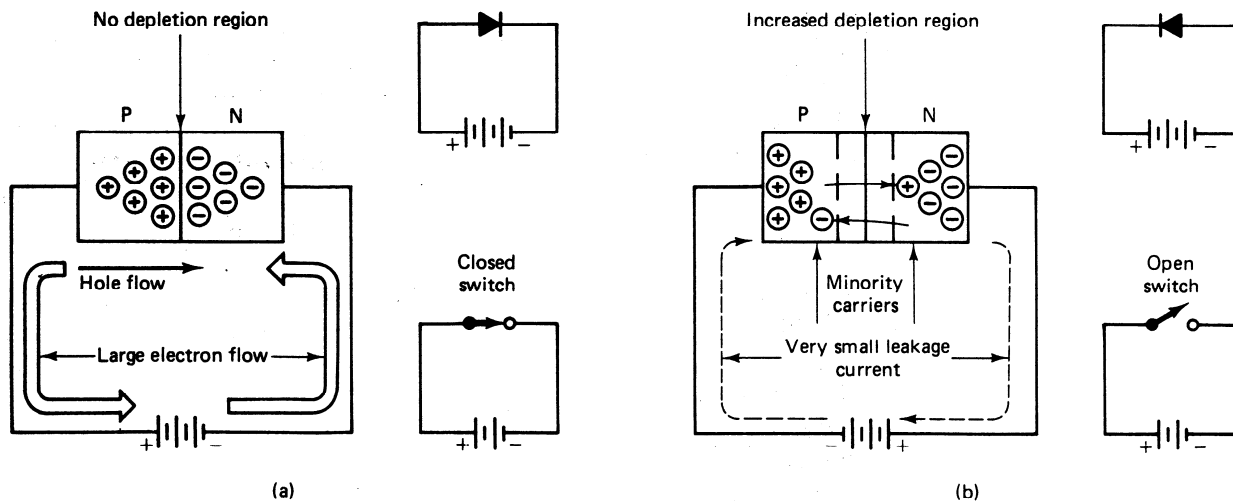

Biasing the diode: (a) forward bias; (b) reverse bias.

Forward and Reverse Biasing of the PN Junction - continued

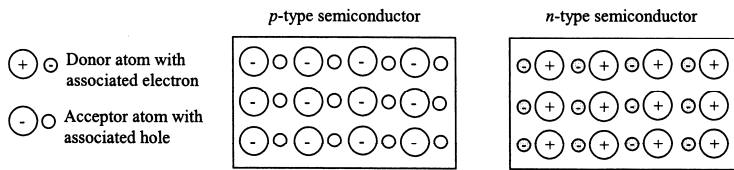


Figure 1-9: Blocks of *p*-type and *n*-type semiconductors before they are joined

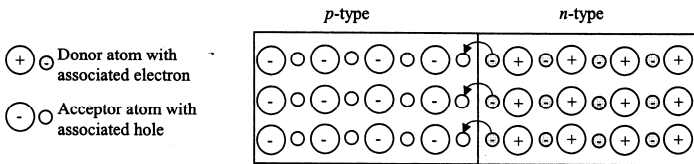


Figure 1-10: Blocks of *p*-type and *n*-type semiconductors at the instant they are joined

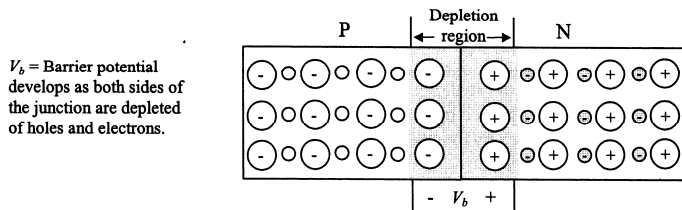


Figure 1-11: The *p-n* junction after recombination of electron-hole pairs

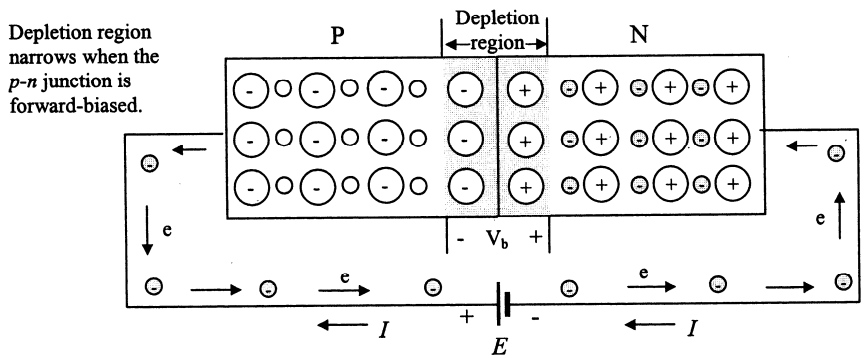


Figure 1-12: Forward biasing the *p-n* junction with an external source

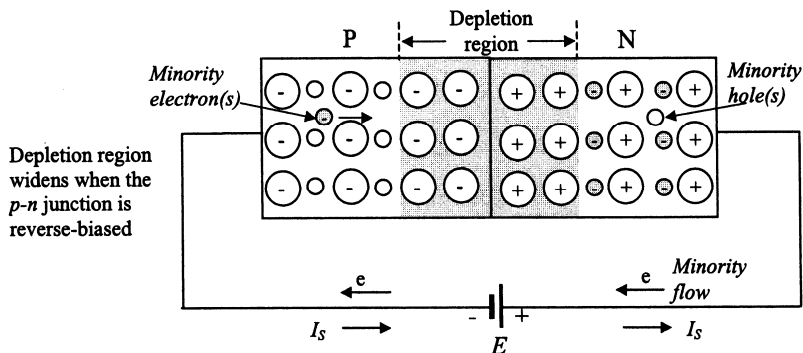


Figure 1-13: Reverse biasing the *p-n* junction with an external source

Diode Rectifiers, Clippers, and Clamps

Source: James Brophy, Basic Electronics for Scientists, 5th Edition

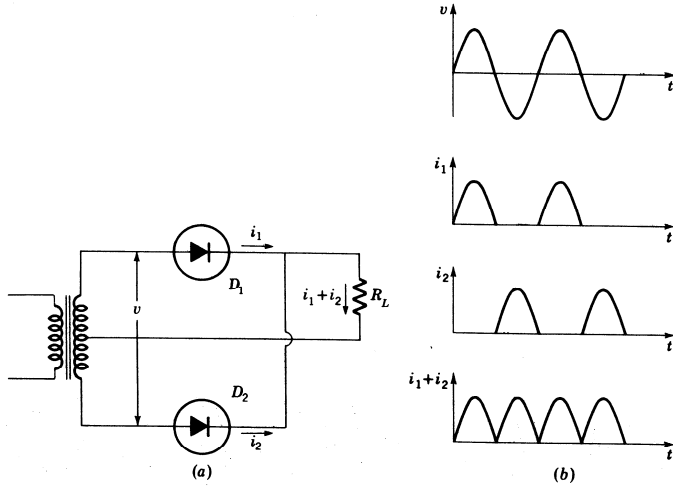


Figure 3-8 (a) Full-wave rectifier and (b) waveforms.

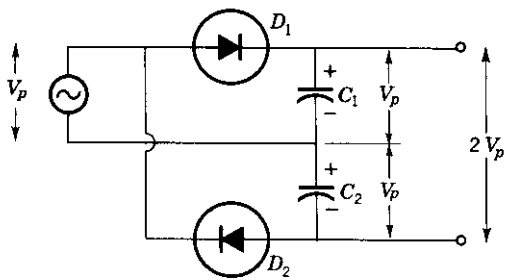


Figure 3-10 Voltage-doubler rectifier yields dc output voltage equal to twice peak input voltage.

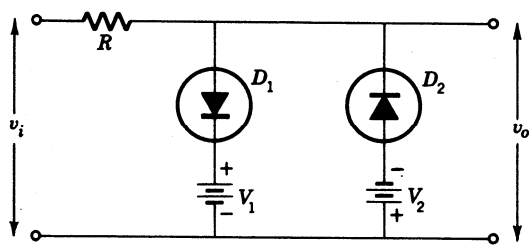


Figure 3-22 Diode clipper.

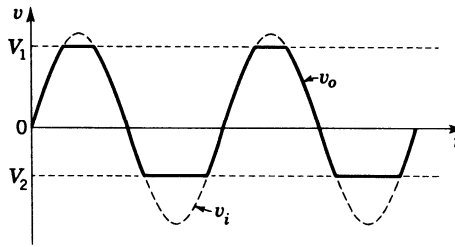


Figure 3-23 Maximum amplitudes in output waveform of diode clipper are limited to values of bias voltage.

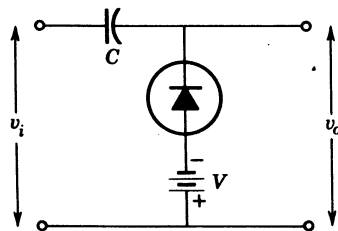


Figure 3-24 Diode clamp.

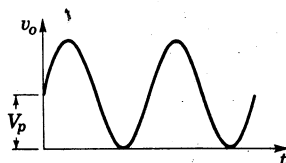


Figure 3-25 Negative peak of output waveform is clamped at zero when $V = 0$ in diode clamp circuit of Fig. 3-24.

Diode Circuits

Example

Calculate V_0

$$V = 0.7 + I_D R_1 + 0.7 + I_D R_2$$

$$V - 0.7 - 0.7 = I_D (R_1 + R_2)$$


$$I_D = [V - (0.7 + 0.7)] / (R_1 + R_2)$$

$$I_D = 14.6 / (2000 + 1000)$$

$$I_D = 4.9 \text{ mA}$$

$$V_0 = 0.7 + I_D R_2$$

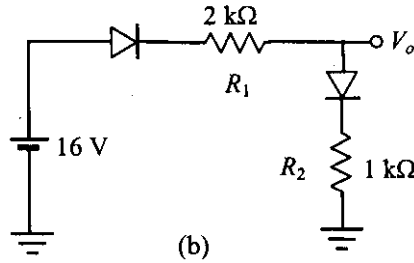
$$V_0 = 0.7 + 0.0049 \times 1000 = 0.7 + 4.9 = 5.6 \text{ V}$$



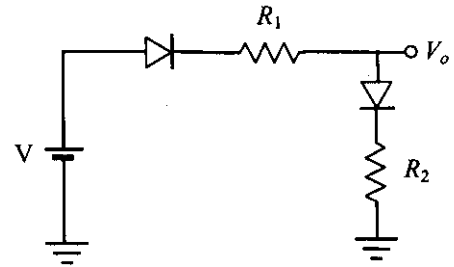Exercise

Calculate V_0 for $V = 15 \text{ V}$, $R_1 = 2200 \Omega$, $R_2 = 3300 \Omega$

Answer: $I_D = 2.5 \text{ mA}$ $V_0 = 8.9 \text{ V}$



Example

Calculate V_0

$$+15 = 0.7 + I_D R_1 + 0.7 + I_D R_2 - 5$$

$$20 - 0.7 - 0.7 = I_D (R_1 + R_2)$$


$$I_D = 18.6 / (R_1 + R_2)$$

$$I_D = 18.6 / (2200 + 3300)$$

$$I_D = 3.38 \text{ mA}$$

$$V_0 = 0.7 + I_D R_2 - 5.0$$

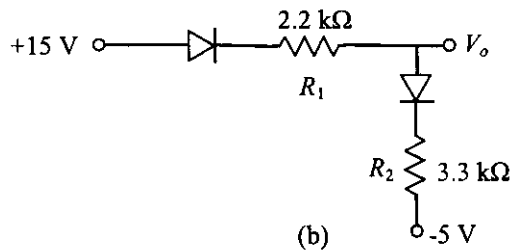
$$V_0 = 0.7 + 0.00338 \times 3300 - 5.0 = 0.7 + 11.2 - 5.0 = 6.9 \text{ V}$$



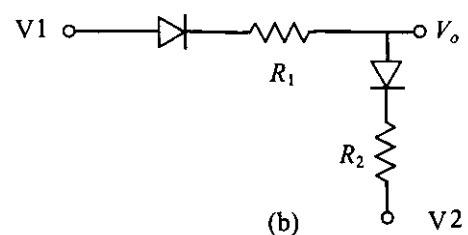Exercise

Calculate V_0 for $V_1 = +10 \text{ V}$ $V_2 = -5 \text{ V}$
 $R_1 = 1100 \Omega$ $R_2 = 2200 \Omega$

Answer: $I_D = 4.1 \text{ mA}$ $V_0 = 4.8 \text{ V}$



Diode Circuits - continued

Example (Refer to the Diode Circuit Lecture Notes)

Calculate the Current I_D

1. Remove Diode (Replace by V_{TH})

For Voltage Divider $V_{TH} = V [R_2 / (R_1 + R_2)]$

$$V_{TH} = 16 [4700 / (5100 + 4700)] = 7.67 \text{ V}$$

2. Short V_{source} (R_1 in parallel with R_2)


$$R_{EQ} = (R_1 \times R_2) / (R_1 + R_2)$$

$$R_{EQ} = (5100 \times 4700) / (5100 + 4700) = 2446 \Omega$$

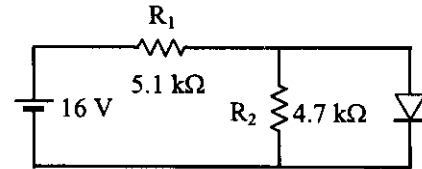3. Redraw with V_{TH} , R_{EQ} , Diode

$$V_{TH} = I_D R_{EQ} + V_D \quad I_D = (V_{TH} - V_D) / R_{EQ}$$

$$I_D = (7.67 - 0.7) / 2446 = 2.85 \text{ mA}$$



Alternative Solution Method

$$V_{R2} = V_D = 0.7 \text{ V}$$

$$I_{R2} = V_{R2} / R_2 = 0.7 / 4700 = 0.15 \text{ mA}$$

$$I_{R1} = (V - V_{R2}) / R_1 = (16.0 - 0.7) / 5100 = 3.0 \text{ mA}$$


$$I_{Total} = I_{R1}$$

$$I_D = I_{Total} - I_{R2} = 3.00 - 0.15 = 2.85 \text{ mA}$$

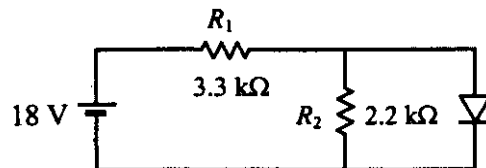Exercise

Calculate the Current I_D

Answer: $I_D = 4.9 \text{ mA}$ $V_D = 0.7 \text{ V}$



Zener Diodes


Note: Zener diodes operate in the reverse biased mode.

Example ($V = 12\text{ V}$, $R = 1000\ \Omega$, $V_Z = 3.3\text{ V}$)

$$V = I_Z R + V_Z$$

$$12 = I_Z \times 1000 + 3.3$$
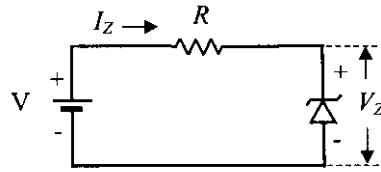
$$I_Z = (12.0 - 3.3) / 1000 = 8.7\text{ mA}$$



If $V_{\text{Source}} > V_Z$ then V_0 maintained at V_Z , else $V_0 = 0$


Example (Refer to the Diode Circuit Notes and Zener Diode Lecture Notes)

For $V_Z = 5.1\text{ V}$, Calculate I_{Total} and I_{R2} and I_Z

1. Calculate V_{TH}

$$V_{\text{TH}} = 20 \left(\frac{3300}{1100 + 3300} \right)$$

$$V_{\text{TH}} = 15\text{ V}$$

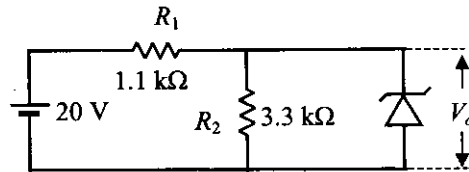

2. Calculate R_{EQ}

$$R_{\text{EQ}} = (1100 \times 3300) / (1100 + 3300)$$

$$R_{\text{EQ}} = 825\ \Omega$$

3. Calculate I_{Total} and I_{R2} and I_Z

$$V_{\text{TH}} = I_{\text{Total}} R_{\text{EQ}} + V_Z$$

$$I_Z = (V_{\text{TH}} - V_Z) / R_{\text{EQ}}$$

$$I_Z = (15 - 5.1) / 825 = 12\text{ mA}$$

$$I_{R2} = V_{R2} / R_2 = V_D / R_2 = 5.1 / 3300 = 1.55\text{ mA}$$

$$I_{\text{Total}} = I_Z + I_2 = 12 + 1.6 = 13.55\text{ mA}$$

Alternative Solution Method

$$V_{R2} = V_Z = 5.1\text{ V}$$

$$I_{R2} = V_{R2} / R_2 = 5.1 / 3300 = 1.55\text{ mA}$$

$$I_{R1} = (V - V_{R2}) / R_1 = (20.0 - 5.1) / 1100 = 13.55\text{ mA}$$

$$I_{\text{Total}} = I_{R1} = 13.55\text{ mA}$$

$$I_Z = I_{\text{Total}} - I_{R2} = 13.55 - 1.55 = 12\text{ mA}$$

Exercise


For $V = 21$, $R_1 = 1000$, $R_2 = 2000$, $V_Z = 7.5\text{ V}$

Calculate I_Z and I_{R2} and I_{Total}




Answers:

$$V_{\text{TH}} = 14\text{ V}, \quad R_{\text{EQ}} = 666\ \Omega, \quad V_0 = V_Z = 7.5\text{ V}$$

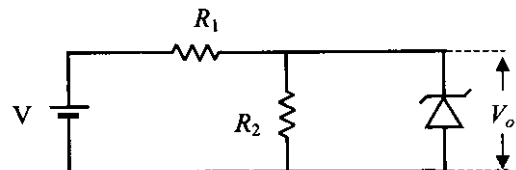
$$I_Z = 9.75\text{ mA}, \quad I_{R2} = 3.75, \quad I_{\text{Total}} = 13.5\text{ mA}$$




Light Emitting Diode LED

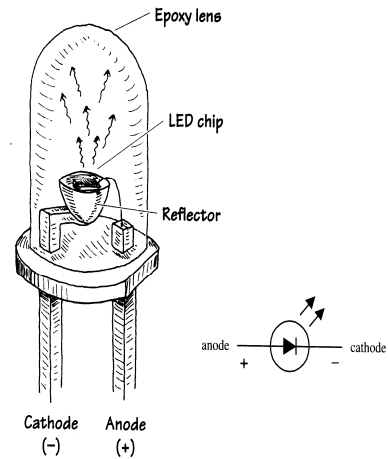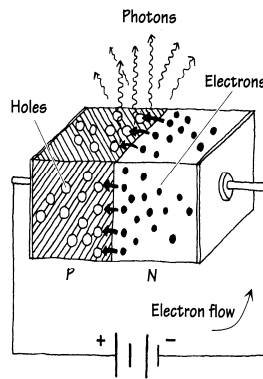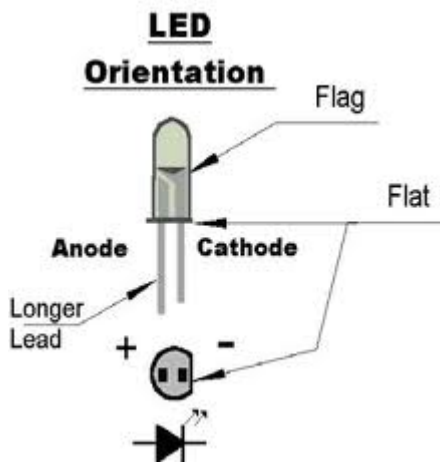

PhotoResistor

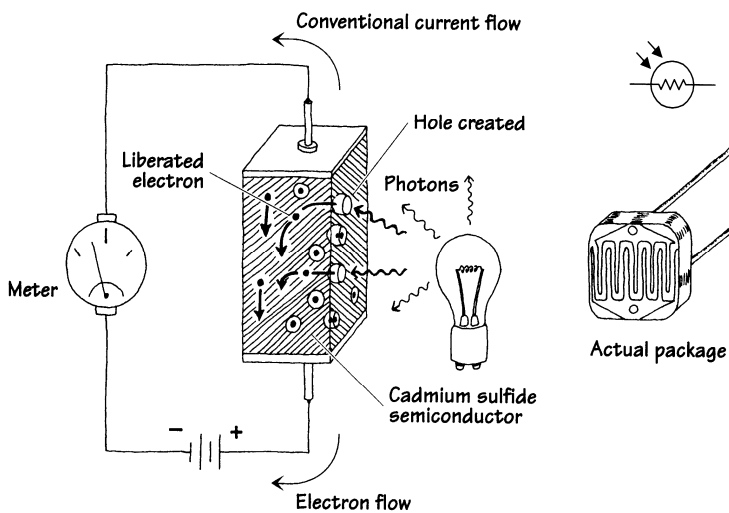


Light-Sensitive Voltage Divider

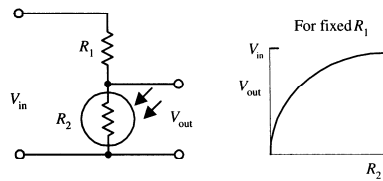


$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

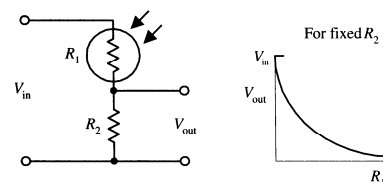
As the intensity of light increases, the resistance of the photoresistor decreases, so V_{out} in the top circuit gets smaller as more light hits it, whereas V_{out} in the lower circuit gets larger.



PhotoDiode

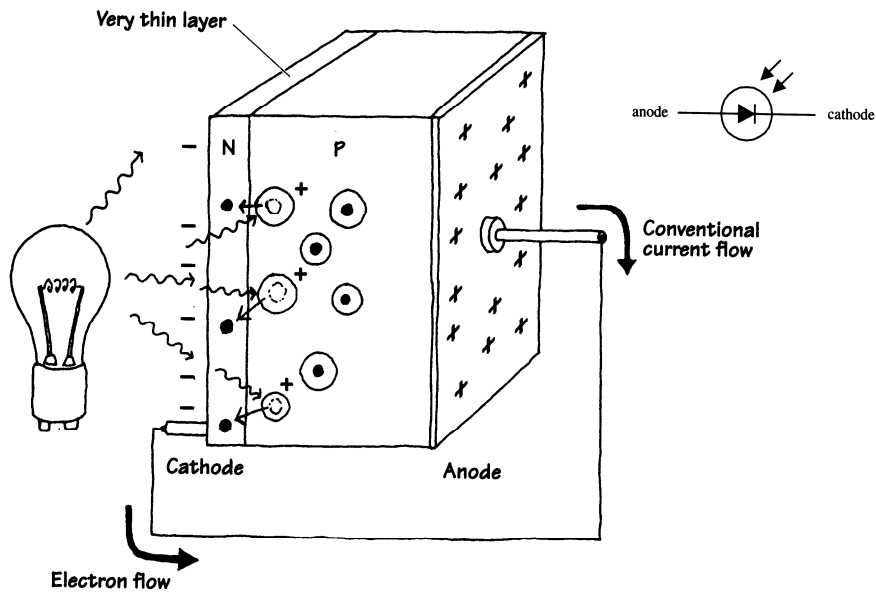


PhotoTransistors

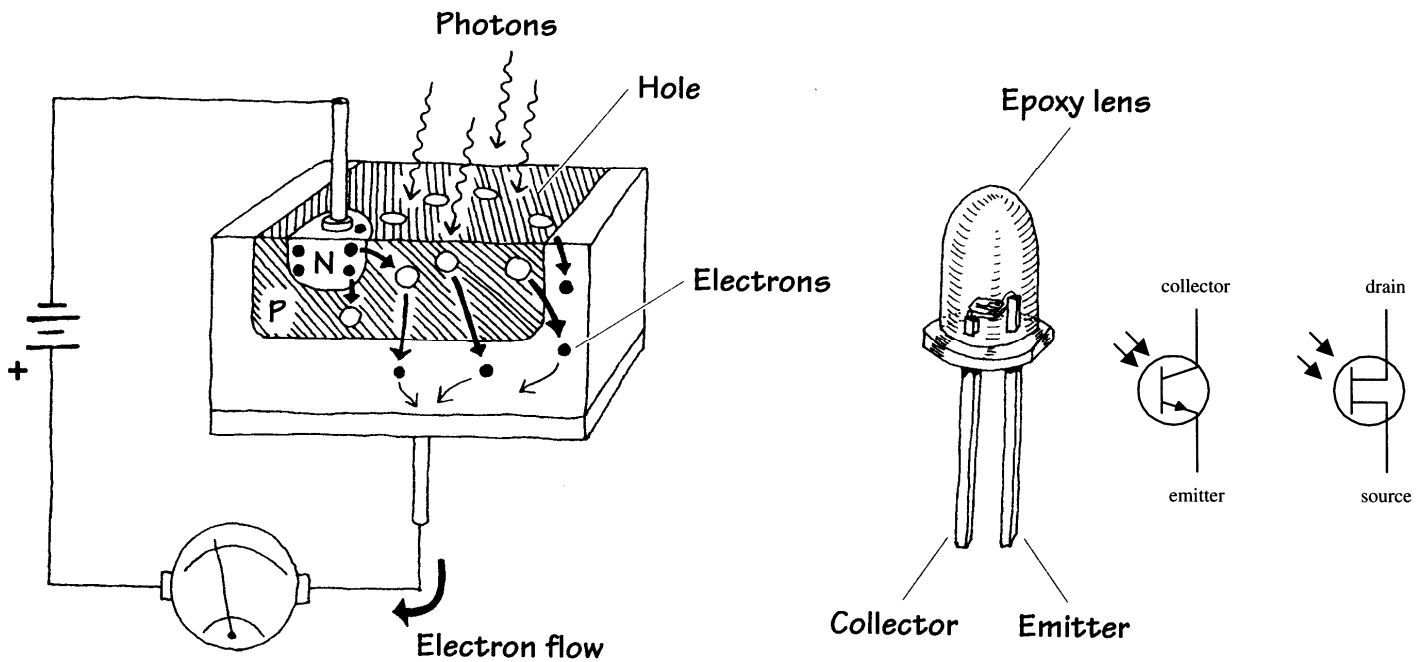


Source: Scherz, Practical Electronics for Inventors, 2nd & 3rd Editions

LED Current Limiting

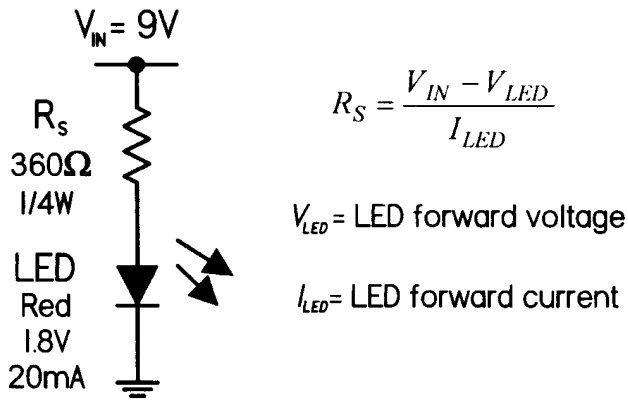


LEDs in Series

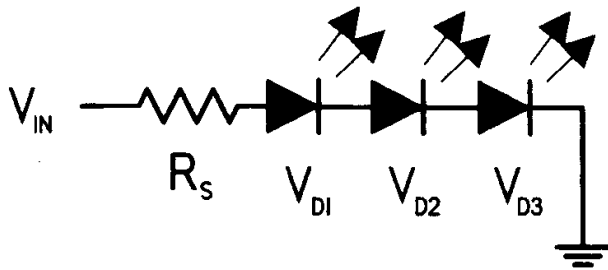


$$R_S = \frac{V_{IN} - (V_{D1} + V_{D2} + V_{D3})}{I_{D,max}}$$

LEDs in Parallel

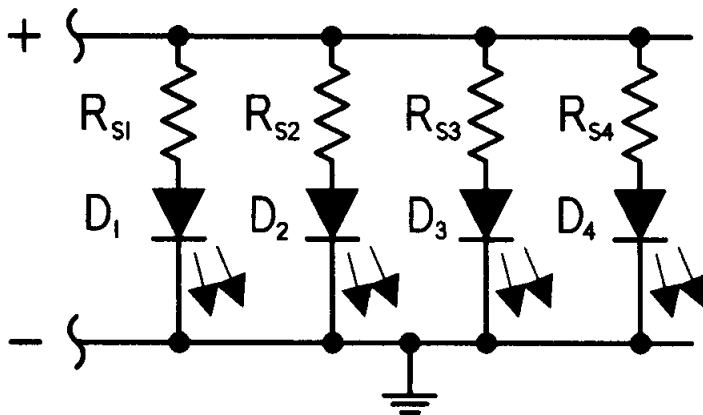


Reference: Scherz, Practical Electronics for Inventors, 2nd & 3rd Editions

AC-DC Polarity Indicator

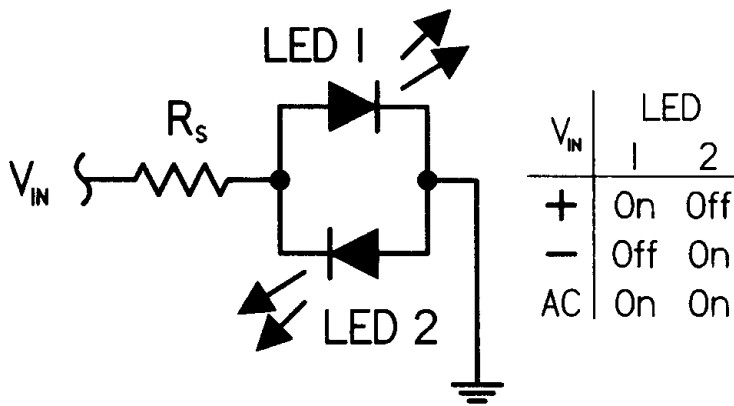

Voltage-Level Indicator

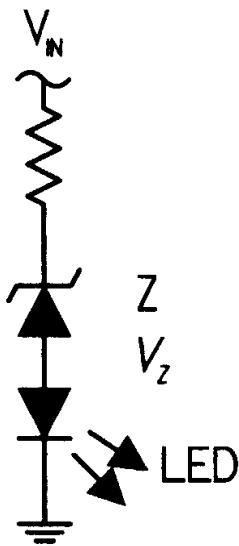


LED lights
when V_Z is
exceeded

$$R_S = \frac{V_{In} - [V_Z + V_{LED}]}{I_{LED}}$$

$$V_{In(\text{Minimum})} = R_S I_{LED} + V_Z + V_{LED}$$


Driving LEDs from 120VAC

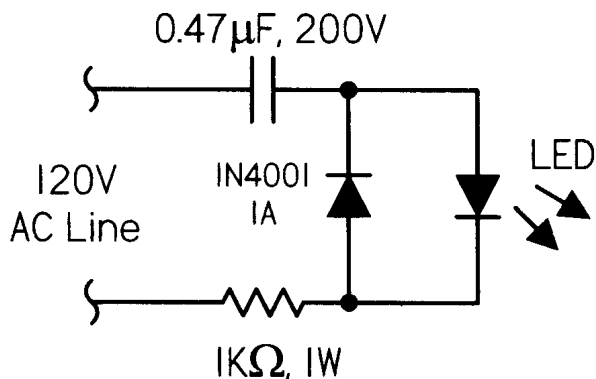


Reference: Scherz, Practical Electronics for Inventors, 2nd & 3rd Editions

Voltage Dropper



DC application

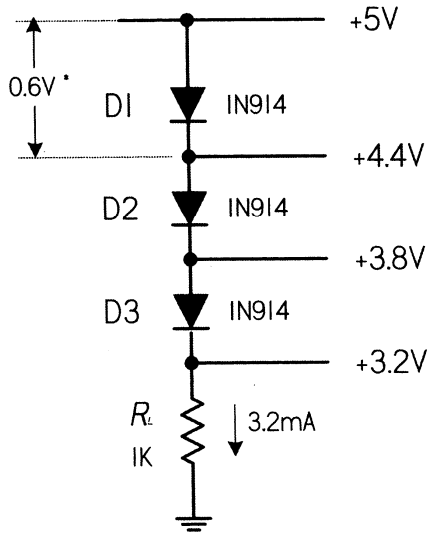

Voltage Regulator

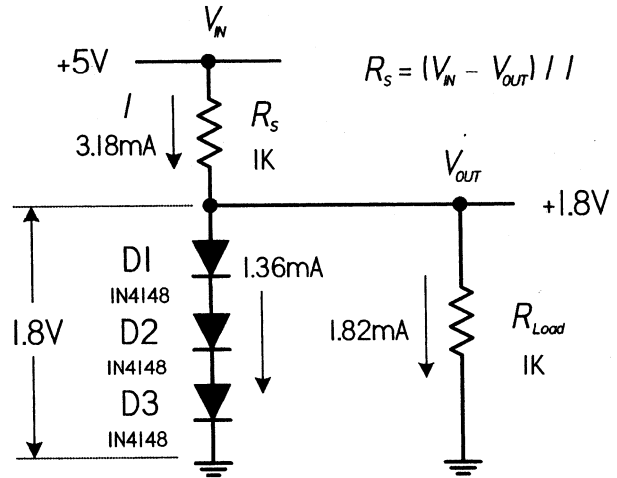

Light-Sensitive Voltage Divider

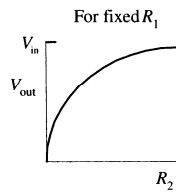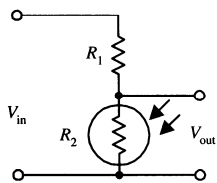

$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

As the intensity of light increases, the resistance of the photoresistor decreases, so V_{out} in the top circuit gets smaller as more light hits it, whereas V_{out} in the lower circuit gets larger.

