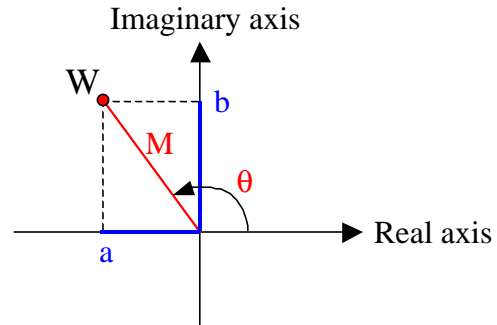


## Review of Complex Numbers

A complex number represents a point in a 2D space. The value of the complex number can be represented either by its real part (a) and imaginary part (b), or by its magnitude (M) and its phase angle ( $\theta$ ), as shown in the figure below.

$$\begin{aligned} \mathbf{W} &= a + jb \\ &= M e^{j\mathbf{q}} = (M \cos \mathbf{q}) + j(M \sin \mathbf{q}) \end{aligned}$$



Computations involving two complex numbers:  $x = a + jb = M e^{j\mathbf{q}}$  and  $y = c + jd = N e^{j\mathbf{j}}$

(a) Addition and subtraction:

$$z = x \pm y = (a + c) + j(b + d)$$

(b) Multiplication:

$$z = x y = (a + jb)(c + jd) = (ac - bd) + j(bc + ad)$$

$$z = x y = (M e^{j\mathbf{q}})(N e^{j\mathbf{j}}) = (MN) e^{j(\mathbf{q} + \mathbf{j})}$$

Therefore, Magnitude of  $z = (\text{magnitude of } x) \cdot (\text{magnitude of } y)$   
 Phase angle of  $z = (\text{phase angle of } x) + (\text{phase angle of } y)$

(c) Division:

$$z = \frac{x}{y} = \frac{a + jb}{c + jd} = \frac{(a + jb)(c - jd)}{(c + jd)(c - jd)} = \left( \frac{ac + bd}{c^2 + d^2} \right) + j \left( \frac{bc - ad}{c^2 + d^2} \right)$$

$$z = \frac{x}{y} = \frac{M e^{j\mathbf{q}}}{N e^{j\mathbf{j}}} = \left( \frac{M}{N} \right) e^{j(\mathbf{q} - \mathbf{j})}$$

Therefore, Magnitude of  $z = (\text{magnitude of } x) \div (\text{magnitude of } y)$   
 Phase angle of  $z = (\text{phase angle of } x) - (\text{phase angle of } y)$

## Power and Voltage Ratios Expressed in Decibels (dB's)

$$1 \text{ Bel} = \log(\text{Power}_2 / \text{Power}_1)$$

$$1 \text{ decibel} = 1 \text{ dB} = 0.1 \text{ Bel, hence } 10 \text{ dB} = 1 \text{ Bel}$$

To express a Power Ratio in dB's, use  $\text{dB} = 10 \log(\text{Power}_2 / \text{Power}_1)$

$$\text{Let } \text{Power}_2 = 2 \text{ Power}_1$$

$$\text{Power Ratio in dB's} = 10 \log(2 \text{ Power}_1 / \text{Power}_1) = 10 \log(2) = +3.01$$

$$\text{Let } \text{Power}_2 = 0.5 \text{ Power}_1$$

$$\text{Power Ratio in dB's} = 10 \log(0.5 \text{ Power}_1 / \text{Power}_1) = 10 \log(0.5) = -3.01$$

-3 dB is often expressed as "3 dB Down" which is the half power point ( $\text{Power}_2 = 1/2 \text{ Power}_1$ )

$$\text{Let } \text{Power}_2 = \text{Power}_1$$

$$\text{Power Ratio in dB's} = 10 \log(\text{Power}_1 / \text{Power}_1) = 10 \log(1) = 0$$

dB = 0 does not imply zero power but rather a power ratio of one-to-one

dB = 0 can be used as a zero reference; that is to say, set your reference level to a particular value and then use the dB scale to refer all other values to that reference level.

Examples: Reference Level = 400 watts.

$$200 \text{ watts} = -3 \text{ dB}$$

$$800 \text{ watts} = +3 \text{ dB}$$

$$400 \text{ watts} = 0 \text{ dB}$$

$$4000 \text{ watts} = +10 \text{ dB}$$

$$40 \text{ watts} = -10 \text{ dB}$$

$$650 \text{ watts} = +2.1 \text{ dB}$$

$$65 \text{ watts} = -7.9 \text{ dB}$$

$$100 \text{ watts} = -6 \text{ dB}$$

$$2,500,000 \text{ watts} = +38 \text{ dB}$$

Note: A reference of 1 milliwatts is used for dBm's

$$1 \text{ milliwatts} = 10 \log(1 / 1) = 0 \text{ dBm}$$

$$5 \text{ milliwatts} = 10 \log(5 / 1) = +7 \text{ dBm}$$

$$500 \text{ milliwatts} = +27 \text{ dBm}$$

$$0.001 \text{ milliwatts} = -30 \text{ dBm}$$

For Voltage,  $\text{Power} = IE = (E/R)E = E^2/R$

To express a Voltage Ratio in dB's, use  $\text{dB} = 10 \log(\text{Power}_2 / \text{Power}_1) = 10 \log[(E_2^2/R) / (E_1^2/R)]$   
 $10 \log[(E_2^2/R) / (E_1^2/R)] = 10 \log(E_2^2 / E_1^2) = 20 \log(E_2 / E_1)$

$$\text{For Power Ratio dB} = +3, \quad 20 \log(E_2 / E_1) = +3$$

$$\text{For Power Ratio dB} = -3, \quad 20 \log(E_2 / E_1) = -3$$

$$\text{For Power Ratio dB} = 0, \quad 20 \log(E_2 / E_1) = -0.15 \text{ and } E_2 / E_1 = 0.707 = \text{SQRT}(2) / 2$$

## Ideal Transformer Relations (Equations)

Definitions:

Primary Winding (input - subscript <sub>1</sub>)

Secondary Winding (output - subscript <sub>2</sub>)

Turns Ratio =  $n_1 / n_2$  (number of turns on primary winding / number of turns on secondary winding)

Voltage Ratio:  $V_1 / V_2 = n_1 / n_2$  (Directly Proportional)

Current Ratio:  $I_1 / I_2 = n_2 / n_1$  (Inversely Proportional)

Power Ratio: 1 to 1 (Power Out = Power In) Ideal

Power Out =  $e \times$  Power In where  $e$  is the Efficiency Factor ( $e < 1$ )

Impedance Ratio:  $Z_1 / Z_2 = (n_1 / n_2)^2$

For additional information, refer to



Practical Electronics for Inventors, 3ed pp 374 - 402

## Transformer Problems and Questions

1. Given an ideal transformer with primary turns = 9600 and secondary turns = 480, assume 100% efficiency. For input voltage = 120 VAC and output impedance = 16 ohms;
  - a. Calculate output voltage
  - b. Calculate output current
  - c. Calculate output power
  - b. Calculate input current
  - c. Calculate input power
  - b. Calculate input impedance
2. Determine the turns ratio for an impedance matching transformer where the first stage input impedance is 50 ohms and the second stage output impedance is 8 ohms.

## Half-Wave & Full Wave Rectifiers, Filtering, Regulated Power Supply
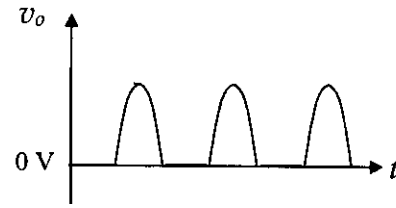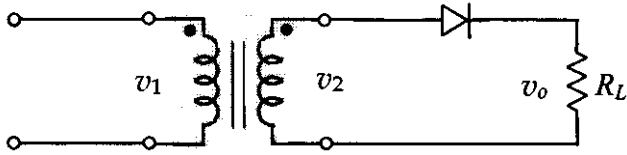
### Half-Wave Rectifier Equivalent DC Output Voltage



#### Example

Given:

$$v_{\text{in(RMS)}} = 110\text{ V (60 HZ)}$$

Turns Ratio 10:1

Find:  $v_{\text{out(DC Effective)}}$

$$v_{\text{in(Peak)}} = 1.414 v_{\text{in(RMS)}} = 1.414 \times 110 = 155.5\text{ V}$$

$$v_{\text{out(Peak)}} = 1/10 v_{\text{in(Peak)}} = 1/10 \times 155.5 = 15.6\text{ V}$$

$$v_{\text{Diode}} = 15.6 - 0.7 = 14.9\text{ V}$$

$$V_{\text{out(DC Effective)}} = 0.318 v_{\text{Diode}} = 0.318 \times 14.9 \approx 4.7\text{ VDC}$$

#### Exercise #1

Given:  $v_{\text{in(RMS)}} = 110\text{ V (60 HZ)}$  Turns Ratio 5:1

Find:  $V_{\text{out(DC Effective)}}$

Answer: 9.7 VDC




#### Exercise #2

Given:  $v_{\text{in(RMS)}} = 120\text{ V (60 HZ)}$  Turns Ratio 5:1

Find:  $V_{\text{out(DC Effective)}}$

Answer: 10.6 VDC
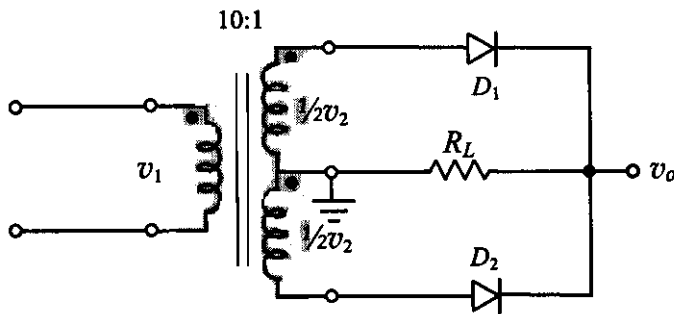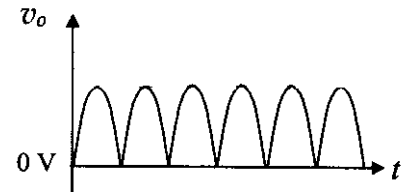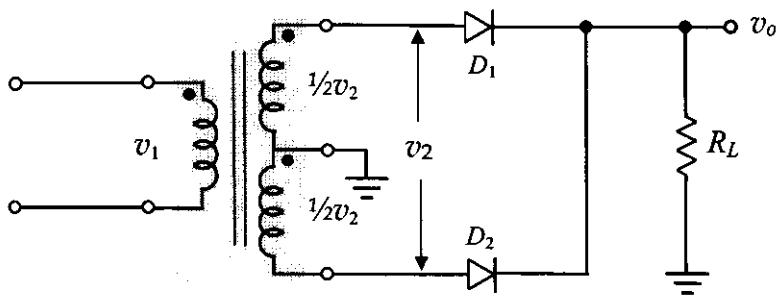
## Full-Wave Center-Tapped Rectifier Equivalent DC Output Voltage



### Example

Given:

$$v_{in(RMS)} = 110 \text{ V (60 HZ)}$$

Turns Ratio 10:1

Find:  $V_{out(DC \text{ Effective})}$

$$v_{in(Peak \text{ Center})} = 1.414 v_{in(RMS)} = 1.414 \times 110 = 155.5 \text{ V}$$

$$v_{out(Peak)} = (1/2) (1/10) v_{in(RMS)} = 1/20 \times 155.5 = 7.8 \text{ V}$$

$$V_{Diode} = 7.8 - 0.7 = 7.1 \text{ V}$$

$$V_{out(DC \text{ Effective})} = 0.636 v_{Diode} = 0.636 \times 7.1 \approx 4.5 \text{ VDC}$$

### Exercise #1

Given:  $v_{in(RMS)} = 110 \text{ V (60 HZ)}$  Turns Ratio 5:1

Find:  $V_{out(DC \text{ Effective})}$

Answer: 9.5 VDC


### Exercise #2

Given:  $v_{in(RMS)} = 120 \text{ V (60 HZ)}$  Turns Ratio 5:1

Find:  $V_{out(DC \text{ Effective})}$

Answer: 10.4 VDC
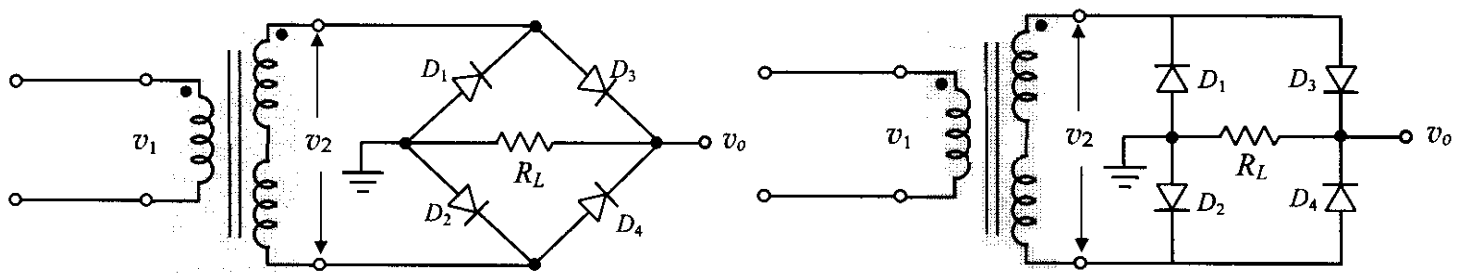
## Full-Wave Bridge Rectifier Equivalent DC Output Voltage



### Example

Given:

$$v_{in(RMS)} = 110 \text{ V (60 HZ)}$$

Turns Ratio 10:1

Find:  $V_{out(DC \text{ Effective})}$

$$v_{in(Peak)} = 1.414 v_{in(RMS)} = 1.414 \times 110 = 155.5 \text{ V}$$

$$v_{out(Peak)} = 1/10 v_{in(RMS)} = 1/10 \times 155.5 = 15.6 \text{ V}$$

$$V_{Diode} = 15.6 - 2(0.7) = 14.2 \text{ V}$$

$$V_{out(DC \text{ Effective})} = 0.636 V_{Diode} = 0.636 \times 14.2 \approx 9 \text{ VDC}$$

### Exercise #1

Given:  $v_{in(RMS)} = 110 \text{ V (60 HZ)}$  Turns Ratio 5:1

Find:  $V_{out(DC \text{ Effective})}$

Answer: 18.9 VDC


### Exercise #2

Given:  $v_{in(RMS)} = 120 \text{ V (60 HZ)}$  Turns Ratio 5:1

Find:  $V_{out(DC \text{ Effective})}$

Answer: 20.7 VDC

## Filtering

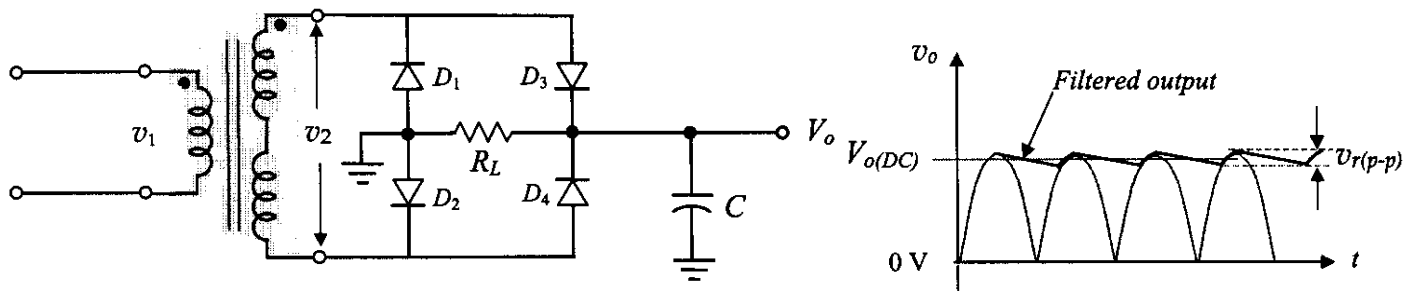

$$v_{\text{ripple(peak-peak)}} = I_{\text{out(DC)}} / 2fC$$

$$I_{\text{out(DC)}} = V_{\text{out(DC)}} / R_{\text{Load}}$$

### Two Steps

1. Assume  $V_{\text{out(DC)}}$  (Without filtering, i.e., use peak of the rectified wave, **NOT** the DC average value.)
2. Solve for  $I_{\text{out(DC)}}$  and  $v_{\text{ripple(peak-peak)}}$
3. Recalculate  $V_{\text{out(DC) Load}} = V_{\text{out(DC) (without filtering)}} - [v_{\text{ripple(peak-peak)}}] / 2$

### Example

Given:

$$v_{\text{in(RMS)}} = 110 \text{ V (60 HZ)}$$

Turns Ratio 10:1

$$R_{\text{Load}} = 100 \Omega \quad C = 1000 \mu\text{F} \quad f = 60 \text{ Hz}$$

Find:  $V_{\text{out(DC) Load}}$

From Full-Wave Bridge Rectifier (from Example page 3, above)  $V_{\text{out(DC) (without filtering)}} = 14.2 \text{ VDC}$

$$I_{\text{out(DC)}} = V_{\text{out(DC)}} / R_{\text{Load}} = 14.2 / 100 = 0.142 \text{ A} = 142 \text{ mA}$$

$$v_{\text{ripple(peak-peak)}} = I_{\text{out(DC)}} / 2fC = 0.142 / (2 \times 60 \times 1000 \times 10^{-6}) = 1.18 \text{ V}$$

$$V_{\text{out(DC) Load}} = V_{\text{out(DC) (without filtering)}} - [v_{\text{ripple(peak-peak)}}] / 2 = 14.2 - (1.18) / 2 = 13.6 \text{ VDC}$$

### Exercise

Given:

$$v_{\text{in(RMS)}} = 120 \text{ V (60 HZ)} \quad \text{Turns Ratio 5:1}$$

$$R_{\text{Load}} = 240 \Omega \quad C = 470 \mu\text{F} \quad f = 60 \text{ Hz}$$

$$V_{\text{out(DC) (without filtering)}} = 32.5 \text{ VDC (from Problem, page 3, above. Note 32.5 not } 32.5 \times .636 = 20.7)$$


Find:  $V_{\text{out(DC) Load}}$

$$\text{Answer: } I_{\text{out(DC)}} = 136 \text{ mA}$$

$$v_{\text{ripple(peak-peak)}} = 2.4 \text{ V}$$

$$V_{\text{out(DC) Load}} = 31.3 \text{ VDC}$$

## Regulated Power Supply

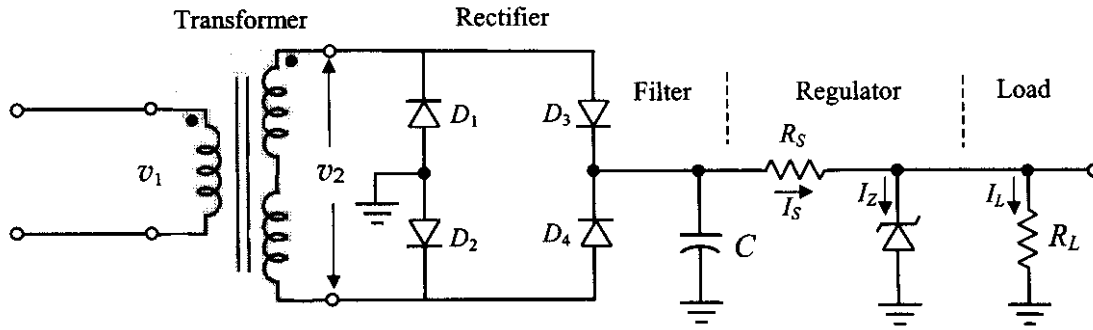

Scanned Images: Electronic Devices, Ali Aminian & Marian Kazimierzuk, Pearson-Prentice Hall, 2004