

Review materials include:

Reading Assignments & Homework

Course Notes

Diode Characteristics

Diode Circuits, Examples, and Problems

Zener Diode Circuits, Examples, and Problems

Optoelectronics (LEDs, PhotoResistors, PhotoDiodes, PhotoTransistors, Diode Logic Gates)

Review Problems (See pages 2 - 4)

Additional Review Problems (Diodes, Zeners, LED Applications)

Types of possible exam questions and problems:

Sketch diode characteristic voltage/current curves including barrier voltage values

Sketch forward and reversed biased diode circuits including mechanical switch analogs

Calculate diode circuit current and voltage values (including voltage drops across series diodes)

Calculate Zener circuit current and voltage values (V_{Zener} , I_{Zener} , V_{Load} , I_{Load} , I_{Total})


Calculate current limiting resistor values for simple LED circuits

Calculate minimum input voltage to activate LED voltage-level indicator circuits

Calculate voltage drops, current draws, and power consumption for LEDs in series and parallel configurations

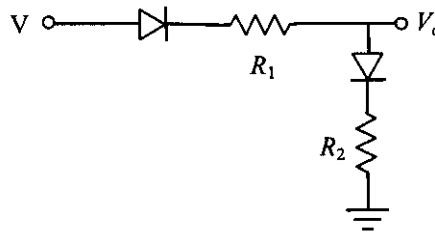1. Given:

- D_1 and D_2 silicon diodes
- $V = 18$ volts
- $R_1 = 1800 \Omega$
- $R_2 = 470 \Omega$




Calculate:

- Diode Currents
- V_o

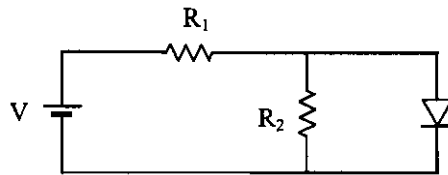2. Given:

- D_1 silicon diode
- $V = 14$ volts
- $R_1 = 220 \Omega$
- $R_2 = 750 \Omega$




Calculate:

- Diode Current
- V_{R1}
- V_{R2}
- I_{R1}
- I_{R2}

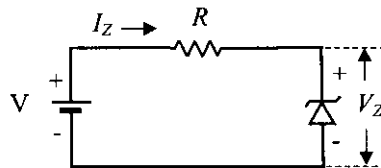3. Given:

- $V = 18$ volts
- $V_Z = 15.1$ volts
- $R = 620 \Omega$




Calculate:

- I_Z
- V_R

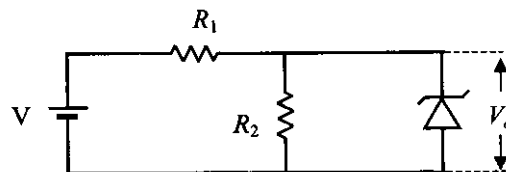4. Given:

- $V = 24$ volts
- $V_Z = 3.3$ volts
- $R_1 = 680 \Omega$
- $R_2 = 200 \Omega$




Calculate:

- V_o
- I_{R1}
- I_{R2}
- I_Z
- I_{Total}

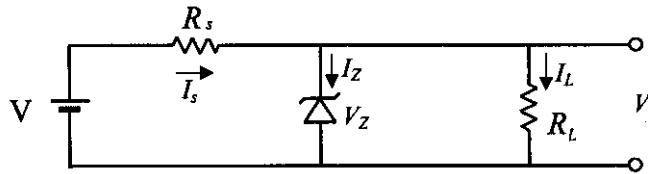5. Given:


- $V = 9$ volts
- $V_Z = 3.3$ volts
- $R_S = 180 \Omega$
- $R_L = 220 \Omega$



Calculate:


- V_o
- I_L
- I_Z
- I_S

6. Diode Voltage Divider

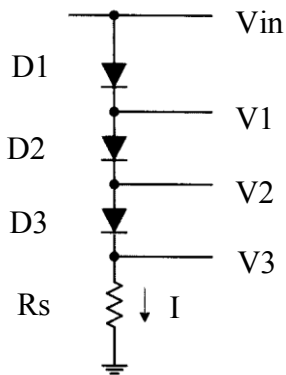


- Calculate R_S for
- $V_{in} = 9$ V
 - $V_D = 0.7$ V
 - $I = 7$ mA

7. LEDs in Series

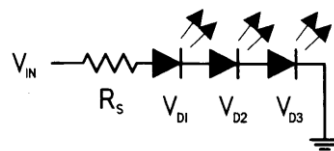


- Calculate R_S for
- $V_{in} = 12$ V
 - $V_{LED} = 1.5$ V
 - $I_{LED} = 20$ mA

8. LEDs in Parallel

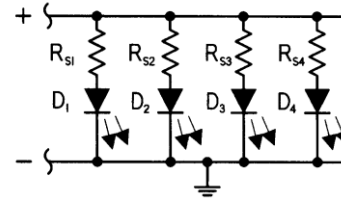


- Calculate R_{Si} for
- $V_{in} = 9$ V
 - $V_{LED1} = 1.2$ V $I_{LED} = 20$ mA
 - $V_{LED2} = 1.8$ V $I_{LED} = 20$ mA
 - $V_{LED3} = 2.4$ V $I_{LED} = 24$ mA
 - $V_{LED4} = 3.0$ V $I_{LED} = 15$ mA

9. Current Limiting Resistor

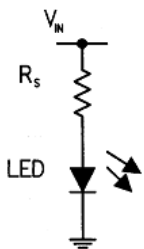

- Calculate R_S for
- $V_{in} = 3$ V
 - $V_{LED} = 1.2$ V
 - $I_{LED} = 15$ mA

10. Voltage Indicator

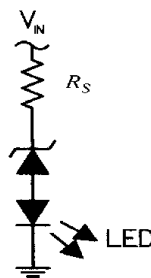

- Calculate Minimum Input Voltage
- $R_S = 470$
 - $V_{Zener} = 3.3$ V
 - $V_{LED} = 1.2$ V
 - $I_{LED} = 10$ mA

1. Diode Circuit

$$\text{Diode Currents} = 7.3 \text{ mA}$$

$$V_0 = 4.1 \text{ V}$$

2. Diode Circuit

$$\text{Diode Current} = 59.5 \text{ mA}$$

$$V_{R1} = 13.3 \text{ V}$$

$$V_{R2} = 0.7 \text{ V}$$

$$I_{R1} = 60.4 \text{ mA}$$

$$I_{R2} = 0.93 \text{ mA}$$

3. Zener Circuit

$$I_Z = 4.7 \text{ mA}$$

$$V_R = 2.9 \text{ V}$$

4. Zener Circuit

$$V_o = 3.3 \text{ V}$$

$$I_{R1} = 30.4 \text{ mA}$$

$$I_{R2} = 16.5 \text{ mA}$$

$$I_Z = 13.9 \text{ mA}$$

$$I_{\text{Total}} = 30.4 \text{ mA}$$

5. Zener Circuit

$$V_o = 3.3 \text{ V}$$

$$I_L = 15 \text{ mA}$$

$$I_Z = 16.7 \text{ mA}$$

$$I_S = 31.7 \text{ mA}$$

6. Diode Voltage Divider

$$R_s = 986 \Omega$$

7. LEDs in Series

$$R_s = 375 \Omega$$

8. LEDs in Parallel

$$R_{S1} = 390 \Omega \quad R_{S2} = 360 \Omega$$

$$R_{S3} = 275 \Omega$$

$$R_{S4} = 400 \Omega$$

9. Current Limiting Resistor

$$R_s = 120 \Omega$$

10. LED Voltage Indicator

$$V_{in} = 9.2 \text{ V}$$