
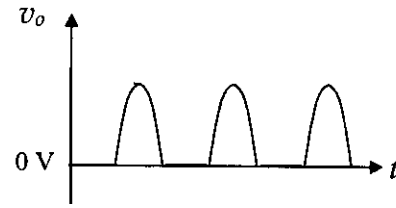


Half-Wave & Full Wave Rectifiers, Filtering, Regulated Power Supply

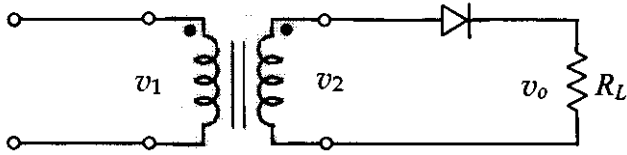Half-Wave Rectifier Equivalent DC Output Voltage



Example

Given:

$$v_{in}(\text{RMS}) = 110 \text{ V (60 HZ)}$$

Turns Ratio 10:1

Find: $v_{out}(\text{DC Effective})$

$$v_{in}(\text{Peak}) = 1.414 v_{in}(\text{RMS}) = 1.414 \times 110 = 155.5 \text{ V}$$

$$v_{out}(\text{Peak}) = 1/10 v_{in}(\text{Peak}) = 1/10 \times 155.5 = 15.6 \text{ V}$$

$$V_{\text{Diode}} = 15.6 - 0.7 = 14.9 \text{ V}$$

$$V_{out}(\text{DC Effective}) = 0.318 V_{\text{Diode}} = 0.318 \times 14.9 \approx 4.7 \text{ VDC}$$

Exercise #1

Given: $v_{in}(\text{RMS}) = 110 \text{ V (60 HZ)}$ Turns Ratio 5:1

Find: $V_{out}(\text{DC Effective})$

Answer: 9.7 VDC




Exercise #2

Given: $v_{in}(\text{RMS}) = 120 \text{ V (60 HZ)}$ Turns Ratio 5:1

Find: $V_{out}(\text{DC Effective})$

Answer: 10.6 VDC

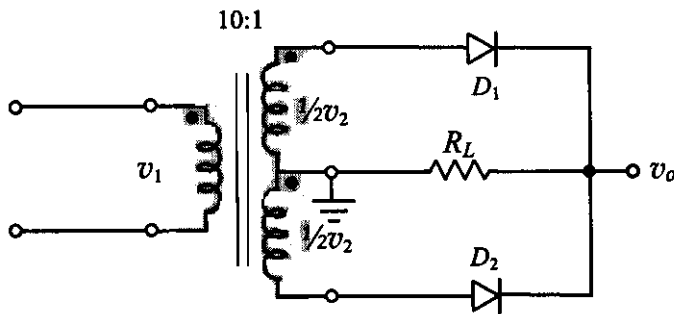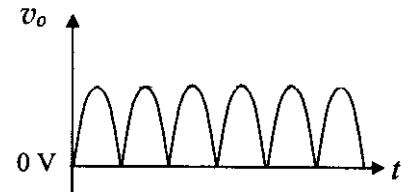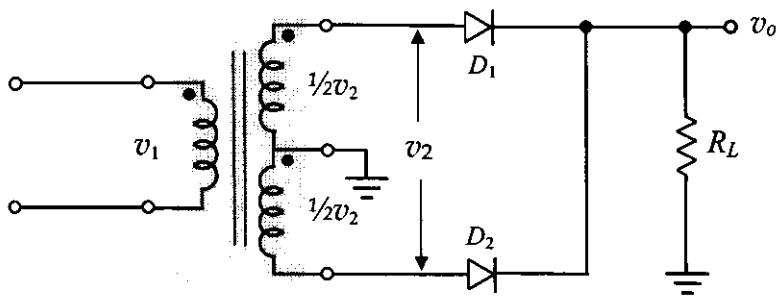Full-Wave Center-Tapped Rectifier Equivalent DC Output Voltage



Example

Given:

$$v_{in(RMS)} = 110 \text{ V (60 HZ)}$$

Turns Ratio 10:1

Find: $V_{out(DC \text{ Effective})}$

$$v_{in(Peak \text{ Center})} = 1.414 v_{in(RMS)} = 1.414 \times 110 = 155.5 \text{ V}$$

$$v_{out(Peak)} = (1/2) (1/10) v_{in(RMS)} = 1/20 \times 155.5 = 7.8 \text{ V}$$

$$V_{Diode} = 7.8 - 0.7 = 7.1 \text{ V}$$

$$V_{out(DC \text{ Effective})} = 0.636 v_{Diode} = 0.636 \times 7.1 \approx 4.5 \text{ VDC}$$

Exercise #1

Given: $v_{in(RMS)} = 110 \text{ V (60 HZ)}$ Turns Ratio 5:1

Find: $V_{out(DC \text{ Effective})}$

Answer: 9.5 VDC


Exercise #2

Given: $v_{in(RMS)} = 120 \text{ V (60 HZ)}$ Turns Ratio 5:1

Find: $V_{out(DC \text{ Effective})}$

Answer: 10.4 VDC

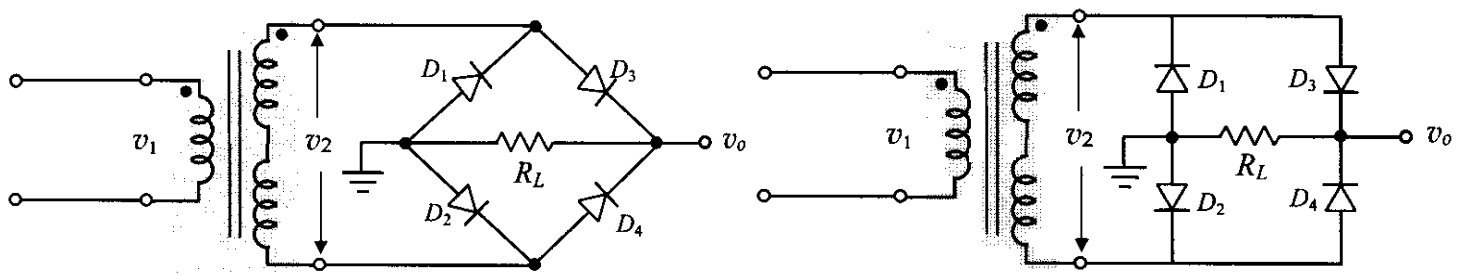Full-Wave Bridge Rectifier Equivalent DC Output Voltage



Example

Given:

$$v_{in(RMS)} = 110 \text{ V (60 HZ)}$$

Turns Ratio 10:1

Find: $V_{out(DC \text{ Effective})}$

$$v_{in(Peak)} = 1.414 v_{in(RMS)} = 1.414 \times 110 = 155.5 \text{ V}$$

$$v_{out(Peak)} = 1/10 v_{in(RMS)} = 1/10 \times 155.5 = 15.6 \text{ V}$$

$$V_{Diode} = 15.6 - 2(0.7) = 14.2 \text{ V}$$

$$V_{out(DC \text{ Effective})} = 0.636 v_{Diode} = 0.636 \times 14.2 \approx 9 \text{ VDC}$$

Exercise #1

Given: $v_{in(RMS)} = 110 \text{ V (60 HZ)}$ Turns Ratio 5:1

Find: $V_{out(DC \text{ Effective})}$

Answer: 18.9 VDC


Exercise #2

Given: $v_{in(RMS)} = 120 \text{ V (60 HZ)}$ Turns Ratio 5:1

Find: $V_{out(DC \text{ Effective})}$

Answer: 20.7 VDC

Filtering

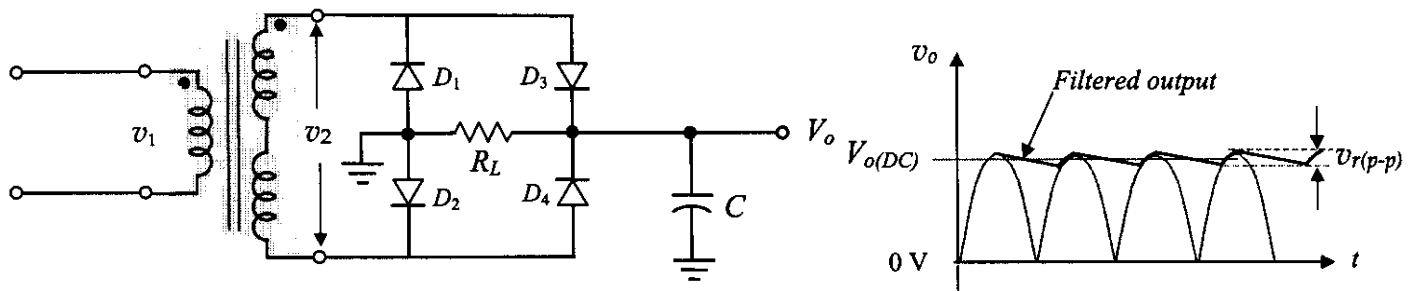

$$v_{\text{ripple(peak-peak)}} = I_{\text{out(DC)}} / 2fC$$

$$I_{\text{out(DC)}} = V_{\text{out(DC)}} / R_{\text{Load}}$$

Two Steps

1. Assume $V_{\text{out(DC)}}$ (Without filtering, i.e., use peak of the rectified wave, **NOT** the DC average value.)
2. Solve for $I_{\text{out(DC)}}$ and $v_{\text{ripple(peak-peak)}}$
3. Recalculate $V_{\text{out(DC) Load}} = V_{\text{out(DC) (without filtering)}} - [v_{\text{ripple(peak-peak)}}] / 2$

Example

Given:

$$v_{\text{in(RMS)}} = 110 \text{ V (60 Hz)}$$

Turns Ratio 10:1

$$R_{\text{Load}} = 100 \Omega \quad C = 1000 \mu\text{F} \quad f = 60 \text{ Hz}$$

Find: $V_{\text{out(DC) Load}}$

From Full-Wave Bridge Rectifier (from Example page 3, above) $V_{\text{out(DC) (without filtering)}} = 14.2 \text{ VDC}$

$$I_{\text{out(DC)}} = V_{\text{out(DC)}} / R_{\text{Load}} = 14.2 / 100 = 0.142 \text{ A} = 142 \text{ mA}$$

$$v_{\text{ripple(peak-peak)}} = I_{\text{out(DC)}} / 2fC = 0.142 / (2 \times 60 \times 1000 \times 10^{-6}) = 1.18 \text{ V}$$

$$V_{\text{out(DC) Load}} = V_{\text{out(DC) (without filtering)}} - [v_{\text{ripple(peak-peak)}}] / 2 = 14.2 - (1.18) / 2 = 13.6 \text{ VDC}$$

Exercise

Given:

$$v_{\text{in(RMS)}} = 120 \text{ V (60 Hz)} \quad \text{Turns Ratio 5:1}$$

$$R_{\text{Load}} = 240 \Omega \quad C = 470 \mu\text{F} \quad f = 60 \text{ Hz}$$

$$V_{\text{out(DC) (without filtering)}} = 32.5 \text{ VDC (from Problem, page 3, above. Note 32.5 not } 32.5 \times .636 = 20.7)$$


Find: $V_{\text{out(DC) Load}}$

Answer: $I_{\text{out(DC)}} = 136 \text{ mA}$

$v_{\text{ripple(peak-peak)}} = 2.4 \text{ V}$

$V_{\text{out(DC) Load}} = 31.3 \text{ VDC}$

Regulated Power Supply

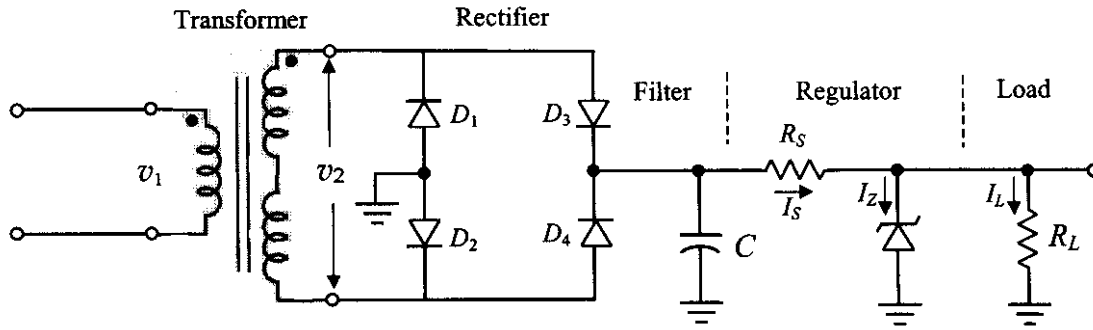

Scanned Images: Electronic Devices, Ali Aminian & Marian Kazimierczuk, Pearson-Prentice Hall, 2004