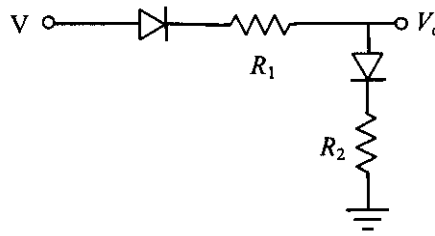


1. Given:

- D_1 and D_2 silicon diodes
- $V = 18$ volts
- $R_1 = 1800 \Omega$
- $R_2 = 470 \Omega$




Calculate:

- Diode Currents (D_1 & D_2)
- V_0

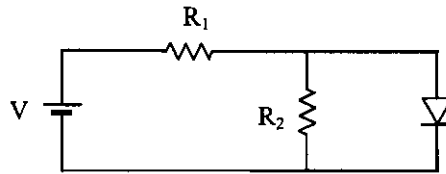2. Given:


- D_1 silicon diode
- $V = 14$ volts
- $R_1 = 220 \Omega$
- $R_2 = 750 \Omega$



Calculate:


- Diode Current
- V_{R1}
- V_{R2}
- I_{R1}
- I_{R2}

3. Diode Voltage Divider

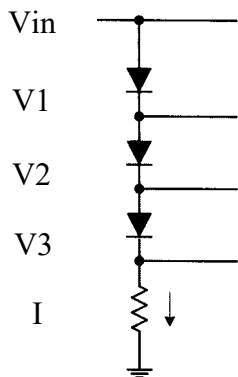


- Calculate R_s for
- $V_{in} = 9$ V
- $V_D = 0.7$ V
- $I = 7$ mA

4. LEDs in Series

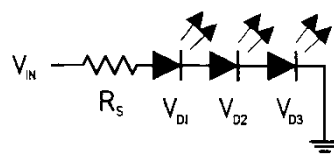

- Calculate R_s for
- $V_{in} = 12$ V
- $V_{LED} = 1.5$ V
- $I_{LED} = 20$ mA


5. LEDs in Parallel

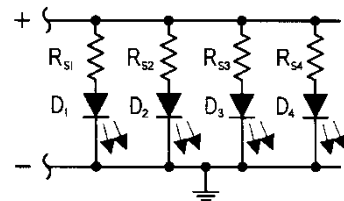

- Calculate R_{Si} for
- $V_{in} = 9$ V
- $V_{LED1} = 1.2$ V $I_{LED} = 20$ mA
- $V_{LED2} = 1.8$ V $I_{LED} = 20$ mA
- $V_{LED3} = 2.4$ V $I_{LED} = 24$ mA
- $V_{LED4} = 3.0$ V $I_{LED} = 15$ mA

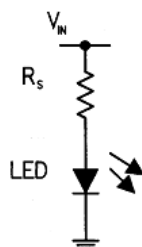6. Current Limiting Resistor

- Calculate R_s for
- $V_{in} = 3$ V
- $V_{LED} = 1.2$ V
- $I_{LED} = 15$ mA



1. Diode Circuit

Diode Currents = 7.3 mA

 $V_0 = 4.1 \text{ V}$

2. Diode Circuit

Diode Current = 59.5 mA

 $V_{R1} = 13.3 \text{ V}$ $V_{R2} = 0.7 \text{ V}$ $I_{R1} = 60.4 \text{ mA}$ $I_{R2} = 0.93 \text{ mA}$

3. Diode Voltage Divider

 $R_s = 986 \Omega$

4. LEDs in Series

 $R_s = 375 \Omega$

5. LEDs in Parallel

 $R_{S1} = 390 \Omega$ $R_{S2} = 360 \Omega$ $R_{S3} = 275 \Omega$ $R_{S4} = 400 \Omega$

6. Current Limiting Resistor

 $R_s = 120 \Omega$