


Junction Field Effect Transistors JFET

Three Terminals: Drain, Source, Gate

Majority Carriers Only (Unipolar)

N Channel Electrons

 By convention, always draw with **Drain** at the top



N Type Channel Arrow Pointing **IN**

Forward Bias Source to Drain V_{DD}

For N Channel

+ to Drain

- to Source

Conventional Current Flow I_D (From Drain to Source)

Reverse Bias Gate to Source $I_G = 0$

- to Gate

+ to Source

V_G is the Gate to Ground Voltage

V_{GS} is the Gate to Source Voltage

V_P (Pinch-Off Voltage) The V_{DS} voltage at which the current I_D levels off (for $V_{GS} = 0$)

$V_{GS(off)}$ (Gate-to-Source Cutoff Voltage $I_D = 0$) $V_P = |V_{GS(off)}|$

I_{DSS} (Drain-Source Saturation Current) Maximum current flow with $V_{GS} = 0$.

Quiescent (Operating Points)

I_{DQ}

V_{DSQ}

Shockley's Equation

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

Notes:

V_{GS} and $V_{GS(off)}$ are always the same algebraic sign, so $V_{GS} / V_{GS(off)}$ will always be positive.

For N Channel, $V_{GS(off)}$ is negative, $V_P = |V_{GS(off)}|$, so $I_D = I_{DSS} \left(1 + \frac{V_{GS}}{V_P} \right)^2$

Biassing N Channel JFETs i.e., calculating Quiescent (Operating Points), I_{DQ} and V_{DSQ}

I_{DSS} and $V_{GS(off)}$ are from readily obtainable from Transfer Characteristics Charts

For Fixed Biased, $V_{GS} = V_{GG}$ (since reversed bias, $I_G = 0$, $V_{RG} = 0$, $V_{GS} = V_{GG}$)


For Self Biased and Voltage Divider Biased, V_{GS} is the solution of a quadratic equation.

For BME 3512, I_{DSS} , $V_{GS(off)}$, V_{GS} will be given.

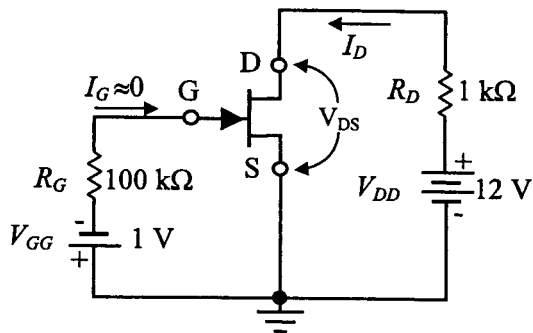Examples Biasing N Channel JFETs Determine Quiescent (Operating Points), I_{DQ} and V_{DSQ}

Fixed Biased

$$I_{DSS} = 12 \text{ mA} \quad V_{GS(off)} = -4 \text{ V}$$



A fixed bias circuit

Given: $I_{DSS} = 12 \text{ mA}$ $V_{GS(off)} = -4 \text{ V}$

Since Gate to Source is reverse biased, $I_G = 0$, hence $V_{R_g} = I_G R_g = 0$

And $V_{GG} = I_G R_g + V_{GS}$

$$V_{GG} = 0 + V_{GS}$$

$$V_{GS} = V_{GG} = -1 \text{ V}$$

From Shockley's Equation


$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = 12 \times 10^{-3} \times \left(1 - \frac{-1}{-4} \right)^2 = 6.75 \text{ mA}$$

$$V_{DD} = V_{DS} + I_D R_D \quad \rightarrow \quad V_{DS} = V_{DD} - I_D R_D = 12 - 6.75 \times 10^{-3} (1 \times 10^{-3}) = 5.25 \text{ V}$$

Answers: $I_{DQ} = 6.8 \text{ mA}$ and $V_{DSQ} = 5.3 \text{ V}$

Self-Biased

 $I_{DSS} = 16 \text{ mA}$ $V_{GS(off)} = -4 \text{ V}$



A self-biased circuit

Given: $I_{DSS} = 16 \text{ mA}$ $V_{GS(off)} = -4 \text{ V}$ $V_{GS} = \text{see below}$

The I_D current through R_S will develop a voltage across R_S such that the Source is at a positive potential with respect to Ground. If any current I_G flows at all, the Gate will be at a negative potential with respect to Ground and hence the Gate to Source will be reversed bias resulting in $I_G = 0$, hence $V_{Rg} = I_G R_g = 0$, and therefore V_G (Gate to Ground) = 0.

But $V_G = V_{GS} + I_D R_S$

$0 = V_{GS} + I_D R_S$

$I_D = -V_{GS} / R_S$

From $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$ and $I_D = -V_{GS} / R_S \rightarrow \frac{-V_{GS}}{R_S} = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$

Solve for V_{GS} (see page 5 Summary of FET Biasing Equations)


Note: For BME 3512 the value of V_{GS} will be given. $V_{GS} = -2.44 \text{ V}$

$I_D = -V_{GS} / R_S = -(-2.44) / 1 \times 10^3 = 2.44 \text{ mA}$

$V_{DD} = V_{DS} + I_D (R_D + R_S) \rightarrow V_{DS} = V_{DD} - I_D (R_D + R_S) = 15 - 2.44 \times 10^{-3} (1500 + 1000) = 8.9 \text{ V}$

Answers: $I_{DQ} = 2.4 \text{ mA}$ and $V_{DSQ} = 8.9 \text{ V}$

Voltage Divider Biased

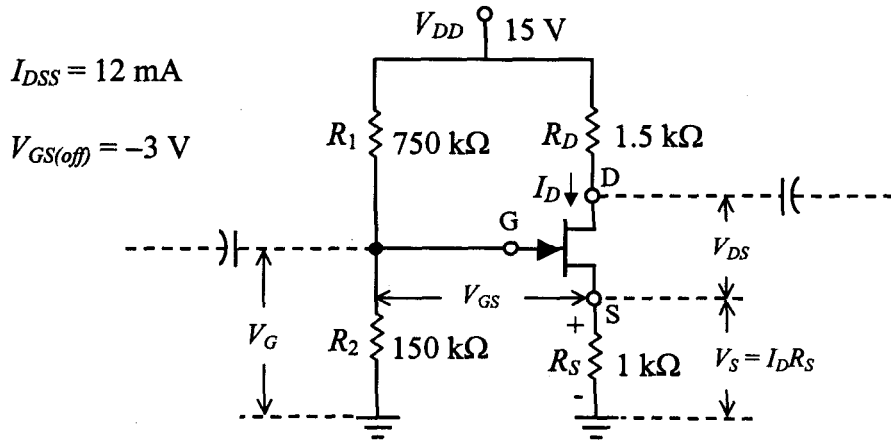

A voltage-divider biased JFET amplifier circuit

Given: $I_{DSS} = 12 \text{ mA}$ $V_{GS(off)} = -3 \text{ V}$ $V_{GS} = \text{see below}$

From the voltage divider network: $V_G = V_{DD} \frac{R_2}{R_1 + R_2}$

By definition: $V_{GS} = V_G - V_S = V_G - I_D R_S$

Hence $I_D = (V_G - V_{GS}) / R_S$

From $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2$ and $I_D = (V_G - V_{GS}) / R_S \rightarrow \frac{V_G - V_{GS}}{R_S} = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2$

Solve for V_{GS} (see page 5 Summary of FET Biasing Equations)

Note: For BME 3512 the value of V_{GS} will be given. $V_{GS} = -1.31 \text{ V}$

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2} = 15 \frac{150 \text{ K}}{750 \text{ K} + 150 \text{ K}} = 2.50 \text{ V}$$

$$I_D = (V_G - V_{GS}) / R_S = [2.5 - (-1.31)] / 1000 = 3.81 \text{ mA}$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S) = 15 - 3.81 \times 10^{-3} (1500 + 1000) = 5.48 \text{ V}$$

Answers: $I_{DQ} = 3.8 \text{ mA}$ and $V_{DSQ} = 5.5 \text{ V}$

Summary of Equations for the Analysis of Self-Biased and Voltage-Divider Biased JFET Amplifier

Self-bias:

$$V_{GS} \Big|_{n\text{-channel}} = \frac{-b + \sqrt{b^2 - 4ac}}{2a}$$

$$V_{GS} \Big|_{p\text{-channel}} = \frac{+b - \sqrt{b^2 - 4ac}}{2a}$$

where,

$$a = \frac{I_{DSS} R_S}{V_P^2} \qquad b = \frac{2I_{DSS} R_S}{|V_P|} + 1 \qquad c = I_{DSS} R_S$$

$$I_D = \frac{-V_{GS}}{R_S}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

Voltage-divider bias:

$$V_{GS} \Big|_{n\text{-channel}} = \frac{-b + \sqrt{b^2 - 4ac}}{2a}$$

$$V_{GS} \Big|_{p\text{-channel}} = \frac{+b - \sqrt{b^2 - 4ac}}{2a}$$

where,

$$a = \frac{I_{DSS} R_S}{V_P^2} \qquad b = \frac{2I_{DSS} R_S}{|V_P|} + 1 \qquad c = I_{DSS} R_S - |V_G|$$

$$I_D = \frac{V_G - V_{GS}}{R_S}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$