

## Logic Circuits

Combinational or Memoryless Logic Circuits  
Function of Current Input Only

Sequential or Memory Logic Circuits  
Function of Current Input plus Past Inputs

State Table (Outputs & Next State)  
Next State = Present State + Current Input

## Moore & Mealy Machines

Moore Machine  
Outputs Function of State Only

Mealy Machine  
Outputs Function of State and Input

## Sequential Machines

Synchronous Sequential Machines  
Defined only at discrete times  
Controlled by external clock  
Uses Flip-Flops to hold  
state variables between clock pulses

Asynchronous Sequential Machines  
Defined for all times  
No need for explicit memory  
Simpler - Two Implementation Restrictions

## Asynchronous Machines

No more than one input variable may change at any one time. State variable must be assigned in such a way that no more than one state variable changes for any possible state changes.

"Simultaneous" Signal Changes

Finite Propagation Times

If  $00 > 11$  may happen in several ways

$00 > 01 > 11$  or

$00 > 10 > 11$

Depends on "who wins the race"

May have "Don't Care" States

## Mealy & Moore Machines

Moore Machine is a finite-state machine whose output values are determined solely by its current state and can be defined as six elements  $(S, S_0, \Sigma, \Lambda, T, G)$ , consisting of the following:

a finite set of states  $(S)$

a start state (also called initial state)  $S_0$  which is an element of  $(S)$

a finite set called the input alphabet  $(\Sigma)$

a finite set called the output alphabet  $(\Lambda)$

a transition function  $(T : S \times \Sigma \rightarrow S)$  mapping a state and the input alphabet to the next state

an output function  $(G : S \rightarrow \Lambda)$  mapping each state to the output alphabet.

Mealy Machine output values are determined both by its current state and by the values of its inputs and can be defined as six elements  $(S, S_0, \Sigma, \Lambda, T, G)$ , consisting of the following:

a finite set of states  $(S)$

a start state (also called initial state)  $S_0$  which is an element of  $(S)$

a finite set called the input alphabet  $(\Sigma)$

a finite set called the output alphabet  $(\Lambda)$

a transition function  $(T : S \times \Sigma \rightarrow S)$  mapping a state and the input alphabet to the next state

**an output function  $(G : S \times \Sigma \rightarrow \Lambda)$  mapping pairs of a state and an input symbol to the corresponding output symbol.**

[http://en.wikipedia.org/wiki/Theory\\_of\\_Computation](http://en.wikipedia.org/wiki/Theory_of_Computation)

## Digital Logic Signal Levels and State Variables

### Simple Positive Logic

Define "Lo" = State "0" = 0; i.e., "near 0 volts, or maybe +0.7V, or less than +2.1V, etc."

Define "Hi" = State "1" = 1; i.e., "near Vcc,

say +5V, or greater than +3.9V, etc. for TTL;  
or +15V, or greater than +13.1V, etc. for CMOS."

Remember these are arbitrary definitions.

Notice however, that State "1" is more positive than State "0". With this in mind, we can even define

"Hi" = State "1" = 1 = 0 volts, and

"Lo" = State "0" = 0 = -5 volts.

We still have State "1" more positive than State "0".

And Boolean Algebra doesn't care!

### Simple Negative Logic

Try reversing things, such that State "1" is more negative than State "0"; i.e.,

State "1" = 0 volts, and

State "0" = +5 volts, or even

State "1" = -5 volts, and

State "0" = 0 volts.

In both cases, State "1" is more negative than State "0".

### Positive Logic Truth Tables

A	B	AND	OR
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

### Negative Logic Truth Tables

$\bar{A}$	$\bar{B}$	OR	AND
1	1	1	1
1	0	1	0
0	1	1	0
0	0	0	0

Note: **Positive AND Logic = Negative  $\overline{\text{OR}}$  Logic**

**Positive OR Logic = Negative  $\overline{\text{AND}}$  Logic**

### DeMorgan's Law

$$\overline{A \bullet B} = \bar{A} + \bar{B}$$

$$\overline{A + B} = \bar{A} \bullet \bar{B}$$

$$\overline{\overline{A \bullet B}} = \overline{\bar{A} + \bar{B}} = \overline{\bar{A}} \bullet \overline{\bar{B}} = A \bullet B$$

$$\overline{\overline{A + B}} = \overline{\bar{A} \bullet \bar{B}} = \overline{\bar{A}} + \overline{\bar{B}} = A + B$$

Positive Logic  $A \bullet B$  = Negative Logic  $\overline{\overline{A + B}}$

Positive Logic  $A + B$  = Negative Logic  $\overline{\overline{A \bullet B}}$

## Making Sense of SR Flip Flop Seemingly Contradictory Explanations

### SR Flip Flop

Unfortunately, there is no consistency in describing the operation of SR Flip Flops (Set Reset); in fact, many of us even refer to them as RS Flip Flops.

However, one property description is pretty much universal:

Set **S** implies  $Q = 1$

Reset **R** implies  $Q = 0$

Adding even more to the confusion, is an error in the Scherz textbook, *Practical Electronics for Inventors*, 3ed, page 770, Figure 12-70 / 4ed, page 759, Figure 12-56 Cross NAND SR Flip Flop; the outputs  $Q$  and  $\bar{Q}$  are reversed.  $Q$  should be associated with the S input NAND gate and  $\bar{Q}$  should be associated with the R input NAND gate.

Be careful, don't confuse yourself when using other resources; some authors associate  $Q$  and  $\bar{Q}$  with S & R respectively, other authors reverse the association. And then there is the confusion with respect to NOR SR Flip Flops, NAND SR Flip Flops, and inverted inputs to both NOR and NAND Flip Flops. For our purposes, the following concepts apply:

Set **S** implies  $Q = 1$

Reset **R** implies  $Q = 0$

Not Allowed      NOR Gates      S = 1 and R = 1  
                             NAND Gates      S = 0 and R = 0

If provisions for a clock pulse are not available, the circuit is known as an asynchronous flip flop.

### Triggered or T Flip Flops

If the S and R inputs are gated with a clock pulse, the circuit is known as a synchronous flip flop.

If gated by a NAND, the S and R inputs are only enabled when the clock pulse is high.

When the clock is low, the inputs are disabled and the flip flop is placed in the Hold mode.

### Latched Data or D Flip Flops (Single Input Device)

Invert the S input and apply to the R input:

if S = 0 then R = 1

if S = 0 then R = 0

but never S = R

Rename S as D:

D	S	R	Q
0	0	1	0 (Reset)
1	1	0	1 (Set)

Each change in the input data toggles a change in the output.

### J K Master-Slave Flip Flop

Inputs: J, K, Set, Clear, Clock

Outputs:  $Q$   $\bar{Q}$

Trailing Edge Triggered Flip Flop


Master triggers on the clock up-tick (slave inactive)

Slave follows master on the clock down-tick

Control	Q
Set	1
Clear	0

Input	Q
J K	Q Hold
0 0	Q Hold
0 1	0 Reset
1 0	1 Set
1 1	$\bar{Q}$ Toggle
 
## 555 Astable Multivibrator Characteristics



The following computational formulas apply to the 555 configuration shown above.

$$\text{On-Time} = t_h = 0.69 (R_1 + R_2) C$$

$$\text{Off-Time} = t_l = 0.69 (R_2) C$$

$$\text{Period} = t_l + t_h = 0.69 (R_1 + 2R_2) C$$

$$\text{Frequency} = 1 / \text{Period} = 1.44 / (R_1 + 2R_2) C$$


$$\text{Duty Cycle} = t_h / (t_l + t_h) = (R_1 + R_2) / (R_1 + 2R_2)$$

## RS Flip Flop Truth Tables

In order to eliminate ambiguity and to achieve some sense of continuity, we will follow the convention:

**Set** implies  $Q = 1$ .

**Reset** implies  $Q = 0$ .

 

**Set Reset**


**NOR Gates**

S	R	Q
0	0	Q Hold
0	1	0 Reset
1	0	1 Set
1	1	X

X = Not Allowed

S=1 => Set (Q=1)

R=1 => Reset (Q=0)

 

**Set Reset**


**NAND Gates**

S	R	Q
0	0	X
0	1	1 Set
1	0	0 Reset
1	1	Q Hold

X = Not Allowed

S=0 => Set (Q=1)

R=0 => Reset (Q=0)

 

**Set Reset**

**NAND Gates with Inverted S & R inputs**

S	R	$\bar{S}$	$\bar{R}$	Q
0	0	1	1	Q Hold
0	1	1	0	0 Reset
1	0	0	1	1 Set
1	1	0	0	X

X = Not Allowed

S=1 =>  $\bar{S}$ =0 => Set (Q=1)

R=1 =>  $\bar{R}$ =0 => Reset (Q=0)

As you can see, there is consistency for **Set** means  $Q=1$  and **Reset** means  $Q=0$ ; but there can be confusion trying to decide whether-or-not S & R are 0 or 1 depending on the type of gates (NOR or NAND).

If inverted S & R inputs are used with the NAND gates, then S=1 is the Set input and R=1 is the Reset input; which is the same as the NOR gates implementation.

# Rectangular Wave & Square Wave Generators (Op-Amp Schmitt Triggers & 555 Timers)

 


Figure 16-15: Square-wave generator

 


Figure 16-17: The 555 timer connected as a rectangular waveform generator

## SQUARE-WAVE GENERATOR

Recall that the output of the Schmitt trigger, which was introduced in Chapter 11 as a bi-reference level comparator, is a square wave with  $\pm v_{o(p)} = \pm V_{sat}$  of the op-amp. With the addition of a capacitor  $C$  and a feedback resistor  $R$ , as shown in Figure 16-15(a), the need for an input signal is eliminated and the output frequency can also be controlled by proper selection of the  $R$  and  $C$ .

 


Figure 16-15: Square-wave generator

Referring to Equations 11-7 and 11-8, the upper and lower threshold voltages ( $V_{UT}$  &  $V_{LT}$ ) or ( $\pm V_{th}$ ) can be written in one equation as follows:

$$\pm V_{th} = \pm V_{sat} \frac{R_2}{R_1 + R_2} \quad (16-64)$$

It can be shown, with some considerable algebraic effort, that the period of the output waveform is as follows:

$$T = 2RC \ln \left( \frac{2R_2}{R_1} + 1 \right) \quad (16-65)$$

$$f_o = \frac{1}{T} = \frac{1}{2RC \ln(2R_2 / R_1 + 1)} \quad (16-66)$$

However, if we select  $R_1$  and  $R_2$  such that  $(1 + 2R_2/R_1) = 2.178$  (the natural log base), then  $\ln(1 + 2R_2/R_1)$  will equal unity.

$$\frac{2R_2}{R_1} + 1 = 2.718 \quad (16-67)$$

$$2R_2 = 1.718R_1 \quad (16-68)$$

$$R_2 = 0.859R_1 \quad (16-69)$$


Hence, the output frequency is a function of  $R$  and  $C$  only, and its equation simplifies as follows:

$$f_o = \frac{1}{2RC} \quad (16-70)$$



## 16.8 THE 555 TIMER

The 555 timer is a popular 8-pin integrated circuit (IC), which may be used in many applications including rectangular waveform generation. Figure 16-17 shows the common configuration of the 555 timer as it is connected to produce a rectangular waveform.

 

**Figure 16-17:** The 555 timer connected as a rectangular waveform generator

The time duration for which the output is high ( $t_H$ ) is given by the following equation:

$$t_H = 0.69(R_1 + R_2)C \quad (16-71)$$

The time duration for which the output is low ( $t_L$ ) is given by the following equation:


$$t_L = 0.69(R_2)C \quad (16-72)$$

Therefore, the period and frequency of the waveform are as follows:


$$T = t_H + t_L = 0.69(R_1 + 2R_2)C \quad (16-73)$$

$$f_o = \frac{1}{T} = \frac{1}{0.69(R_1 + 2R_2)C} \quad (16-74)$$

For a rectangular waveform, the ratio of the pulse duration ( $t_H$ ) to the period  $T$  is referred to as the *duty cycle* ( $d$ ) of the waveform. A square wave is a rectangular waveform with  $d = 0.5$  or 50% duty cycle. Examining the equations for  $t_H$  and  $t_L$ , we notice that it would not be possible to produce a square wave with the circuit of Figure 16-16. However, there is a simple solution for this problem, and that is to connect a diode across the  $R_2$  and let  $R_1 = R_2 = R$ , as illustrated in Figure 16-18(a).

 

(a) Circuit diagram

 

(b) Output waveform

**Figure 16-18:** The 555 timer connected as a square-wave generator

When the output is high, the diode is forward-biased, shorting out  $R_2$ ; hence,

$$t_H = 0.69(R_1)C = 0.69RC \quad (16-75)$$

When the output is low, the diode is unbiased, behaving like an open-circuit; hence,


$$t_L = 0.69(R_2)C = 0.69RC \quad (16-76)$$

$$T = t_H + t_L = 0.69RC + 0.69RC = 1.38RC \quad (16-77)$$


$$f_o = \frac{1}{T} = \frac{1}{1.38RC} \quad (16-78)$$

$$d = \frac{t_H}{T} = \frac{0.69RC}{1.38RC} = 0.5 \quad (16-79)$$

 In order to produce a rectangular waveform with a duty cycle less than 50% ( $t_H < t_L$ ), we can pick  $R_2$  larger than  $R_1$ , as required. However, the practical solution is to split  $R_2$  into a series combination of a fixed resistor and a potentiometer, so that  $R_2$  can be adjusted for a desired duty cycle.



(a) Circuit diagram

 

(b) Output waveform

**Figure 16-19:** Rectangular waveform generator of Design Example 16-6