

Seven Concepts

Seven Concepts that make this course worthwhile.

? ? ? ? ? ? ?

Ohm's Law
Joule's Law (*I Squared R Loss*)
Open Switch / Closed Switch
Multimeters
 Connect volt meter in parallel (*across potential*)
 Connect ammeter in series (*in-line flow*)
Product over the Sum (*Parallel Resistors*)
Voltage Divider

Ohm's Law

The current (I) is proportional to the voltage (V)

$I \propto V$ (The current is linearly proportional to the voltage)

$$I = \frac{1}{R}V$$

$I = V / R$ Note: $1/R$ is the slope of the current voltage curve

$$V = I R$$

$$R = V / I$$


Joule's Law (Power)

$$P = I V$$

$$P = (V / R) V = V^2 / R \quad \text{from } I = V / R$$


$$P = I (I R) = I^2 R \quad \text{from } V = I R$$

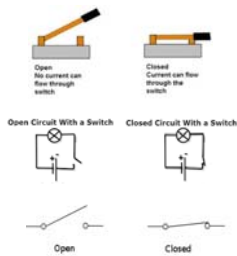
Note: $P = I^2 R$ is the so called "I squared R loss" (heat loss)




Open Switch = No Current Flow
 Voltage across Switch = Supply Voltage
 Voltage across Load = Zero

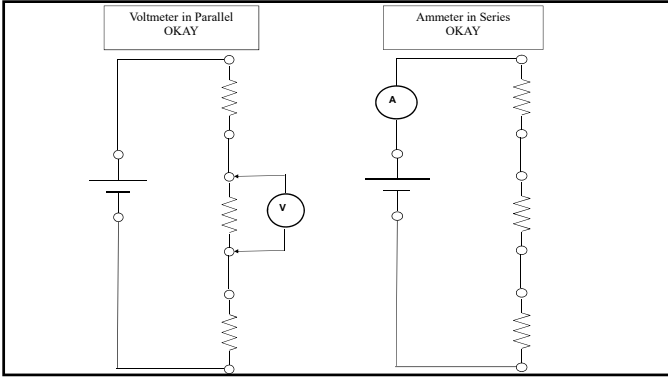
Closed Switch = Maximum Current Flow
 Voltage across Switch = Zero
 Voltage across Load = Supply Voltage



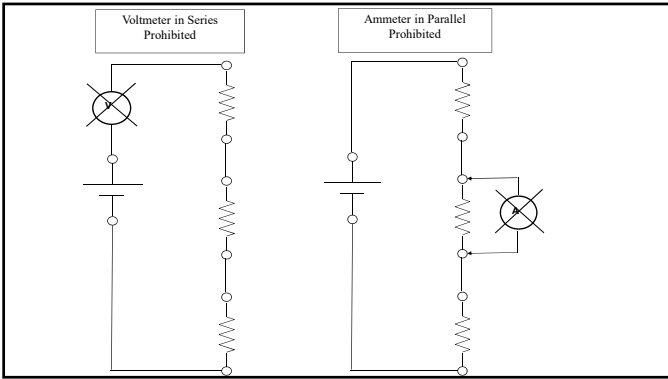

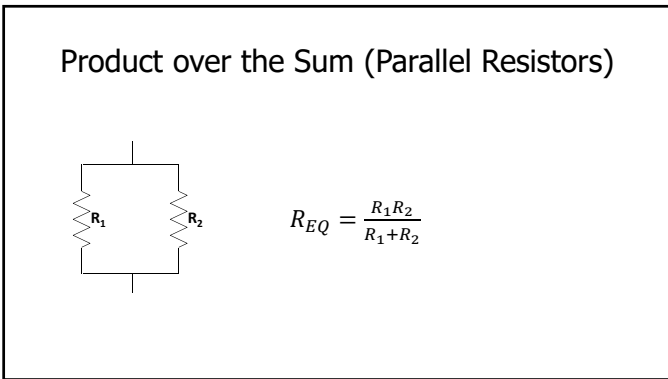

Voltage Divider

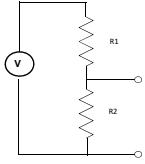

$$V_{R_2} = V \frac{R_2}{R_1 + R_2}$$
