

BJT Biasing Homework Problems


1. Emitter Biased, Common Emitter

Determine the quiescent operating point (I_{CQ} & V_{CEQ}) and $V_{CE \text{ Cut-off}}$ & $I_{C \text{ Saturation}}$

$$\begin{aligned}\beta &= 150 \\ V_{CC} &= 10 \text{ V} \\ R_B &= 300 \text{ K } \Omega \\ R_C &= 1100 \Omega\end{aligned}$$

Find:

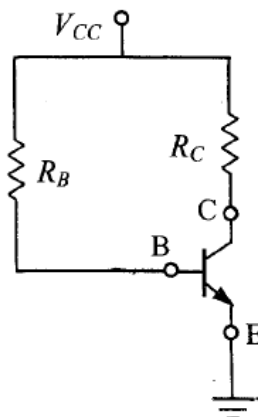- Quiescent Current I_{CQ}
- Quiescent Voltage V_{CEQ}
- $V_{CE \text{ Cut-off}}$
- $I_{C \text{ Saturation}}$




2. Emitter Biased, Common Emitter with Emitter Resistor

Determine the quiescent operating point (I_{CQ} & V_{CEQ}) and $V_{CE \text{ Cut-off}}$ & $I_{C \text{ Saturation}}$

$$\begin{aligned}\beta &= 180 \\ V_{CC} &= 16 \text{ V} \\ R_B &= 330 \text{ K } \Omega \\ R_C &= 1100 \Omega \\ R_E &= 550 \Omega\end{aligned}$$

Find:

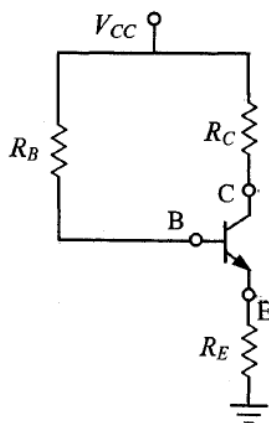- Quiescent Current I_{CQ}
- Quiescent Voltage V_{CEQ}
- $V_{CE \text{ Cut-off}}$
- $I_{C \text{ Saturation}}$




BJT Biasing Homework Problems

3. Voltage-Divider Biased, Common Emitter Configuration

Calculate the quiescent points (I_{CQ} and V_{CEQ})

And determine $V_{CE \text{ Cut-off}}$ and $I_{C \text{ Saturation}}$
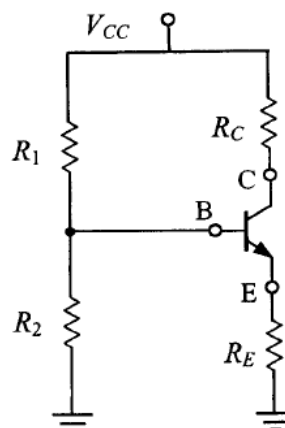
$$\begin{aligned} \beta &= 100 \\ V_{CC} &= 16 \text{ V} \\ R_1 &= 47\text{K } \Omega \\ R_2 &= 12\text{K } \Omega \\ R_C &= 2200 \Omega \\ R_E &= 1800 \Omega \end{aligned}$$



Find:

- a. Quiescent Current I_{CQ}
- b. Quiescent Voltage V_{CEQ}
- c. $V_{CE \text{ Cut-off}}$
- d. $I_{C \text{ Saturation}}$


4. Voltage-Divider Biased, Cascaded Amplifier

Calculate the quiescent points (I_{CQ} and V_{CEQ}) for Q_1 and Q_2 .

$$\begin{aligned} \beta_1 \text{ and } \beta_2 &= 100 \\ V_{CC} &= 21 \text{ V} \\ R_1 &= 47\text{K } \Omega \\ R_2 &= 10\text{K } \Omega \\ R_3 &= 15\text{K } \Omega \\ R_C &= 1200 \Omega \\ R_E &= 1800 \Omega \end{aligned}$$


Find:

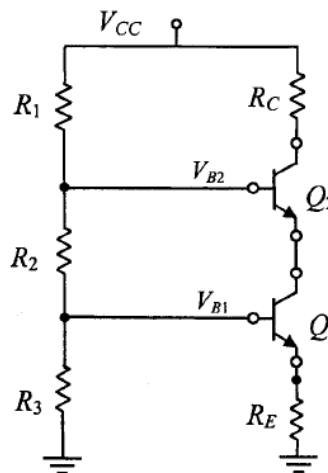- a. Q_1 I_{CQ}
- b. Q_1 V_{CEQ}
- c. Q_2 I_{CQ}
- d. Q_2 V_{CEQ}



BJT Biasing Homework Problems

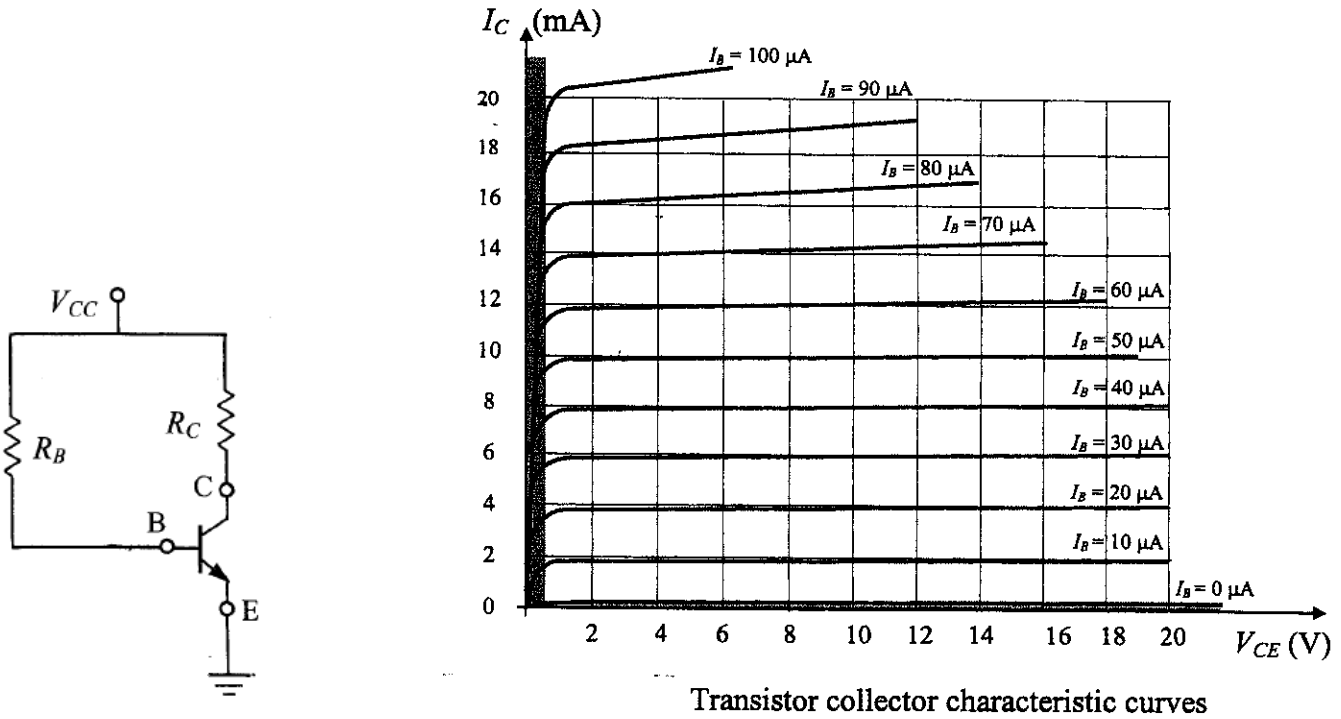5. Use the Collector Characteristic Curves for I_B , I_C , & V_{CE} to determine values for R_B and R_C for the BJT circuit below.



Set the quiescent point at approximately $I_{CQ} = 8 \text{ mA}$ and $V_{CEQ} = 9.5 \text{ V}$ with $V_{CC} = 16 \text{ Volts}$.

Hint: Use the chart to determine a value for $\beta = I_C / I_B$.

Calculate a value for R_B , consult the web or a catalog or your textbook to choose the nearest real world valued resistors and then recalculate values for I_B and I_C .

- Calculated value for R_B
- Real world value for R_B
- Re-calculated value for I_{BQ}
- Re-calculated value for I_{CQ}

Calculate a value for R_C , consult the web or a catalog or your textbook to choose the nearest real world valued resistors and then calculate values for V_{CEQ} , $I_{C \text{ sat}}$, and $V_{CE \text{ cut-off}}$

- Calculated value for R_C
- Real world value for R_C
- Calculated value for V_{CEQ}
- Calculated value for $I_{C \text{ sat}}$
- Re-calculated value for $V_{CE \text{ cut-off}}$

BJT Biasing Homework Solutions

1. Emitter Biased, Common Emitter

- $I_{CQ} = 4.65 \text{ mA}$
- $V_{CEQ} = 4.9 \text{ V}$
- $V_{CE \text{ Cut-off}} = 10 \text{ V}$
- $I_{C \text{ Saturation}} = 9.1 \text{ mA}$

2. Emitter Biased, Common Emitter with Emitter Resistor

- $I_{CQ} = 6.4 \text{ mA}$
- $V_{CEQ} = 5.4 \text{ V}$
- $V_{CE \text{ Cut-off}} = 16 \text{ V}$
- $I_{C \text{ Saturation}} = 9.7 \text{ mA}$

3. Voltage-Divider Biased, Common Emitter Configuration

- $I_{CQ} = 1.4 \text{ mA}$
- $V_{CEQ} = 10.4 \text{ V}$
- $V_{CE \text{ Cut-off}} = 16 \text{ V}$
- $I_{C \text{ Saturation}} = 4 \text{ mA}$

4. Voltage-Divider Biased, Cascaded Amplifier

- $Q_1 \ I_{CQ} = 2 \text{ mA}$
- $Q_1 \ V_{CEQ} = 2.9 \text{ V}$
- $Q_2 \ I_{CQ} = 2 \text{ mA}$
- $Q_2 \ V_{CEQ} = 12.0 \text{ V}$

5. Note: $\beta = 200$, for $I_B = 40 \mu\text{A}$ and $I_{CQ} = 8 \text{ mA}$, set Q at $I_{CQ} = 8 \text{ mA}$ and $V_{CEQ} = 9.5 \text{ V}$ with $V_{CC} = 16 \text{ Volts}$.

- First-cut value for $R_B = 382,500 \ \Omega$
- Pick $R_B = 390 \text{ K}\Omega$
- Re-calculated value for $I_{BQ} = 39.2 \ \mu\text{A}$
- Re-calculated value for $I_{CQ} = 7.84 \text{ mA}$
- First-cut value for $R_C = 829 \ \Omega$
- Pick $R_B = 820 \ \Omega$
- Calculated value for $V_{CEQ} = 9.6 \text{ V}$
- Calculated value for $I_{C \text{ sat}} = 20 \text{ mA}$
- Calculated value for $V_{CE \text{ cut-off}} = 16 \text{ V}$

Calculating Operating Points (Quiescent I_{CQ} & V_{CEQ}) for Voltage-Divider Biased BJT Cascaded Amplifiers

Caveats:

The following is NOT a computational algorithm; nor is it a step-by-step cookbook recipe to be followed blindly. But rather, it is a list of insights illustrating a generalized method for solving similar problems.

Refer to Take-Home Quiz cascading amplifier schematic.

Insights:

To find I_{CQ} , V_{CEQ1} , and V_{CEQ2}

1. $I_{C2} = I_{E2} = I_{C1} = I_{E1} = I_C$

2. V_{B1} is the voltage from the base of Q_1 to ground:

Voltage Divider
$$V_{B1} = V_{CC} \frac{R_3}{R_1 + R_2 + R_3}$$

Calculate V_{B1}

V_{B1} also equals
$$V_{B1} = V_{BE1} + I_C R_E$$

So
$$I_C = \frac{V_{B1} - V_{BE1}}{R_E} \quad \text{where } V_{BE1} = 0.7 \text{ V}$$

Calculate I_{CQ}

3. V_{B2} is the voltage from the base of Q_2 to ground:

Voltage Divider
$$V_{B2} = V_{CC} \frac{R_2 + R_3}{R_1 + R_2 + R_3}$$

Calculate V_{B2}

V_{B2} also equals
$$V_{B2} = V_{BE2} + V_{CE1} + I_C R_E$$

So
$$V_{CE1} = V_{B2} - V_{BE2} - I_C R_E \quad \text{where } V_{BE2} = 0.7 \text{ V}$$

Calculate V_{CEQ1}

4. Finally,
$$V_{CC} = I_C R_C + V_{CE2} + V_{CE1} + I_C R_E$$

So
$$V_{CE2} = V_{CC} - V_{CE1} - I_C (R_C + R_E)$$

Calculate V_{CEQ2}