

## Field Effect Transistor (FETs) Homework Problems

### JFET (Self-Biased) - Corrected


03-19-2017

$V_{DD} =$	+12 V
$R_G =$	470 K $\Omega$
$R_S =$	750 $\Omega$
$R_D =$	3300 $\Omega$
$I_{DSS} =$	12 mA
$V_{GS(off)} =$	-1.73 V
$V_{GS} =$	-1.12 V

Calculate:

$$I_{DQ}$$

$$V_{DSQ}$$

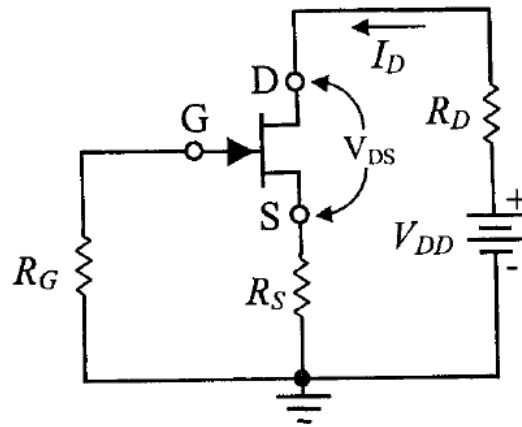


### JFET (Voltage Divider)

$V_{DD} =$	-15 V
$R_1 =$	750 K $\Omega$
$R_2 =$	120K $\Omega$
$R_D =$	1500 $\Omega$
$R_S =$	1200 $\Omega$
$I_{DSS} =$	-10 mA
$V_{GS(off)} =$	3.33 V
$V_{GS} =$	1.57 V

Calculate:

$$I_{DQ}$$

$$V_{DSQ}$$

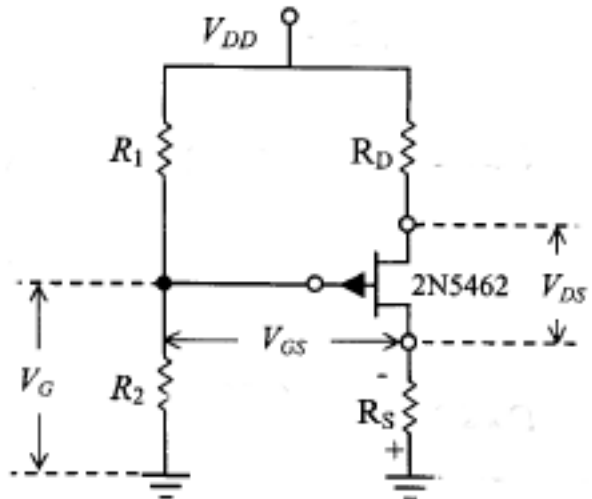

## FET Biasing Homework Solutions - corrected 03-19-2017

### 1. N Channel Self-Biased

$$I_{DQ} = 1.5 \text{ mA}$$

$$V_{DSQ} = 6.0 \text{ V}$$

### 2. P Channel Voltage Divider Biased

$$I_{DQ} = -3 \text{ mA}$$

$$V_{DSQ} = -6.8 \text{ V}$$