

Op-Amp Low Pass and High Pass Active Filters

Illustrated below are four configurations of Op-Amp Active Filters.

Identify each of them as either a Low Pass Filter or a High Pass Filter by simply analyzing the circuit behavior for input signal V_s at low frequency and at high frequency.

